

Chapter 1 Power Electronic Systems

Chapter 1 Power Electronic Systems	3
1-1 Introduction	3
1-2 Power Electronics versus Linear Electronics	4
1-3 Scope and Applications	7
1-4 Classification of Power Processors and Converters	9
1-5 About the Text	12
1-6 Interdisciplinary Nature of Power Electronics	13
1-7 Convention of Symbols Used	14
<i>Problems</i>	<i>14</i>
<i>References</i>	<i>15</i>

Power Electronic Systems


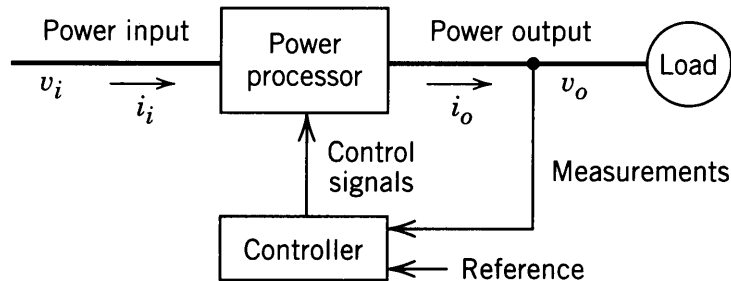
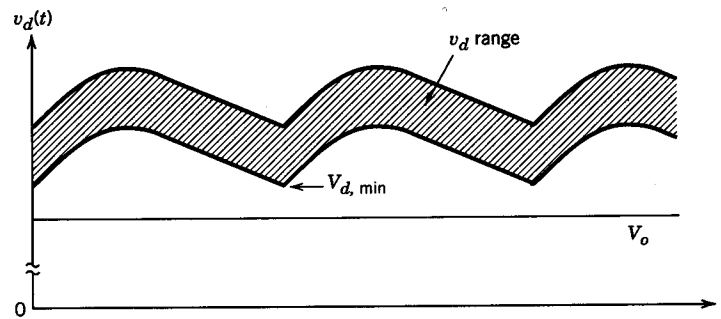


Figure 1-1 Block diagram of a power electronic system.


- Block diagram
- Role of Power Electronics
- Reasons for growth

Linear Power Supply

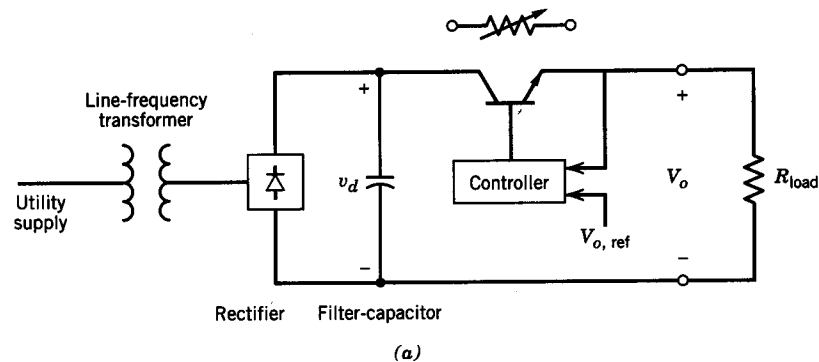


- Series transistor as an adjustable resistor
- Low Efficiency
- Heavy and bulky

Switch-Mode Power Supply

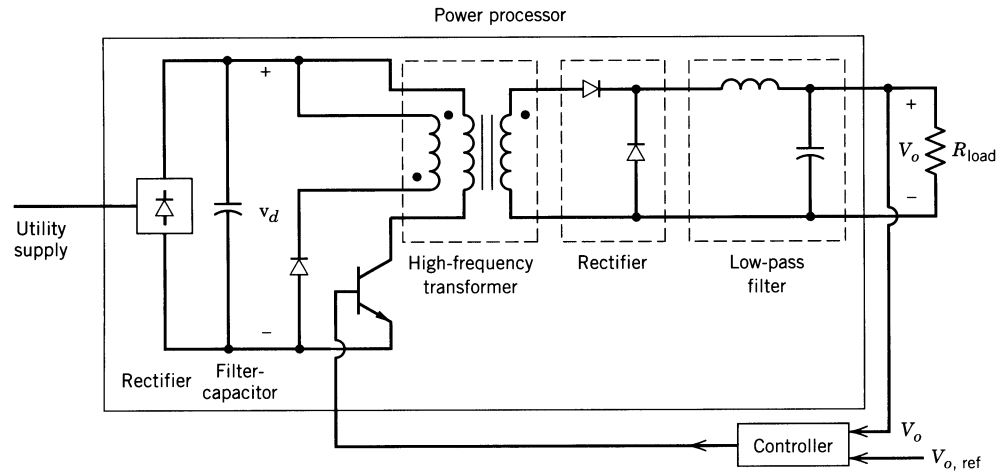

(a)

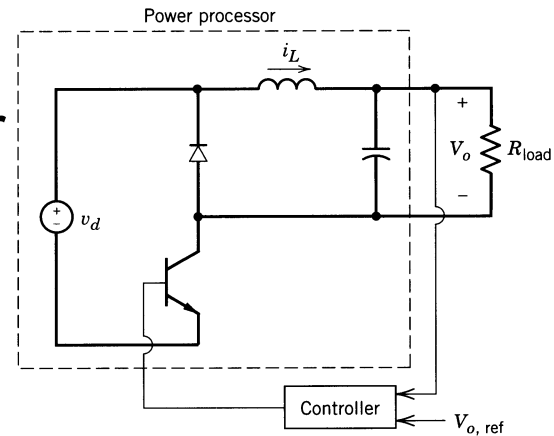
- Transistor as a switch
- High Efficiency
- High-Frequency Transformer




(b)

Figure 1-3 Switch-mode dc power supply.


Basic Principle of Switch-Mode Synthesis

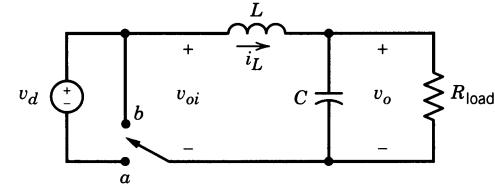


(a)

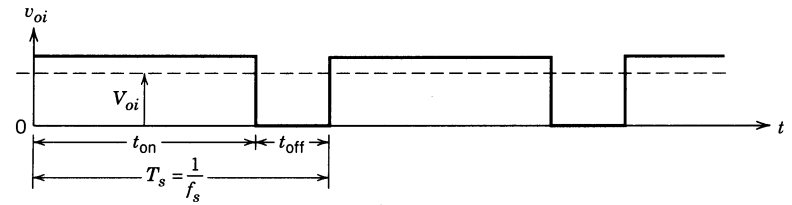

(b)

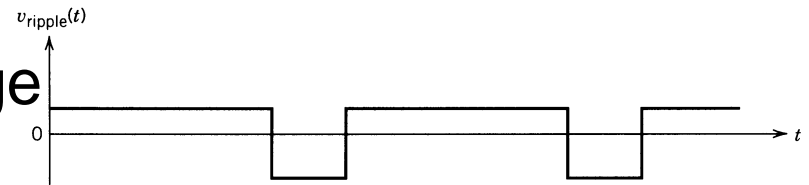

(c)

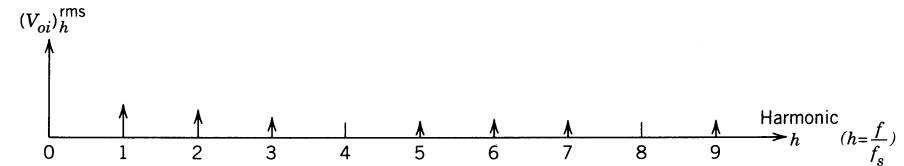

(d)

- Constant switching frequency
- pulse width controls the average
- L-C filters the ripple

Figure 1-4 Equivalent circuit, waveforms, and frequency spectrum of the supply in Fig. 1-3.

Application in Adjustable Speed Drives

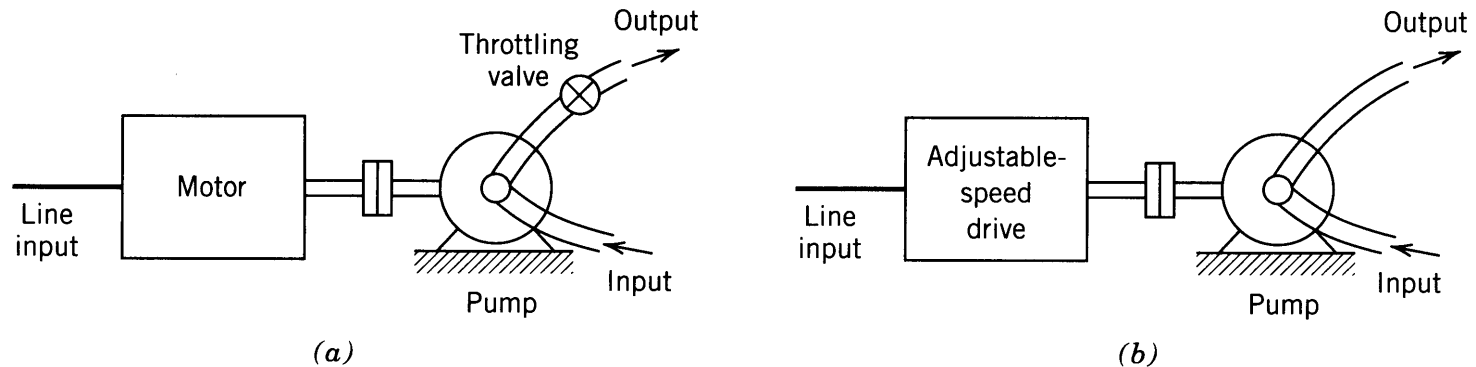


Figure 1-5 Energy conservation: (a) conventional drive, (b) adjustable-speed drive.

- Conventional drive wastes energy across the throttling valve to adjust flow rate
- Using power electronics, motor-pump speed is adjusted efficiently to deliver the required flow rate

Scope and Applications

TABLE 1-1 Power Electronic Applications

(a) <i>Residential</i> Refrigeration and freezers Space heating Air conditioning Cooking Lighting Electronics (personal computers, other entertainment equipment)	(d) <i>Transportation</i> Traction control of electric vehicles Battery chargers for electric vehicles Electric locomotives Street cars, trolley buses Subways Automotive electronics including engine controls
(b) <i>Commercial</i> Heating, ventilating, and air conditioning Central refrigeration Lighting Computers and office equipment Uninterruptible power supplies (UPSs) Elevators	(e) <i>Utility systems</i> High-voltage dc transmission (HVDC) Static var compensation (SVC) Supplemental energy sources (wind, photovoltaic), fuel cells Energy storage systems Induced-draft fans and boiler feedwater pumps
(c) <i>Industrial</i> Pumps Compressors Blowers and fans Machine tools (robots) Arc furnaces, induction furnaces Lighting Industrial lasers Induction heating Welding	(f) <i>Aerospace</i> Space shuttle power supply systems Satellite power systems Aircraft power systems (g) <i>Telecommunications</i> Battery chargers Power supplies (dc and UPS)

Power Processor as a Combination of Converters

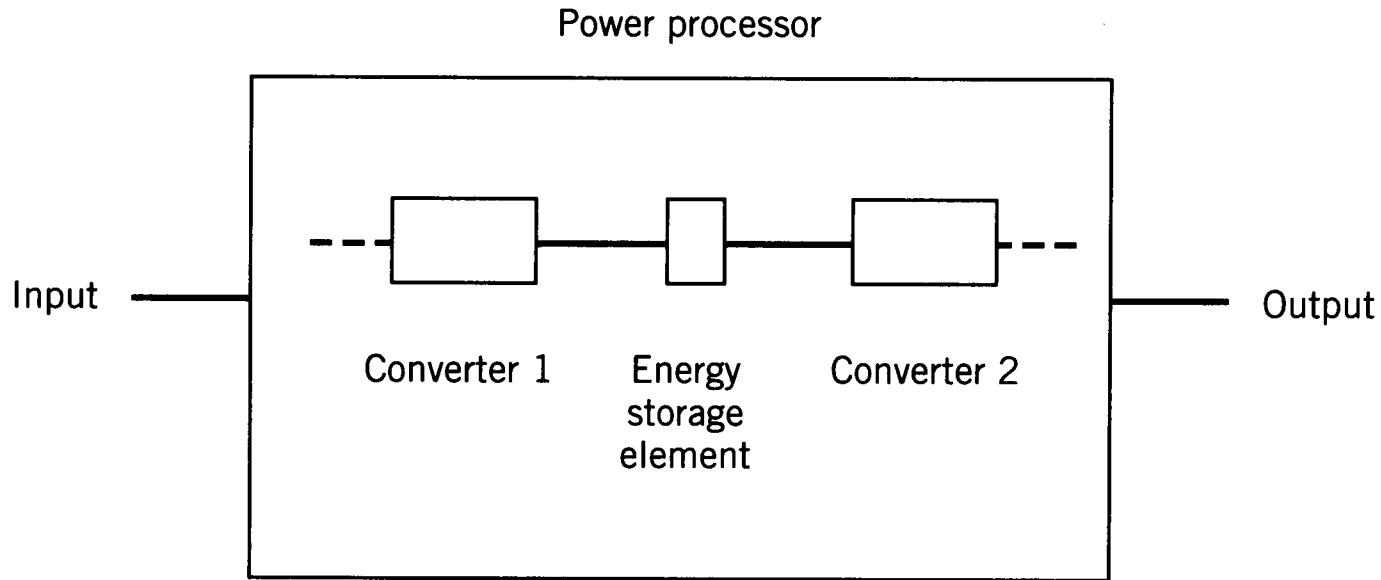


Figure 1-6 Power processor block diagram.

- Most practical topologies require an energy storage element, which also decouples the input and the output side converters

Power Flow through Converters

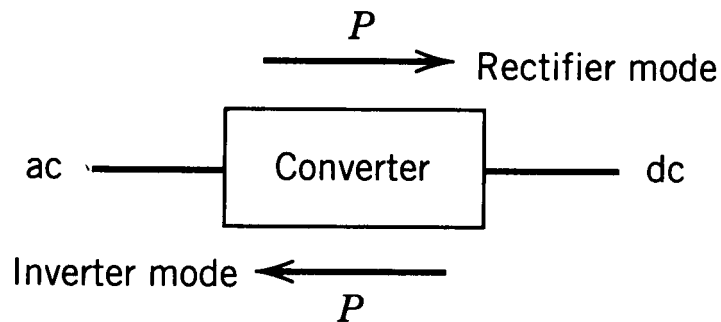


Figure 1-7 ac-to-dc converters.

- Converter is a general term
- An ac/dc converter is shown here
- Rectifier Mode of operation when power from ac to dc
- Inverter Mode of operation when power from ac to dc

AC Motor Drive

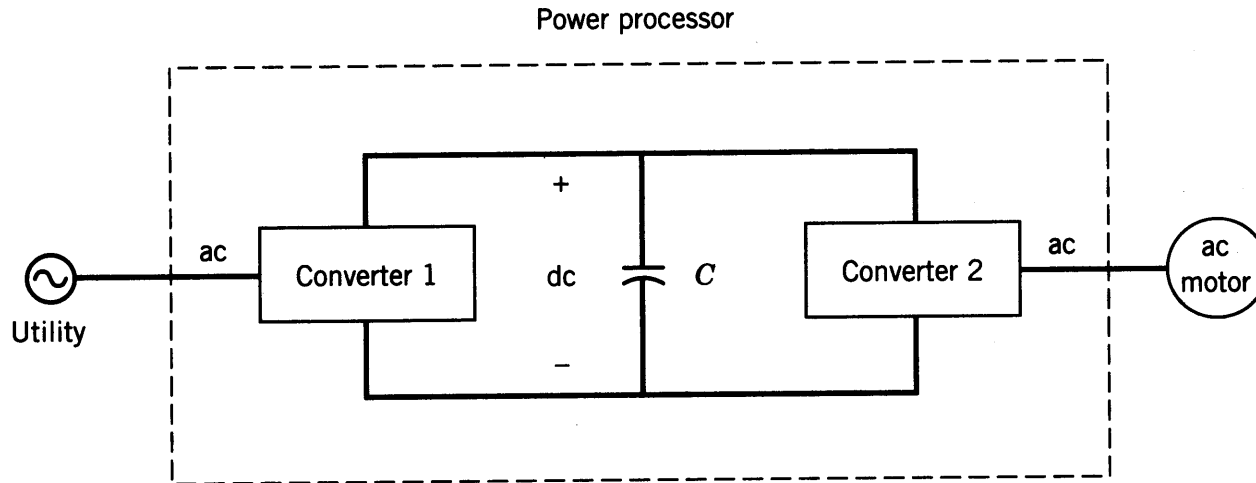


Figure 1-8 Block diagram of an ac motor drive.

- Converter 1 rectifies line-frequency ac into dc
- Capacitor acts as a filter; stores energy; decouples
- Converter 2 synthesizes low-frequency ac to motor
- Polarity of dc-bus voltage remains unchanged
 - ideally suited for transistors of converter 2

Matrix Converter

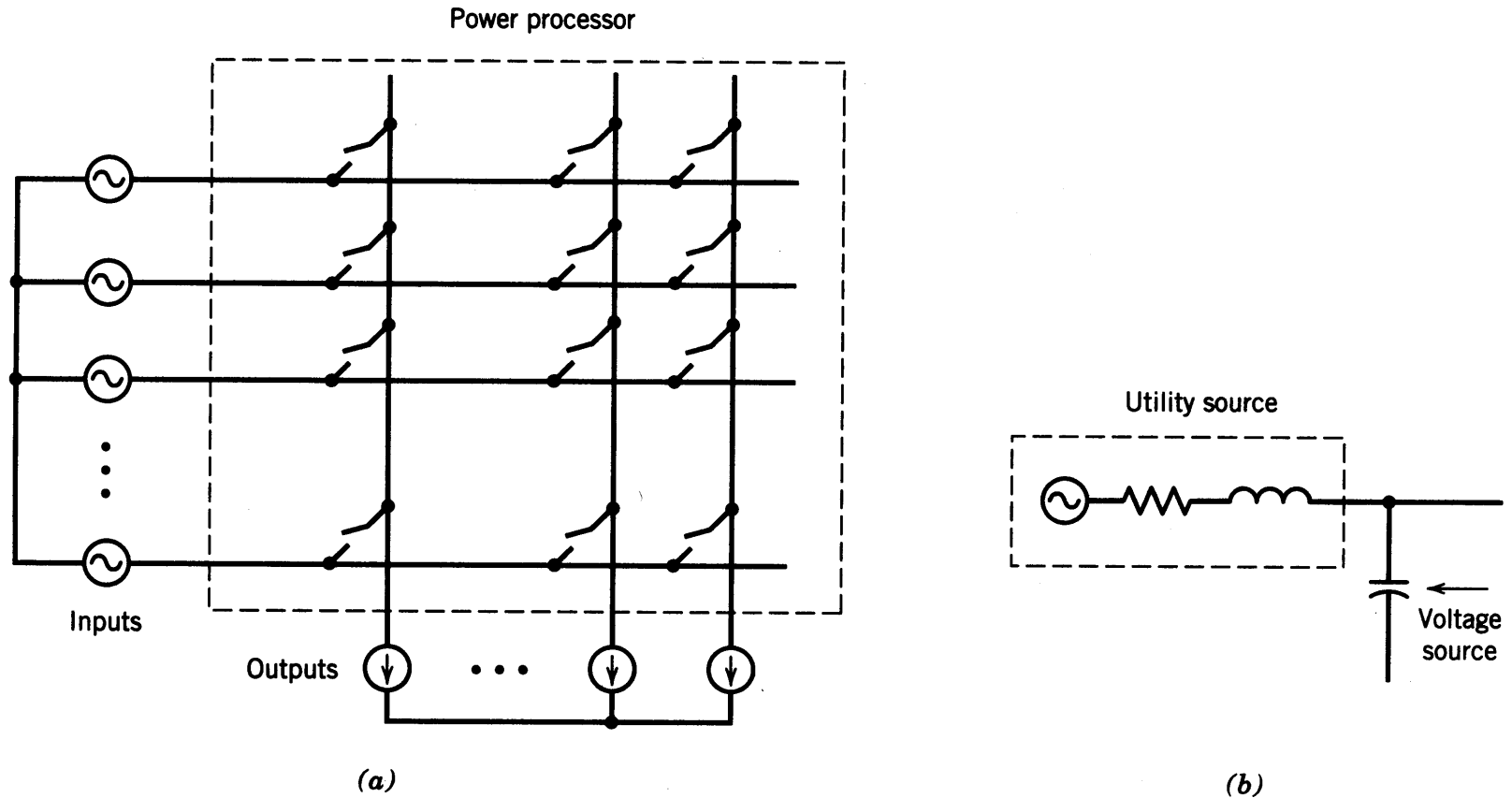


Figure 1-9 (a) Matrix converter. (b) Voltage source.

- Very general structure
- Would benefit from bi-directional and bi-polarity switches
- Being considered for use in specific applications

Interdisciplinary Nature of Power Electronics

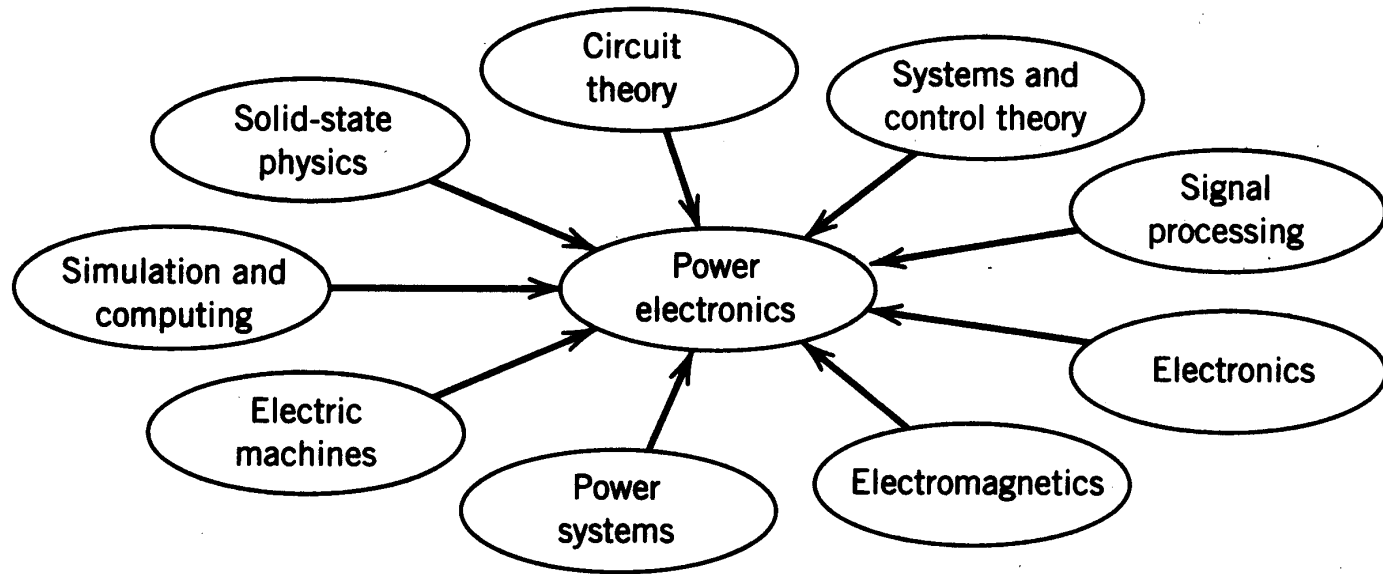


Figure 1-10 Interdisciplinary nature of power electronics.