


# Chapter 11

## Power Conditioners and Uninterruptible Power Supplies

<b>Chapter 11 Power Conditioners and Uninterruptible Power Supplies</b>	<b>354</b>
11-1 Introduction	354
11-2 Power Line Disturbances	354
11-3 Power Conditioners	357
11-4 Uninterruptible Power Supplies (UPSs)	358
<i>Summary</i>	363
<i>Problems</i>	363
<i>References</i>	364

- Becoming more of a concern as utility de-regulation proceeds

# Distortion in the Input Voltage

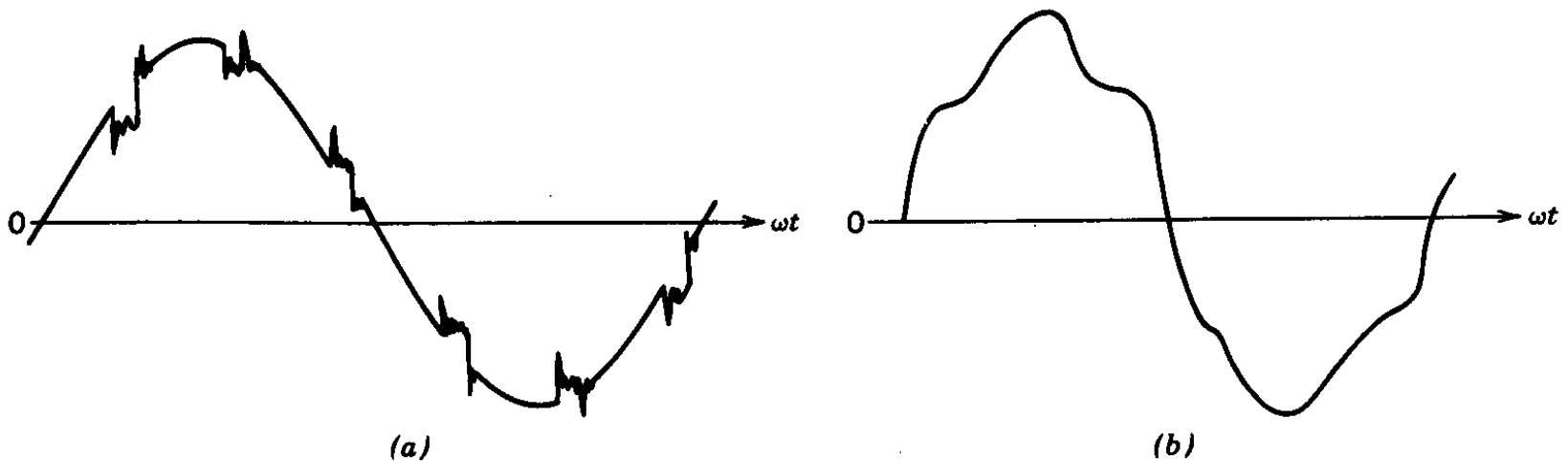

**Figure 11-1** Possible distortions in input voltage: (a) chopped voltage waveform; (b) distorted voltage waveform due to harmonics.

- The voltage supplied by the utility may not be sinusoidal

# Typical Voltage Tolerance Envelope for Computer Systems

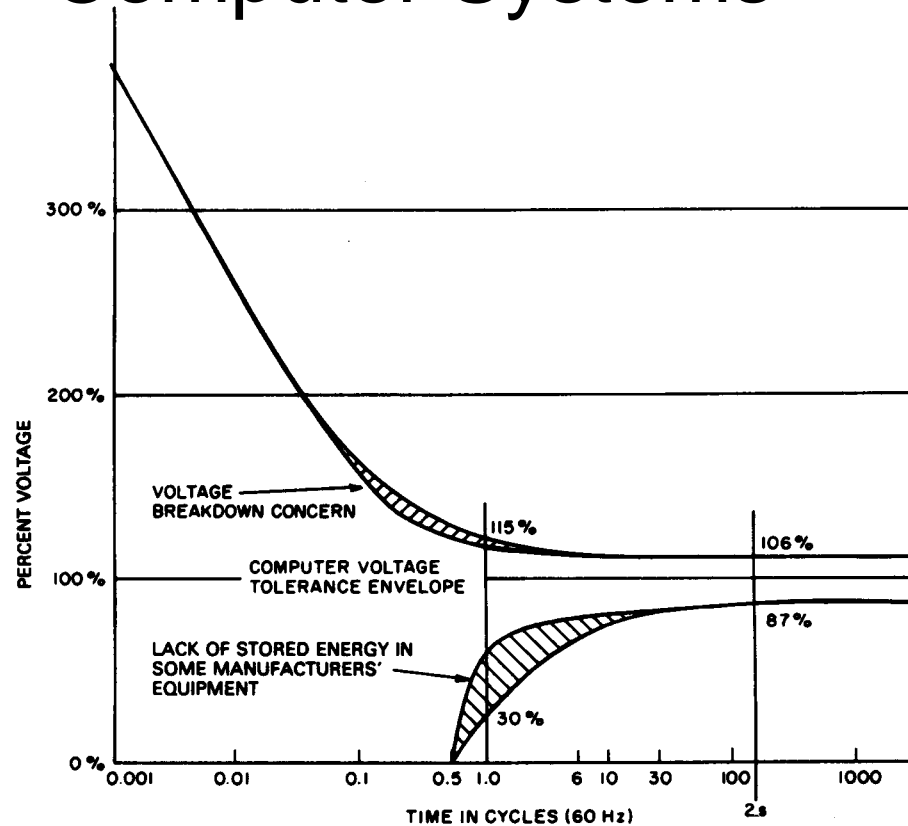


Figure 11-2 Typical computer system voltage tolerance envelope. (Source: IEEE Std. 446, "Recommended Practice for Emergency and Standby Power Systems for Industrial and Commercial Applications.")

- This has been superseded by a more recent standard

# Typical Range of Input Power Quality

**Table 11-1** Typical Range of Input Power Quality and Load Parameters of Major Computer Manufacturers

<i>Parameters<sup>a</sup></i>	<i>Range or Maximum</i>
1. Voltage regulation, steady state	+5, -10 to +10%, -15% (ANSI C84.1—1970 is +6, -13%)
2. Voltage disturbances	
a. Momentary undervoltage	-25 to -30% for less than 0.5 s, with -100% acceptable for 4–20 ms
b. Transient overvoltage	+150 to 200% for less than 0.2 ms
3. Voltage harmonic distortion <sup>b</sup>	3–5% (with linear load)
4. Noise	No standard
5. Frequency variation	60 Hz ± 0.5 Hz to ±1 Hz
6. Frequency rate of change	1 Hz/s (slew rate)
7. 3φ, Phase voltage unbalance <sup>c</sup>	2.5–5%
8. 3φ, Load unbalance <sup>d</sup>	5–20% maximum for any one phase
9. Power factor	0.8–0.9
10. Load demand	0.75–0.85 (of connected load)

<sup>a</sup>Parameters 1, 2, 5, and 6 depend on the power source, while parameters 3, 4, and 7 are the product of an interaction of source and load, and parameters 8, 9, and 10 depend on the computer load alone.

<sup>b</sup>Computed as the sum of all harmonic voltages added vectorially.


<sup>c</sup>Computed as follows:

$$\text{Percent phase voltage unbalance} = \frac{3(V_{\max} - V_{\min})}{V_a + V_b + V_c} \times 100$$

<sup>d</sup>Computed as difference from average single-phase load.

*Source:* IEEE Std. 446, “Recommended Practice for Emergency and Standby Power Systems for Industrial and Commercial Applications.”


# Electronic Tap Changers

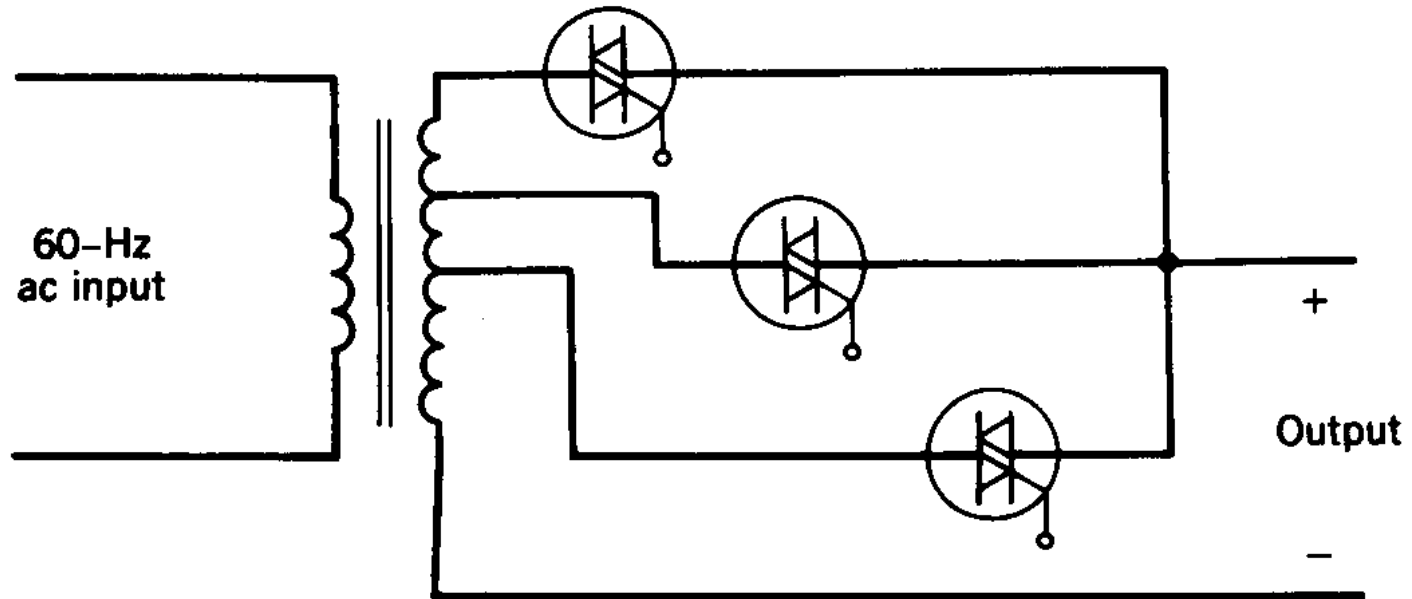

**Figure 11-3** Electronic tap changer.

- Controls voltage magnitude by connecting the output to the appropriate transformer tap


# Uninterruptible Power Supplies (UPS)

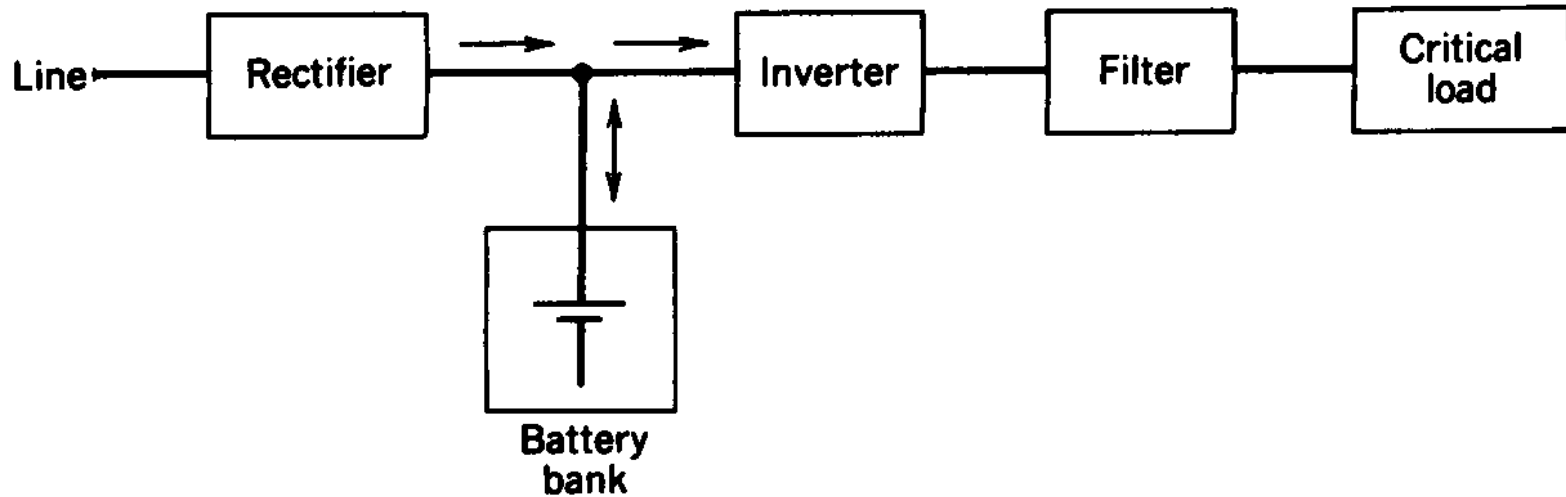

**Figure 11-4** A UPS block diagram.

- Block diagram; energy storage is shown to be in batteries but other means are being investigated


# UPS: Possible Rectifier Arrangements

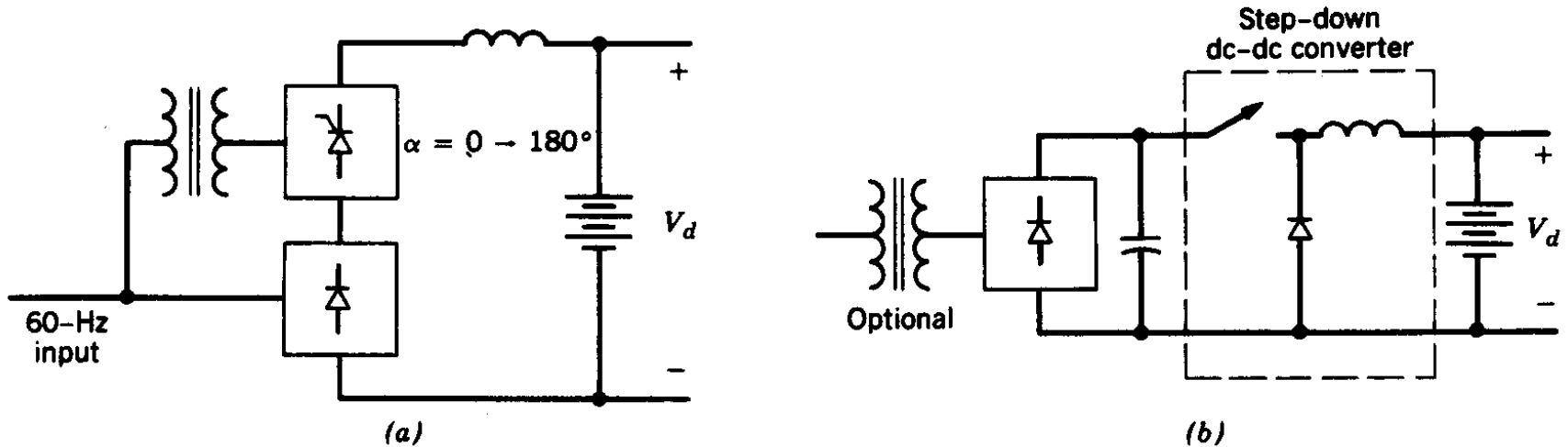

**Figure 11-5** Possible rectifier arrangements.

- The input normally supplies power to the load as well as charges the battery bank

# UPS: Another Possible Rectifier Arrangement

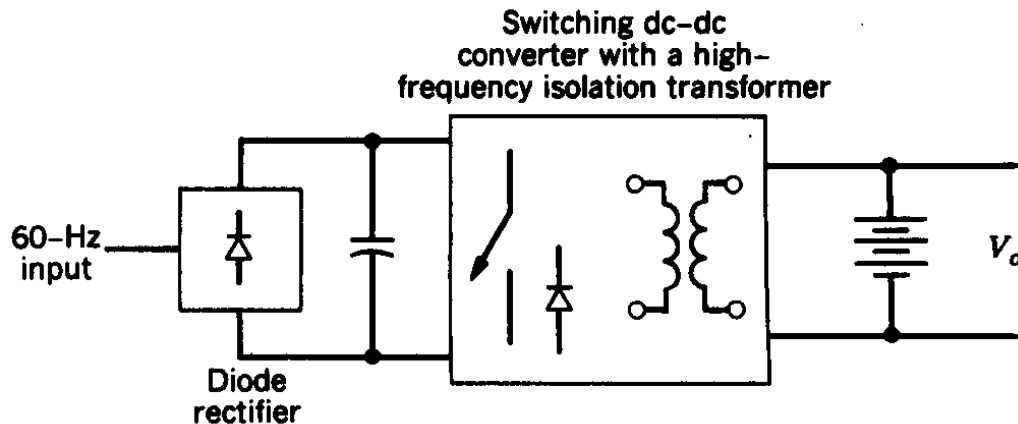


**Figure 11-6** Rectifier consisting of a high-frequency isolation transformer.

- Consists of a high-frequency isolation transformer




# UPS: Another Possible Input Arrangement

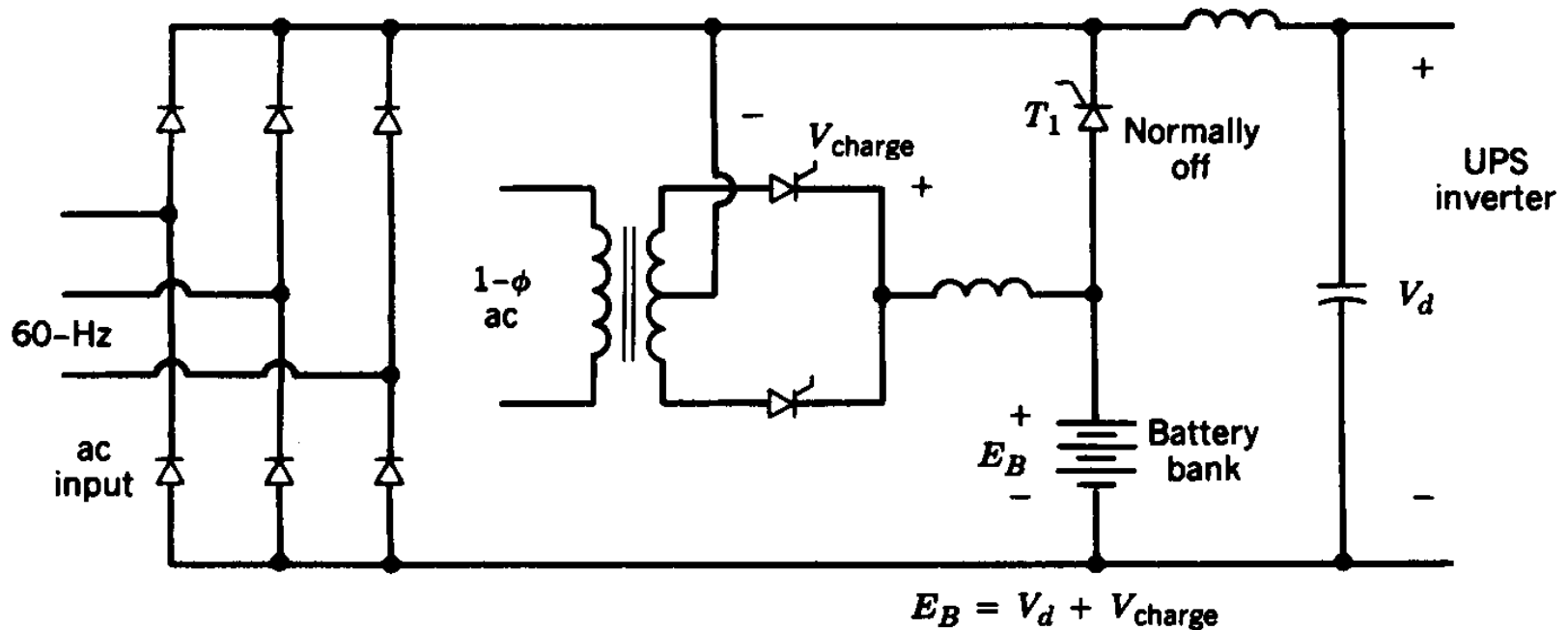

**Figure 11-7** A rectifier with a separate battery charger circuit.

- A separate small battery charger circuit

# Battery Charging Waveforms as Function of Time

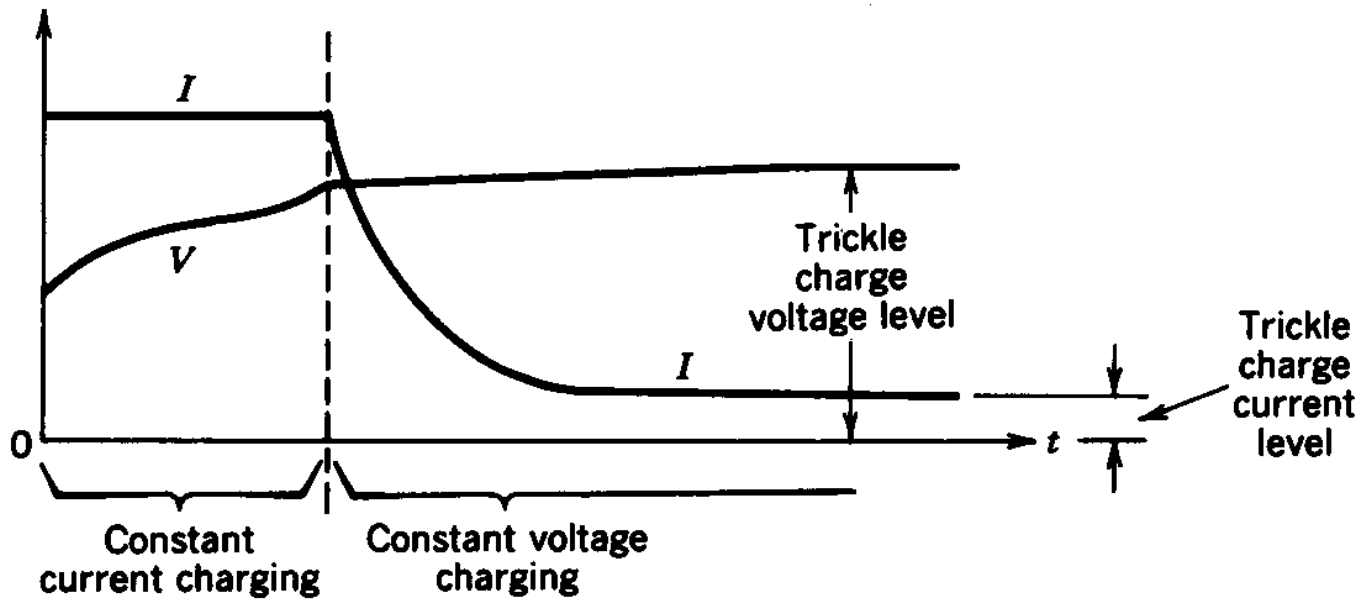

**Figure 11-8** Charging of a battery after a line outage causes battery discharge.

- Initially, a discharged battery is charged with a constant current

# UPS: Various Inverter Arrangements


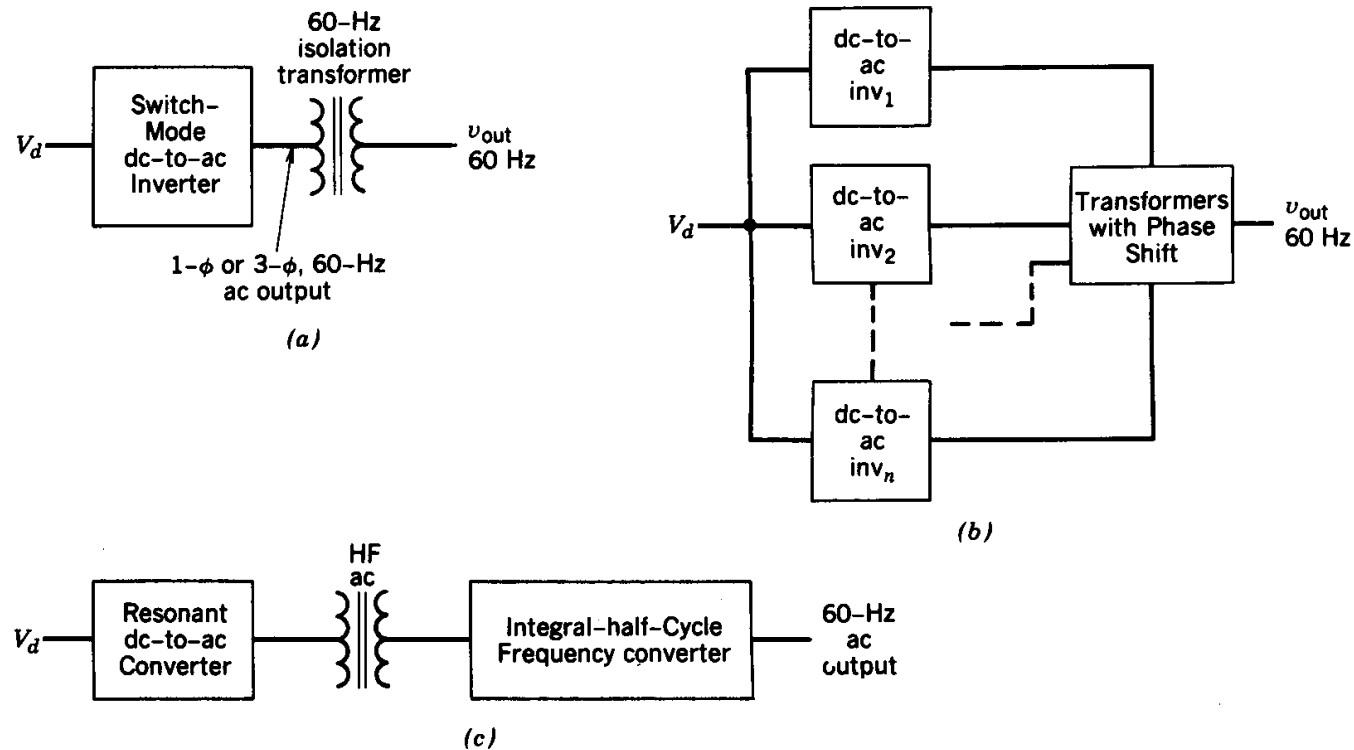


Figure 11-9 Various inverter arrangements.

- Depends on applications, power ratings


# UPS: Control

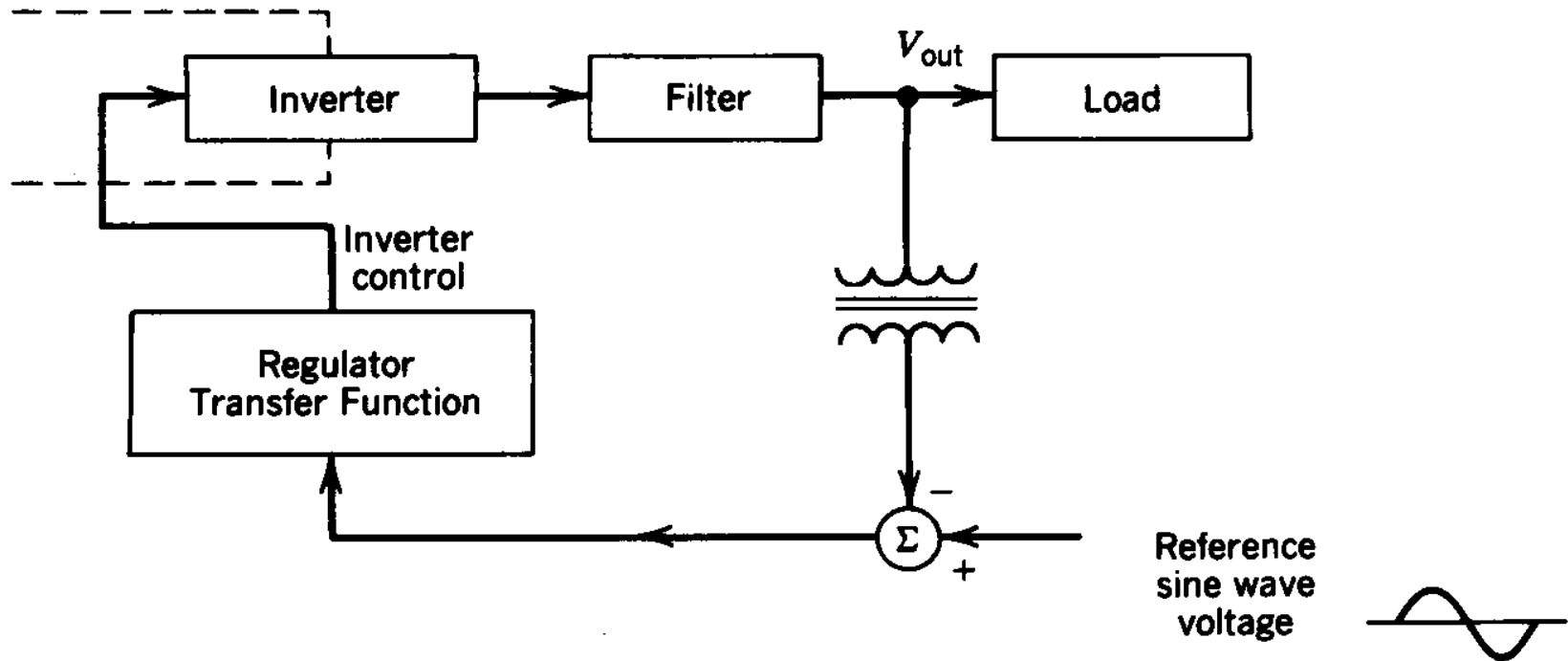

**Figure 11-10** Uninterruptible power supply control.

- Typically the load is highly nonlinear and the voltage output of the UPS must be as close to the desired sinusoidal reference as possible


# UPS Supplying Several Loads

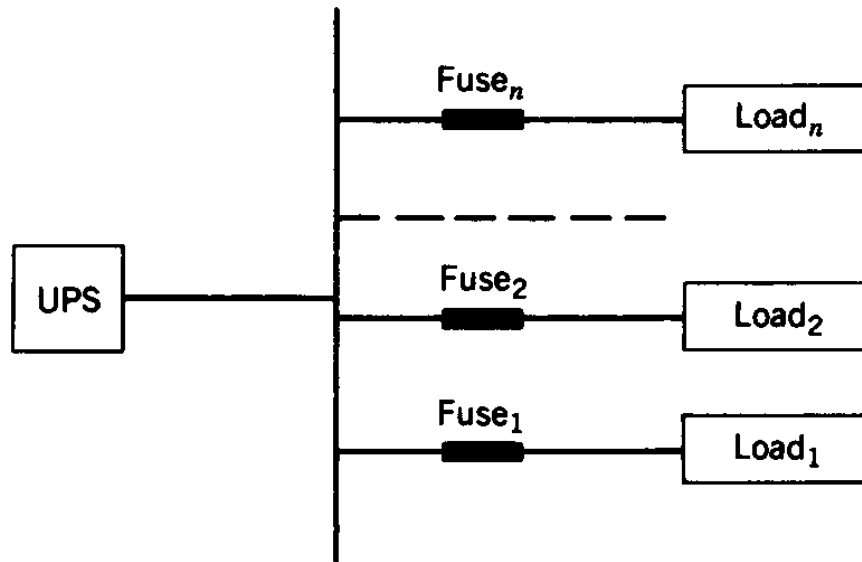

**Figure 11-11** A UPS supplying several loads.

- With higher power UPS supplying several loads, malfunction within one load should not disturb the other loads


# Another Possible UPS Arrangement

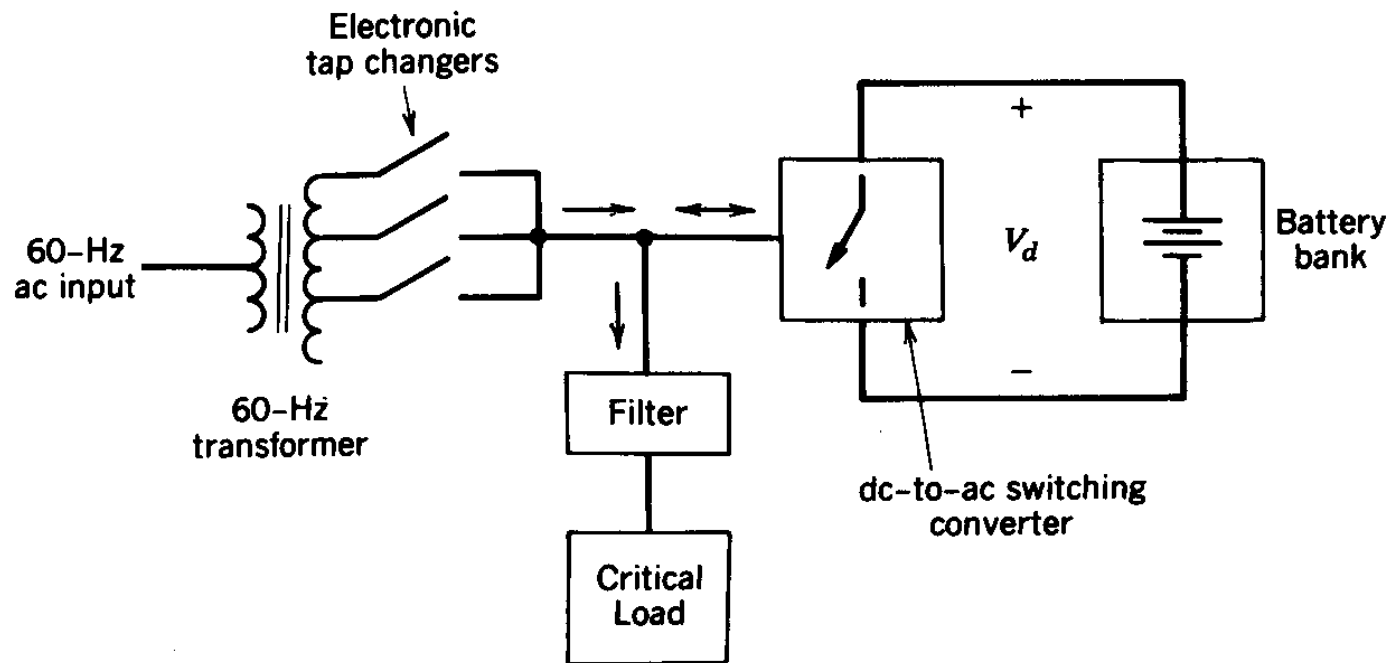

**Figure 11-12** A UPS arrangement where the functions of battery charging and inverter are combined.

- Functions of battery charging and the inverter are combined

# UPS: Using the Line Voltage as Backup

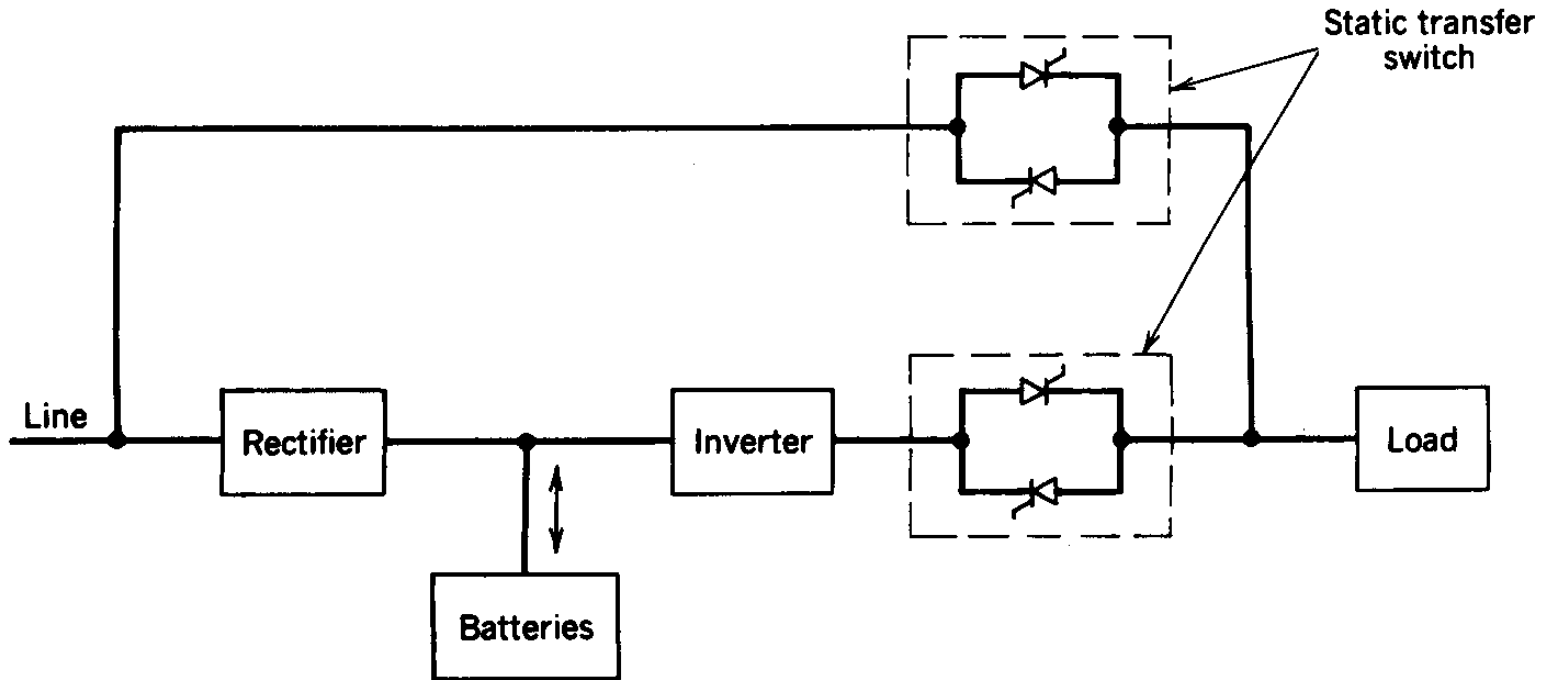

**Figure 11-13** Line as backup.

- Needs static transfer switches