


# Chapter 13

## DC-Motor Drives

<b>Chapter 13</b>	<b>dc Motor Drives</b>	<b>377</b>
13-1	Introduction	377
13-2	Equivalent Circuit of dc Motors	377
13-3	Permanent-Magnet dc Motors	380
13-4	dc Motors with a Separately Excited Field Winding	381
13-5	Effect of Armature Current Waveform	382
13-6	dc Servo Drives	383
13-7	Adjustable-Speed dc Drives	391
	<i>Summary</i>	396
	<i>Problems</i>	396
	<i>References</i>	398

- These drives continue to be used


# DC-Motor Structure

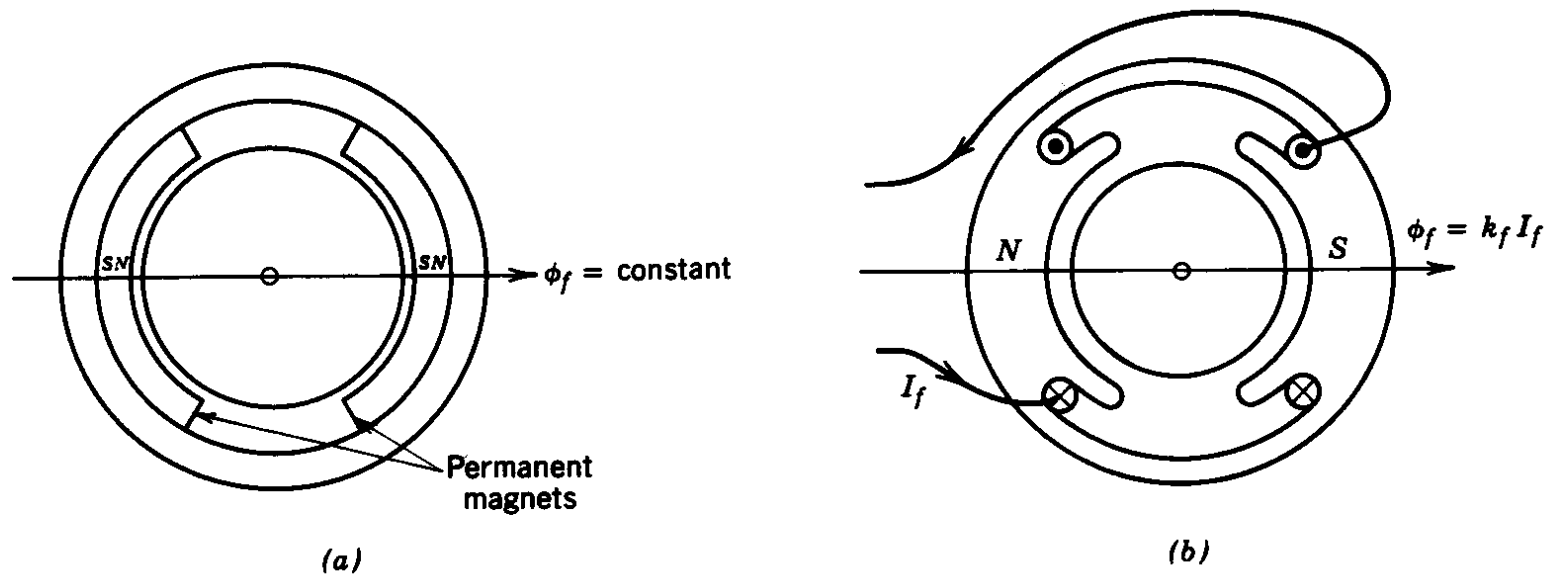

**Figure 13-1** A dc motor: (a) permanent-magnet motor; (b) dc motor with a field winding.

- With permanent magnets or a wound field


# DC-Motor Equivalent Circuit

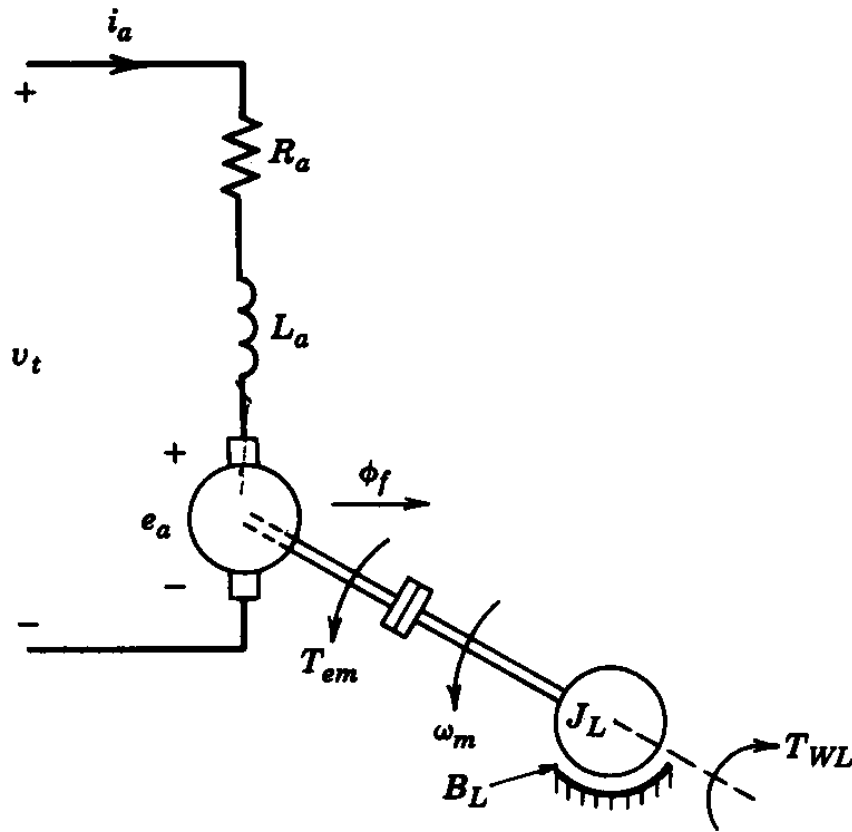

**Figure 13-2** A dc motor equivalent circuit.

- The mechanical system can also be represented as an electrical circuit


# Four-Quadrant Operation of DC-Motor Drives

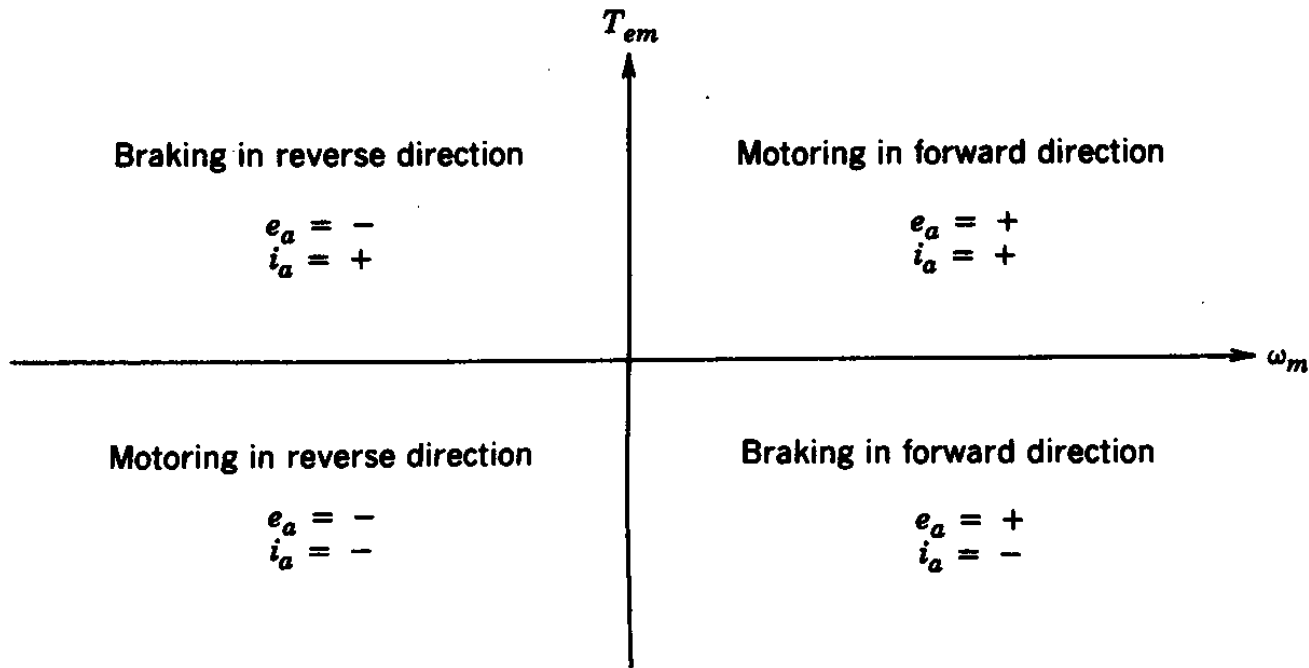

**Figure 13-3** Four-quadrant operation of a dc motor.

- High performance drives may operate in all four quadrants


# DC-Motor Drive Torque-Speed Characteristics and Capabilities

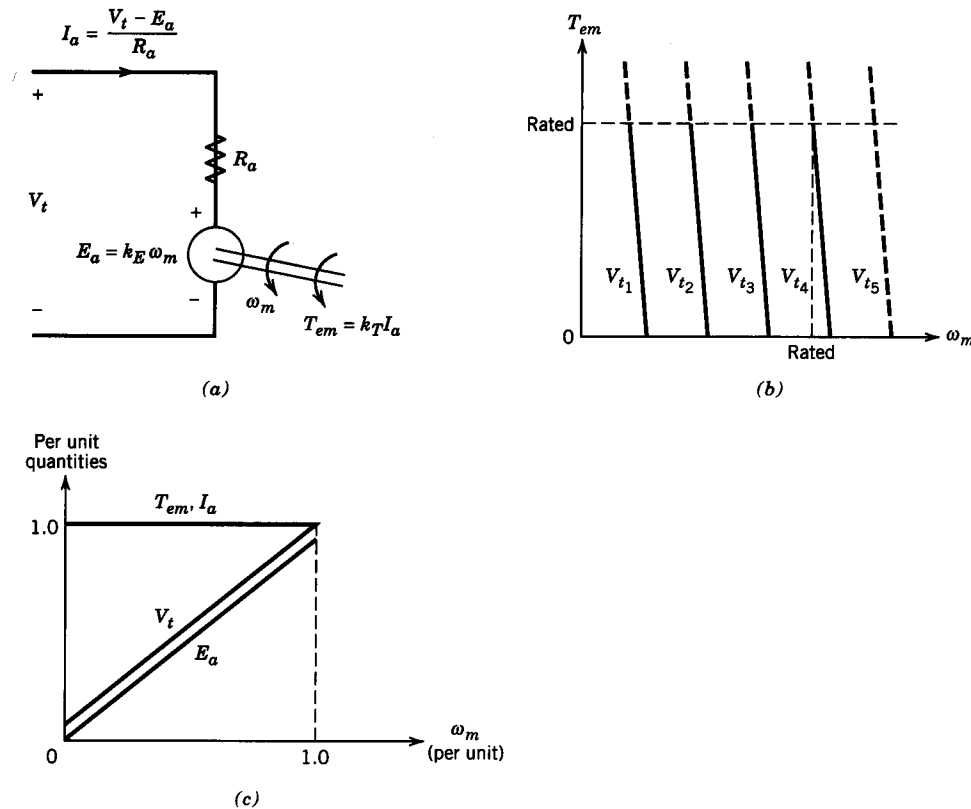


**Figure 13-4** Permanent-magnet dc motor: (a) equivalent circuit; (b) torque-speed characteristics:  $V_{t5} > V_{t4} > V_{t3} > V_{t2} > V_{t1}$ , where  $V_{t4}$  is the rated voltage; (c) continuous torque-speed capability.

- With permanent magnets

# DC-Motor Drive Capabilities

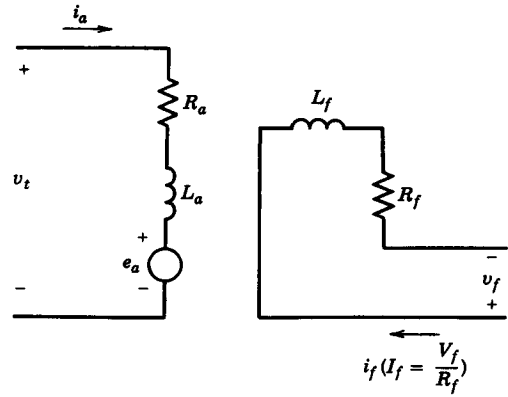


(a)

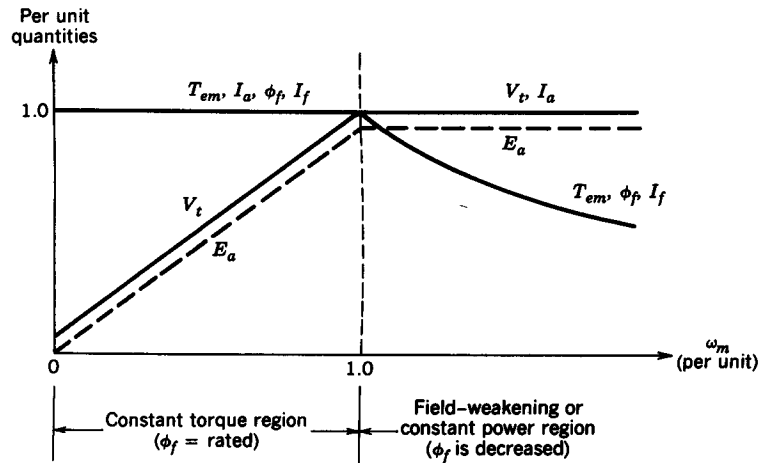

**Figure 13-5** Separately excited dc motor: (a) equivalent circuit; (b) continuous torque–speed capability.

- Separately-Excited field


# Controlling Torque, Speed and Position

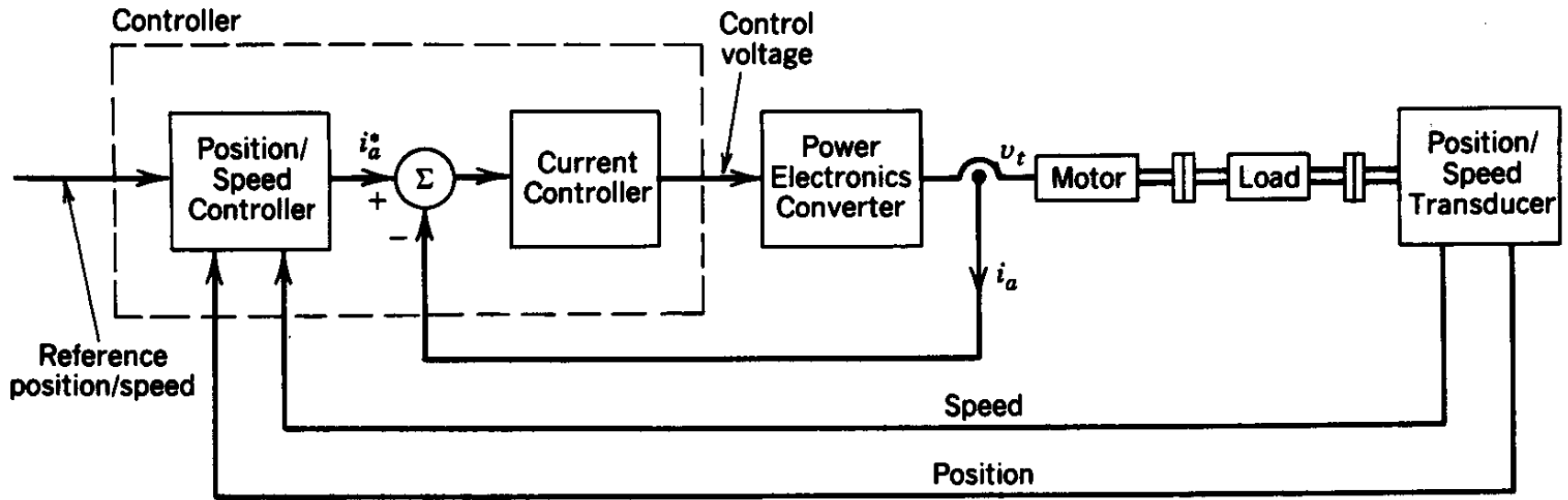

**Figure 13-6** Closed-loop position/speed dc servo drive.

- Cascaded control is commonly used

# Small-Signal Representation of DC Machines

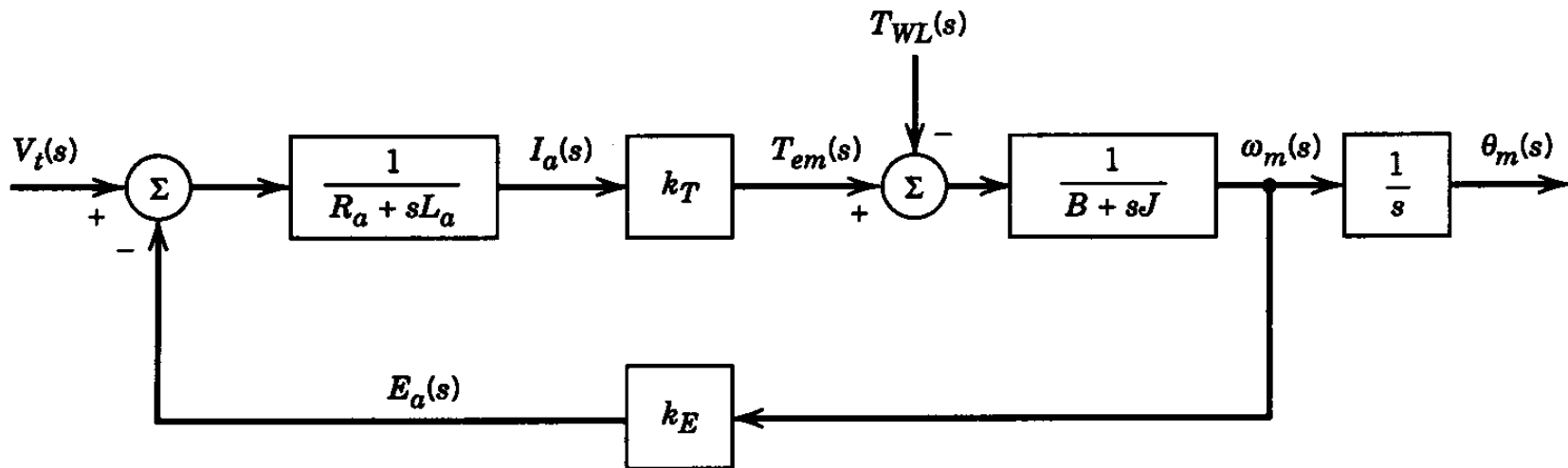


**Figure 13-7** Block diagram representation of the motor and load (without any feedback).

- Around a steady state operating point




# Electrical Time-Constant of the DC Machine

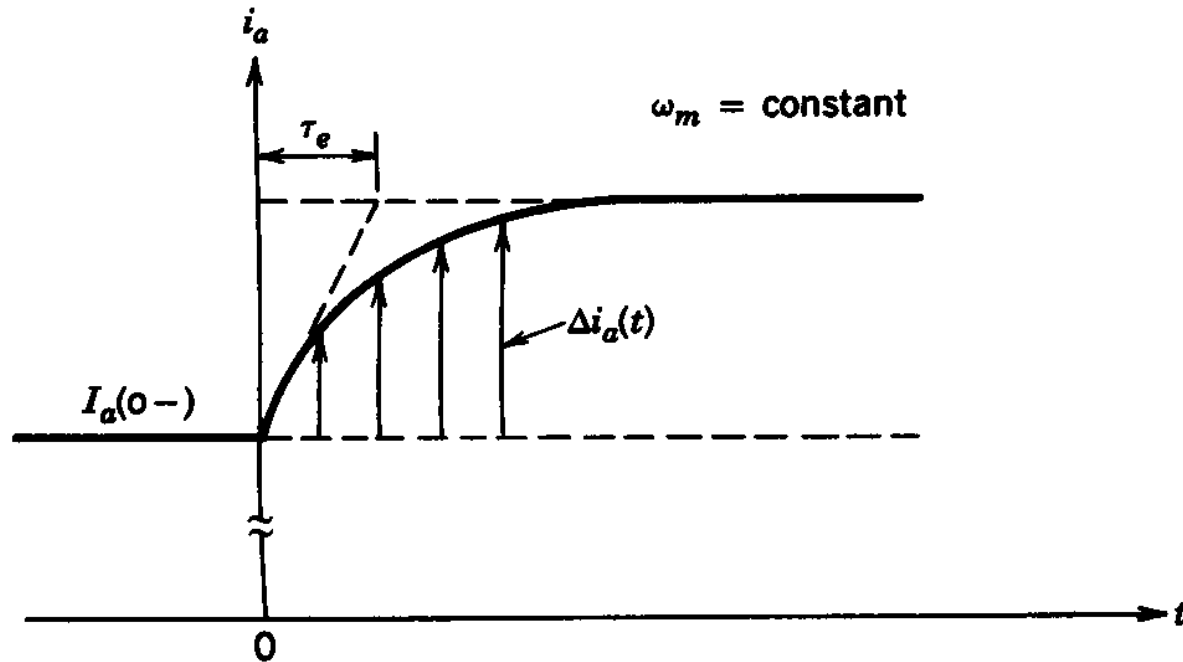

**Figure 13-8** Electrical time constant  $\tau_e$ ; speed  $\omega_m$  is assumed to be constant.

- The speed is assumed constant


# Mechanical Time-Constant of the DC Machine

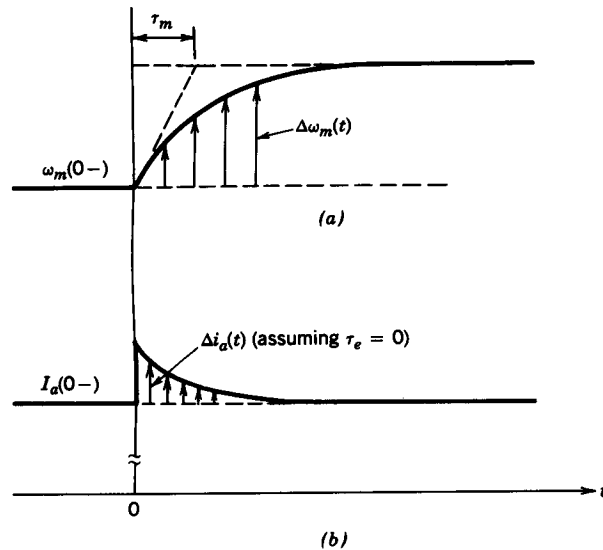

**Figure 13-9**  
Mechanical time constant  $\tau_m$ ; load torque is assumed to be constant.

- The load-torque is assumed constant


# DC-Motor Drive: Four-Quadrant Capability

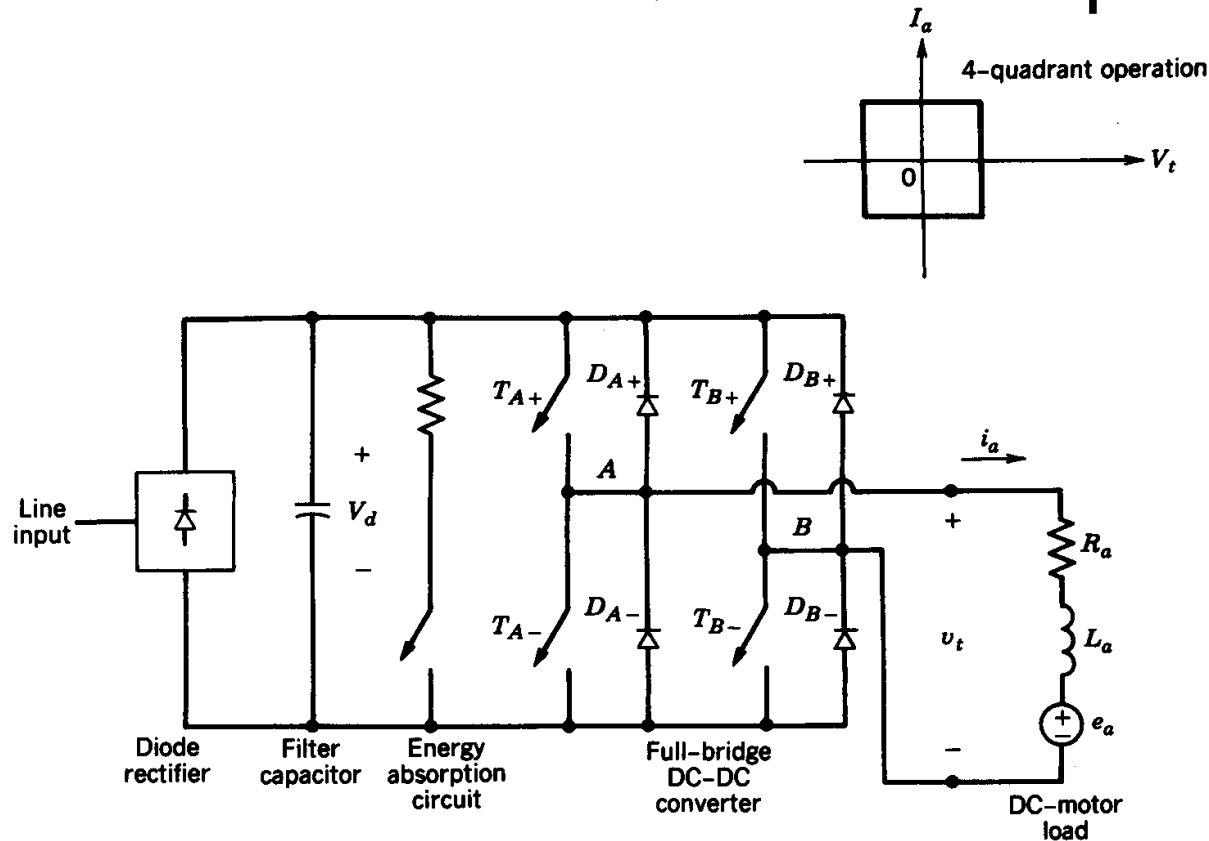

**Figure 13-10** A dc motor servo drive; four-quadrant operation.

- If a diode-rectifier is used, the energy recovered during regenerative braking is dissipated in a resistor

# Ripple in the Armature Current

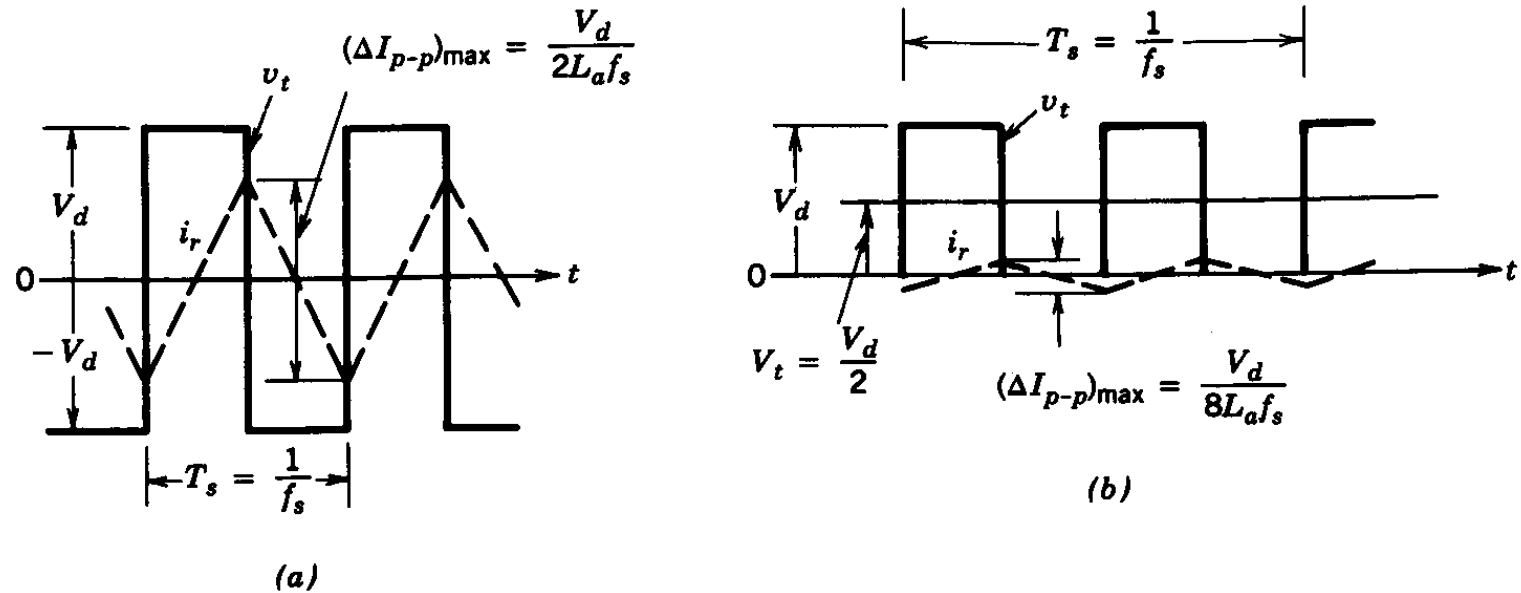

**Figure 13-11** Ripple  $i_r$  in the armature current: (a) PWM bipolar voltage switching,  $V_t = 0$ ; (b) PWM unipolar voltage switching,  $V_t = \frac{1}{2}V_d$ .

- Bi-polar and uni-polar voltage switchings

# Control of Servo Drives


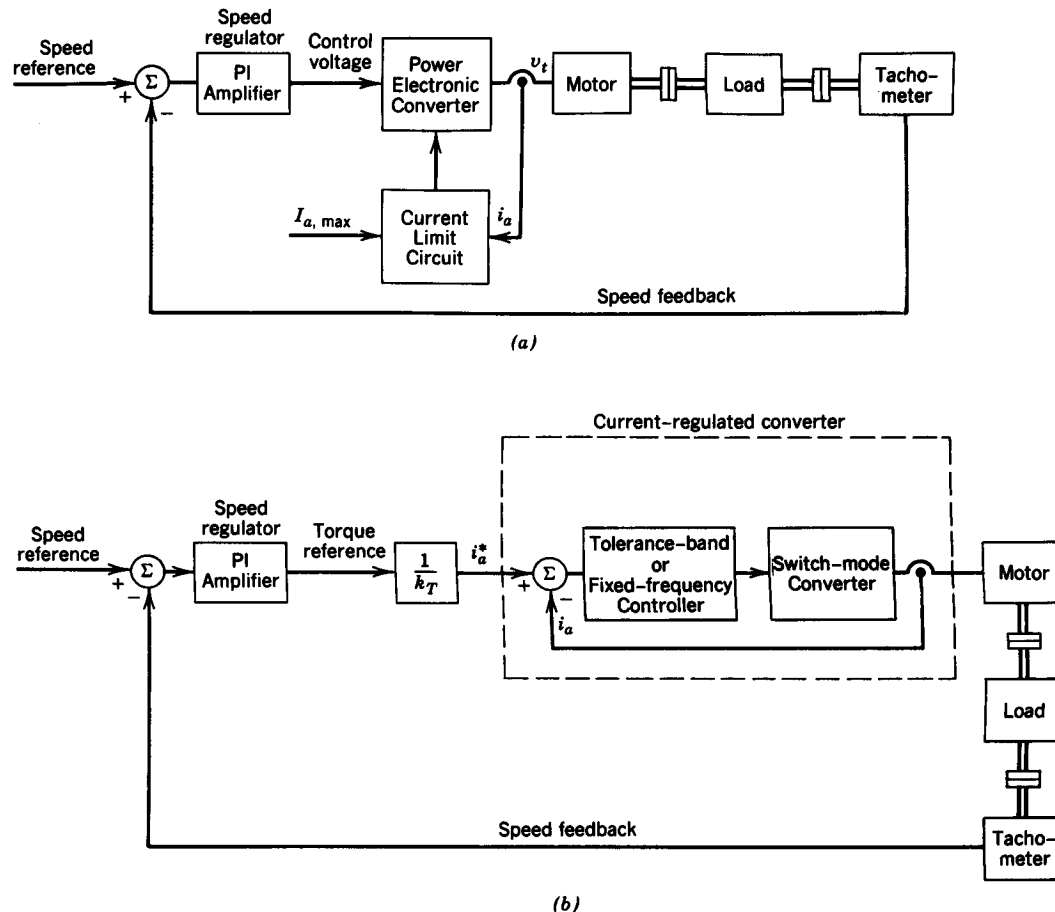


Figure 13-12 Control of servo drives: (a) no internal current-control loop; (b) internal current-control loop.

- A concise coverage is presented in “Electric Drives: An Integrative Approach” by N. Mohan ([www.MNPERE.com](http://www.MNPERE.com))

# Effect of Blanking Time

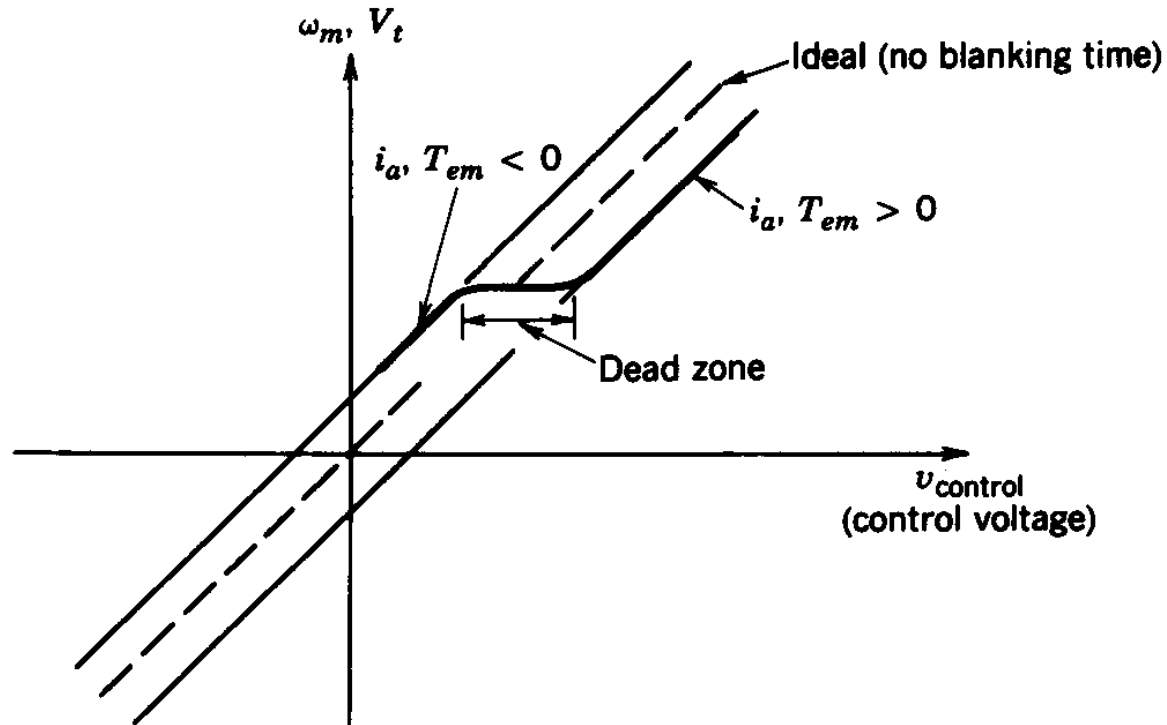

**Figure 13-13** Effect of blanking time.

- Non-linearity is introduced

# Converters for Limited Operational Capabilities

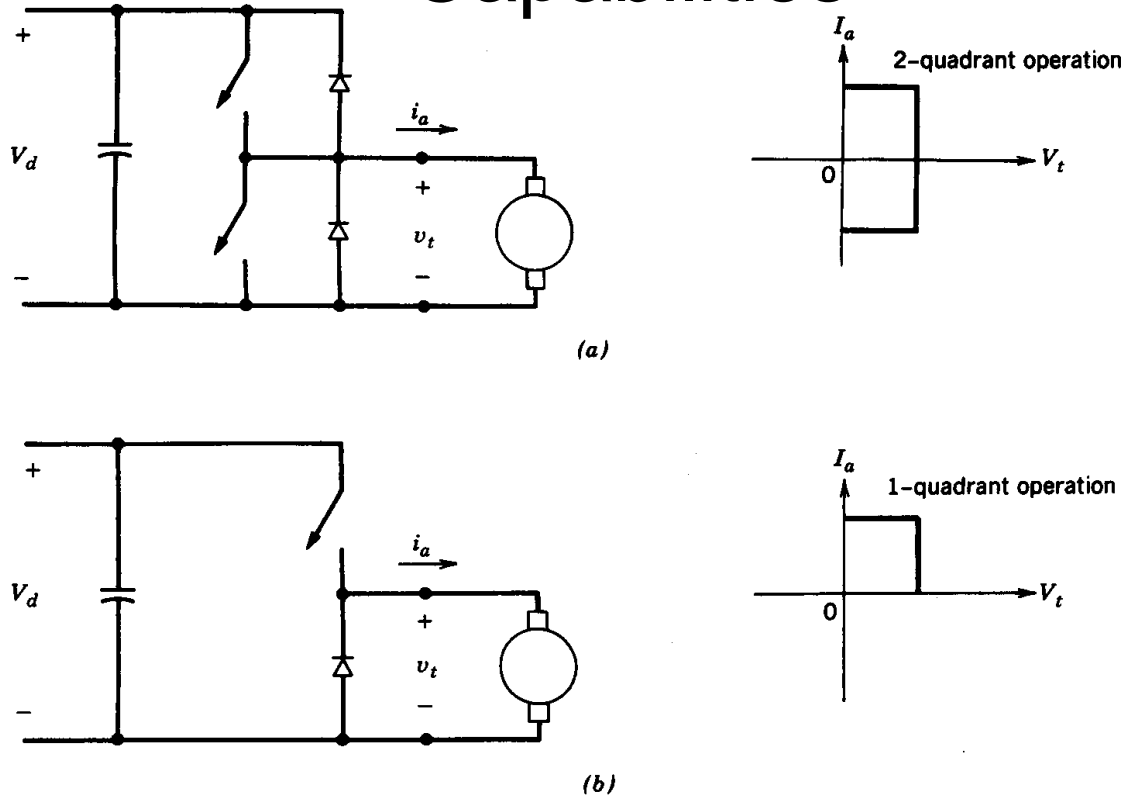
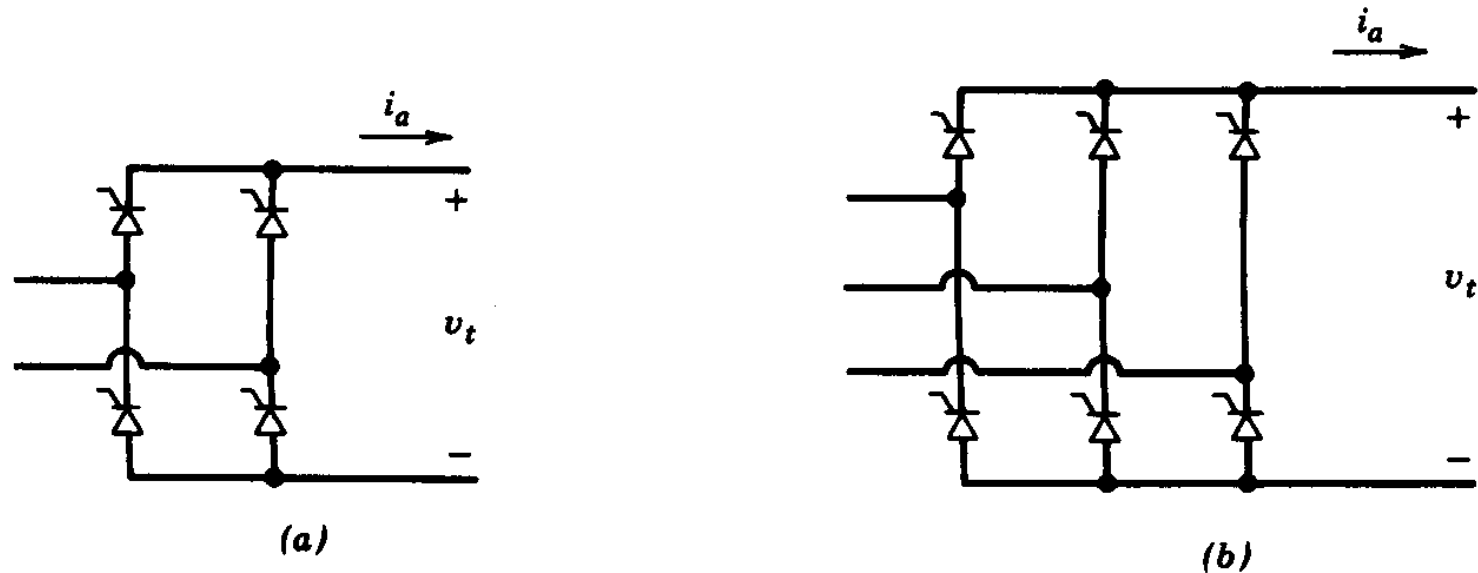


Figure 13-14 (a) Two-quadrant operation; (b) single-quadrant operation.

- Two switches for 2-quadrant operation and only one switch for 1-quadrant operation

# Line-Controlled Converters for DC Drives

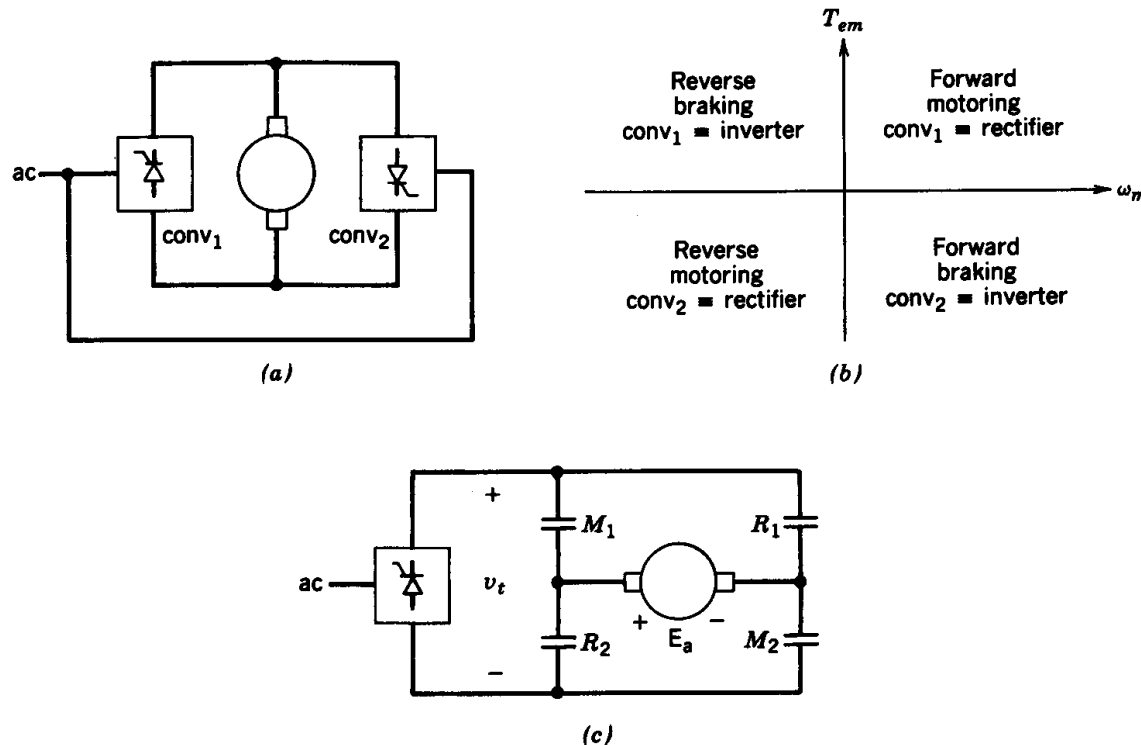


**Figure 13-15** Line-frequency-controlled converters for dc motor drives: (a) single-phase input; (b) three-phase input.

- Large low-frequency ripple in the dc output of converters




# Four Quadrant Operation using Line Converters



**Figure 13-16** Line-frequency-controlled converters for four-quadrant operation:  
 (a) back-to-back converters for four-quadrant operation (without circulating current);  
 (b) converter operation modes; (c) contactors for four-quadrant operation.

- Two options to achieve 4-quadrant operation

# Effect of Discontinuous Current Conduction

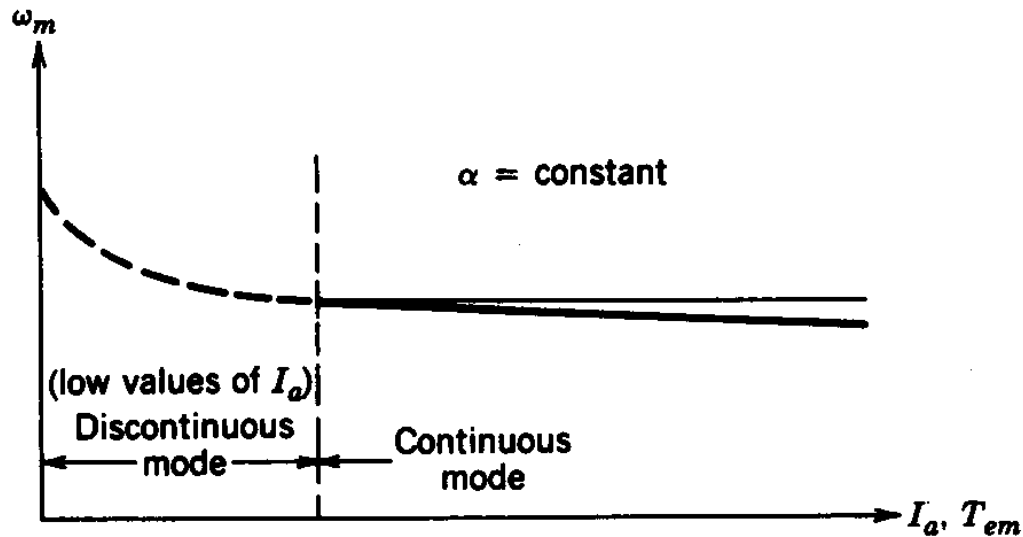

**Figure 13-17** Effect of discontinuous  $i_a$  on  $\omega_m$ .

- Speed goes up unless it is controlled

# Open-Loop Speed Control


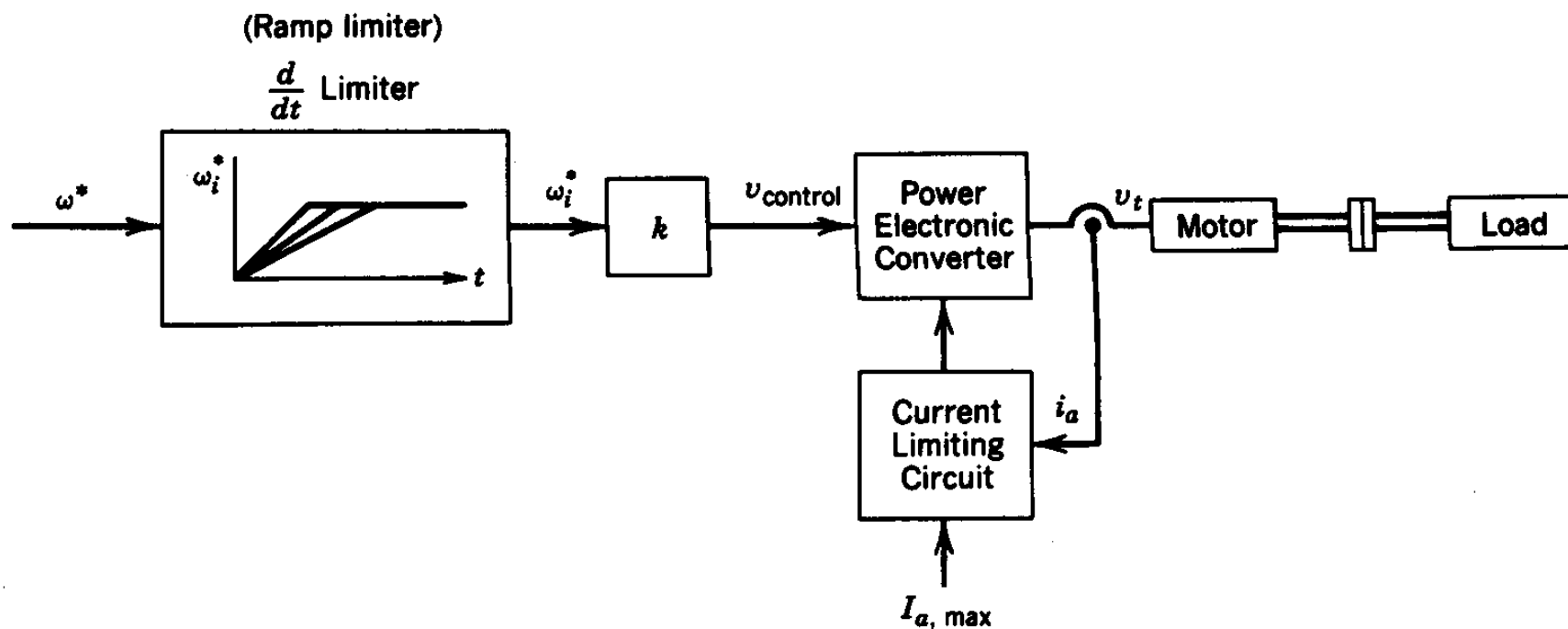


Figure 13-18 Open-loop speed control.

- Adequate for general-purpose applications

# DC Drive Characteristics and Capabilities

- Line current in switch-mode and line-converter drives

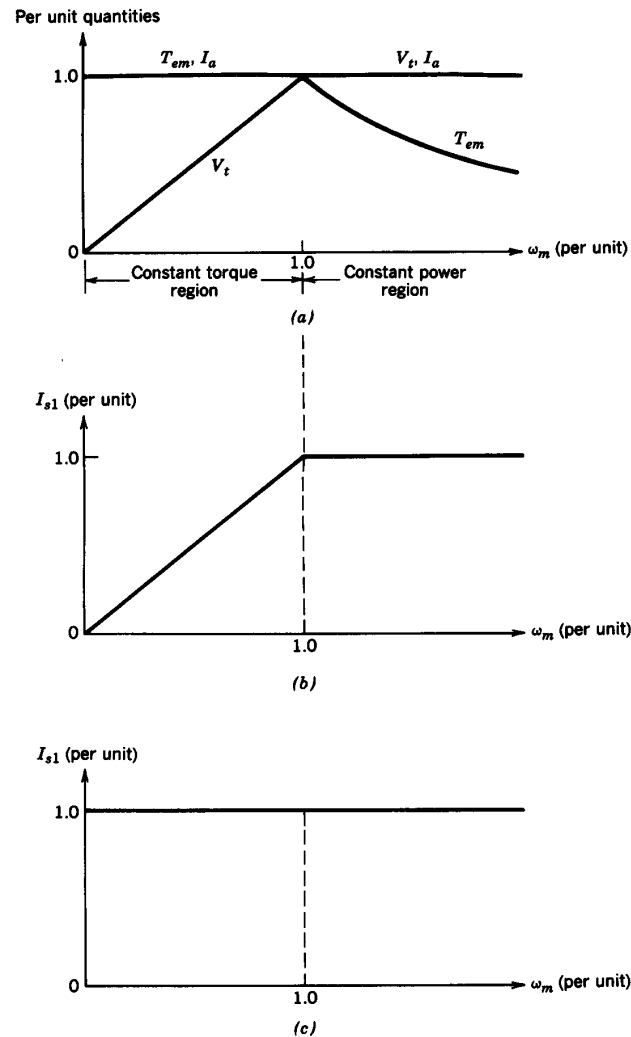

**Figure 13-19** Line current in adjustable-speed dc drives: (a) drive capability; (b) switch-mode converter drive; (c) line-frequency thyristor converter drive.