## Chapter 15

## Synchronous Motor Drives

#### **Chapter 15 Synchronous Motor Drives** 435 15-1 Introduction 435 15-2 Basic Principles of Synchronous Motor Operation 435 15-3 Synchronous Servomotor Drives with Sinusoidal Waveforms 439 15-4 Synchronous Servomotor Drives with Trapezoidal Waveforms 440 15-5 Load-Commutated Inverter Drives 442 15-6 Cycloconverters Summary 445 **Problems** 446 447 References

A large variety of applications – higher efficiency

### Rotor Structure


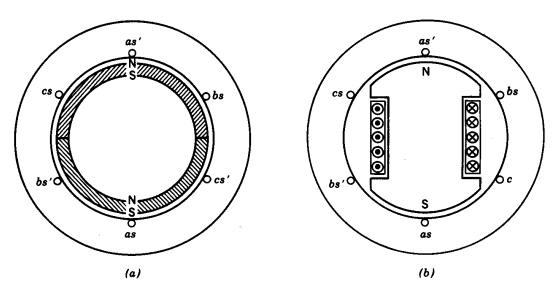


Figure 15-1 Structure of synchronous motors: (a) permanent-magnet rotor (two-pole); (b) salient-pole wound rotor (two-pole).

 Permanent-magnet or wound with a field winding

### Per-Phase Representation

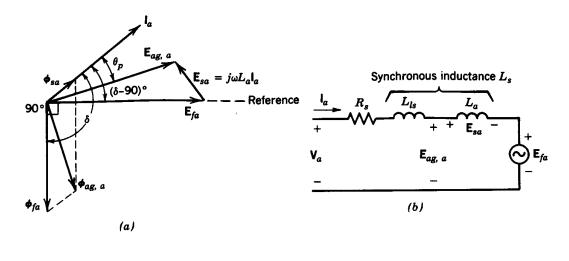


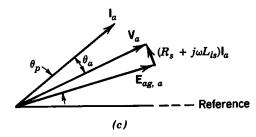


Figure 15-2 Per-phase representation: (a) phasor diagram; (b) equivalent circuit; (c) terminal voltage.

#### In sinusoidal steady state

# Phasor Diagram

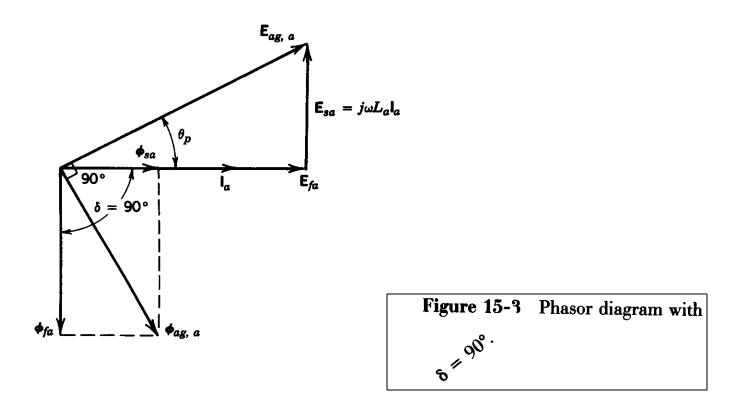

Optimum operation

#### **Rotor Position**

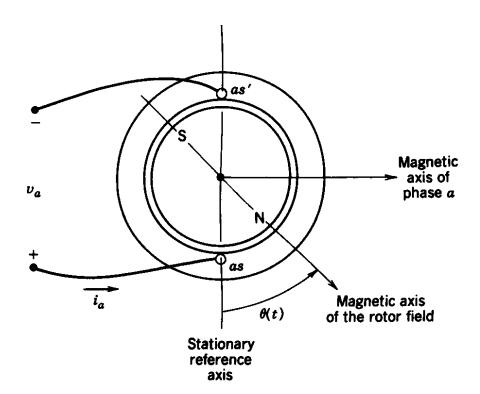


Figure 15-4 Measured rotor position  $\theta$  at time t.

Needs closed-loop operation knowing the rotor position

## Synchronous Motor Drive


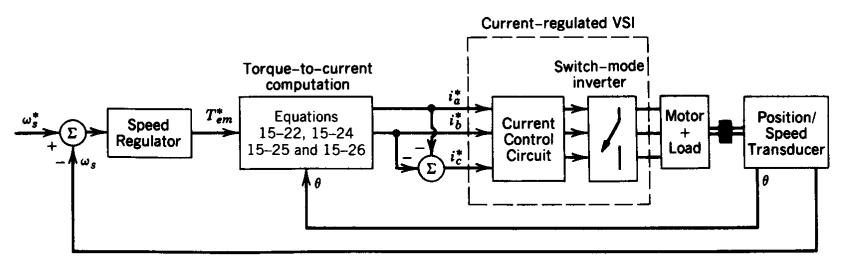


Figure 15-5 Synchronous motor servo drive.

Controller based on steady state operation


# Trapezoidal Waveform Synchronous Motor

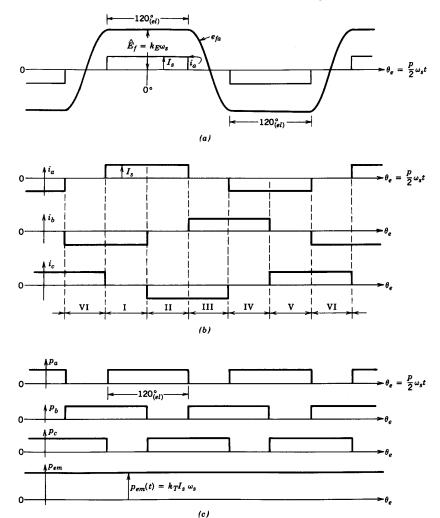

 ${\bf Figure~15-6} \quad {\bf Trapezoidal\text{-}wave form~synchronous~motor~drive}.$ 

used in applications where speed of response not critical

### Load-Commutated Inverter (LCI) Drive

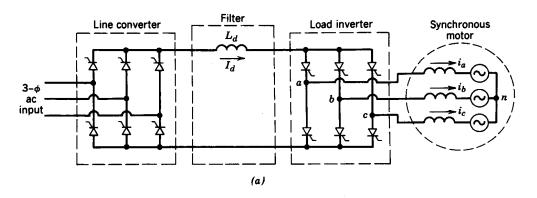

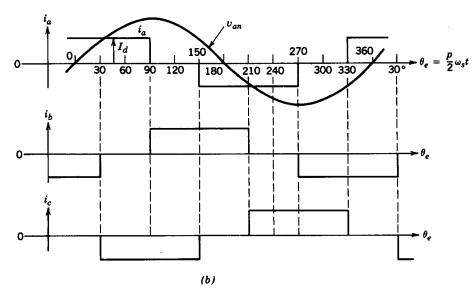


Figure 15-7 An LCI drive: (a) circuit; (b) idealized waveforms.

#### Used in very large power ratings

### LCI Drive Controller


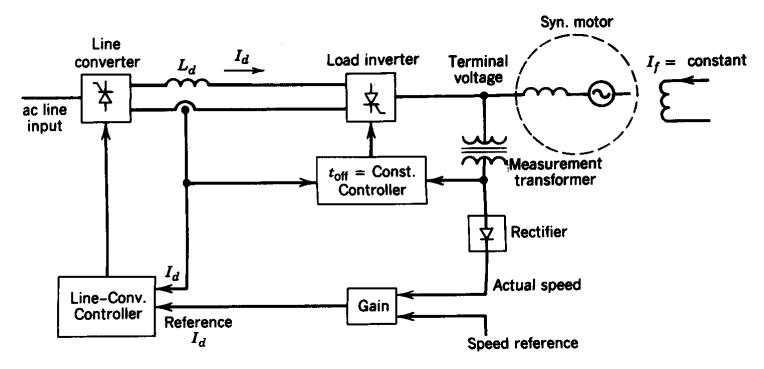


Figure 15-8 An LCI drive controller.

Line converter controls the dc-link current

### Three-Phase Cycloconverter

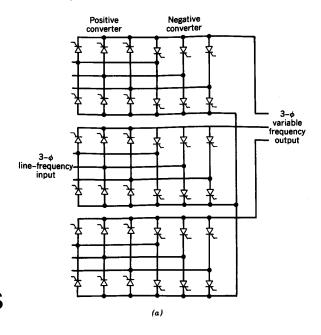

 Low-frequency ac output is synthesized

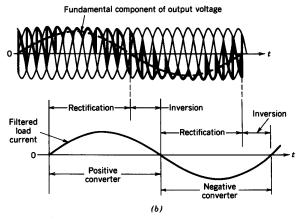


Figure 15-9 Three-phase cycloconverter.