

Lecture Notes


Gate Turn-off Thyristors (GTOS)

OUTLINE


- GTO construction and I-V characteristics.
- Physical operation of GTOs.
- Switching behavior of GTOS

GTO (Gate Turn-off Thyristor) Construction

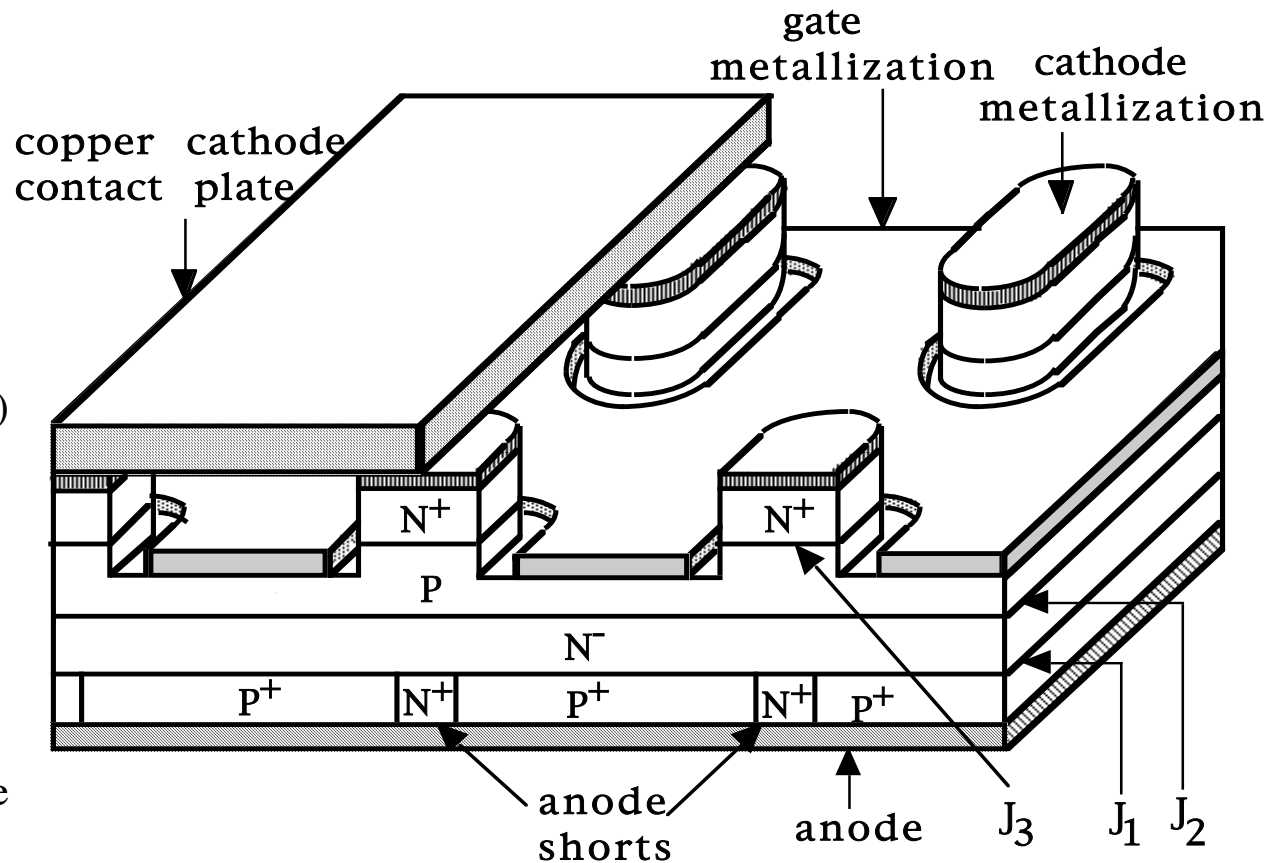
- Unique features of the GTO.
 - Highly interdigitated gate-cathode structure (faster switching)
 - Etched cathode islands (simplify electrical contacts)
 - Anode shorts (speed up turn-off)
- GTO has no reverse blocking capability because of anode shorts
- Otherwise i-v characteristic the same as for standard SCR



GTO circuit symbol

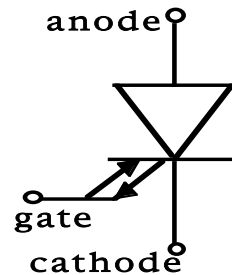


GTO Turn-off Gain

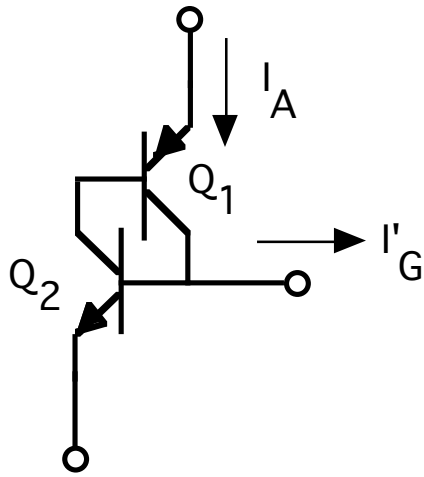

- Large turn-off gain requires $\beta_2 \approx 1, \beta_1 \ll 1$
- Make β_1 small by
 1. Wide n_1 region (base of Q_1) - also needed for large blocking voltage
 2. Short lifetime in n_1 region to remove excess carriers rapidly so Q_1 can turn off
- Short lifetime causes higher on-state losses
- Anode shorts helps resolve lifetime dilemma
 1. Reduce lifetime only moderately to keep on-state losses reasonable
 2. N^+ anode regions provide a sink for excess holes - reduces turn-off time
- Make $\beta_2 \approx$ unity by making p_2 layer relatively thin and doping in n_2 region heavily (same basic steps used in making beta large in BJTs).
- Use highly interdigitated gate-cathode geometry to minimize cathode current crowding and di/dt limitations.

- Turn off GTO by pulling one or both of the BJTs out of saturation and into active region.
- Force Q_2 active by using negative base current I_G' to make $I_{B2} < \frac{I_{C2}}{\beta_2}$
- $I_{B2} = \beta_1 I_A - I_G' \quad ; \quad I_{C2} = (1 - \beta_1) I_A$
- $\beta_1 I_A - I_G' < \frac{(1 - \beta_1) \beta_A \beta_1}{\beta_2} = \frac{(1 - \beta_1) (1 - \beta_2) \beta_A \beta_1}{\beta_2}$
- $I_G' < \frac{I_A \beta_1}{\beta_{off}} \quad ; \quad \beta_{off} = \frac{\beta_2}{(1 - \beta_1) \beta_2} = \text{turn-off gain}$


Maximum Controllable Anode Current

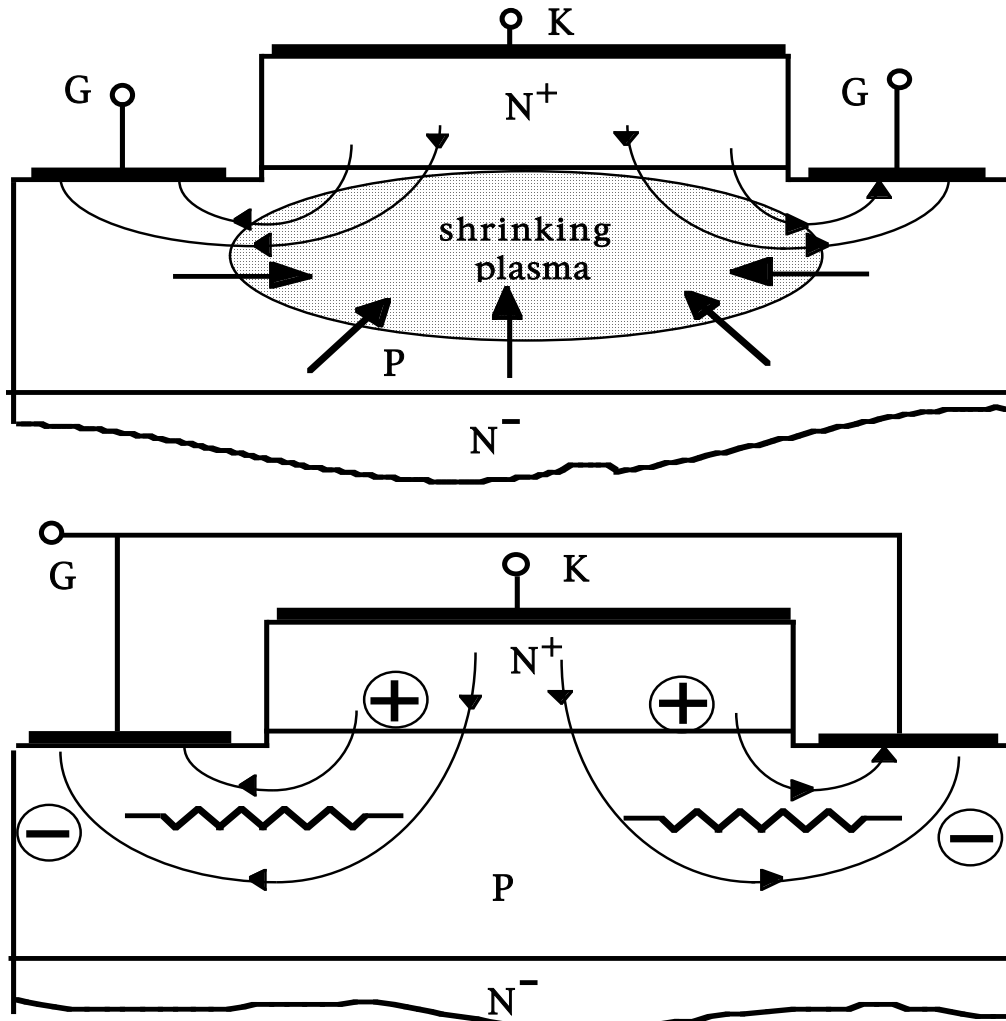


- Large negative gate current creates lateral voltage drops which must be kept smaller than breakdown voltage of J₃.
- If J₃ breaks down, it will happen at gate-cathode periphery and all gate current will flow there and not sweep out any excess carriers as required to turn-off GTO.
- Thus keep gate current less than I_{G,max} and so anode current restricted by $I_A < \frac{I_{G,max}}{\beta_{off}}$

GTO Step-down Converter

- GTO used in medium-to-high power applications where electrical stresses are large and where other solid state devices used with GTOs are slow e.g. free-wheeling diode D_F .
- GTO almost always used with turn-on and turn-off snubbers.
 1. Turn-on snubber to limit overcurrent from D_F reverse recovery.
 2. Turn-off snubber to limit rate-of-rise of voltage to avoid retriggering the GTO into the on-state.
- Hence should describe transient behavior of GTO in circuit with snubbers.

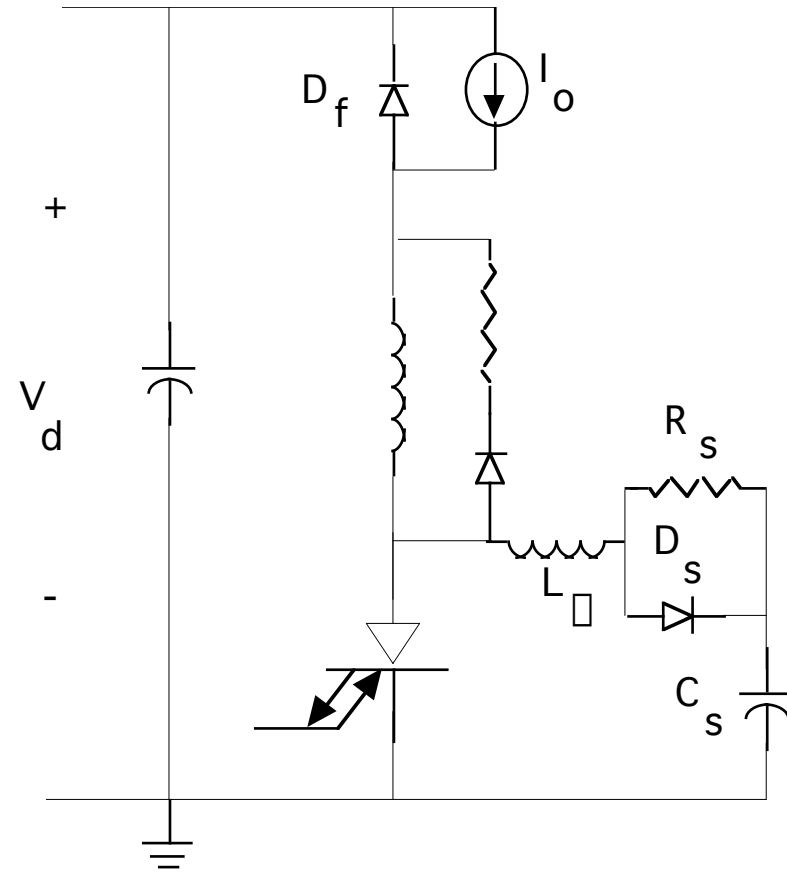


GTO Turn-on Waveforms

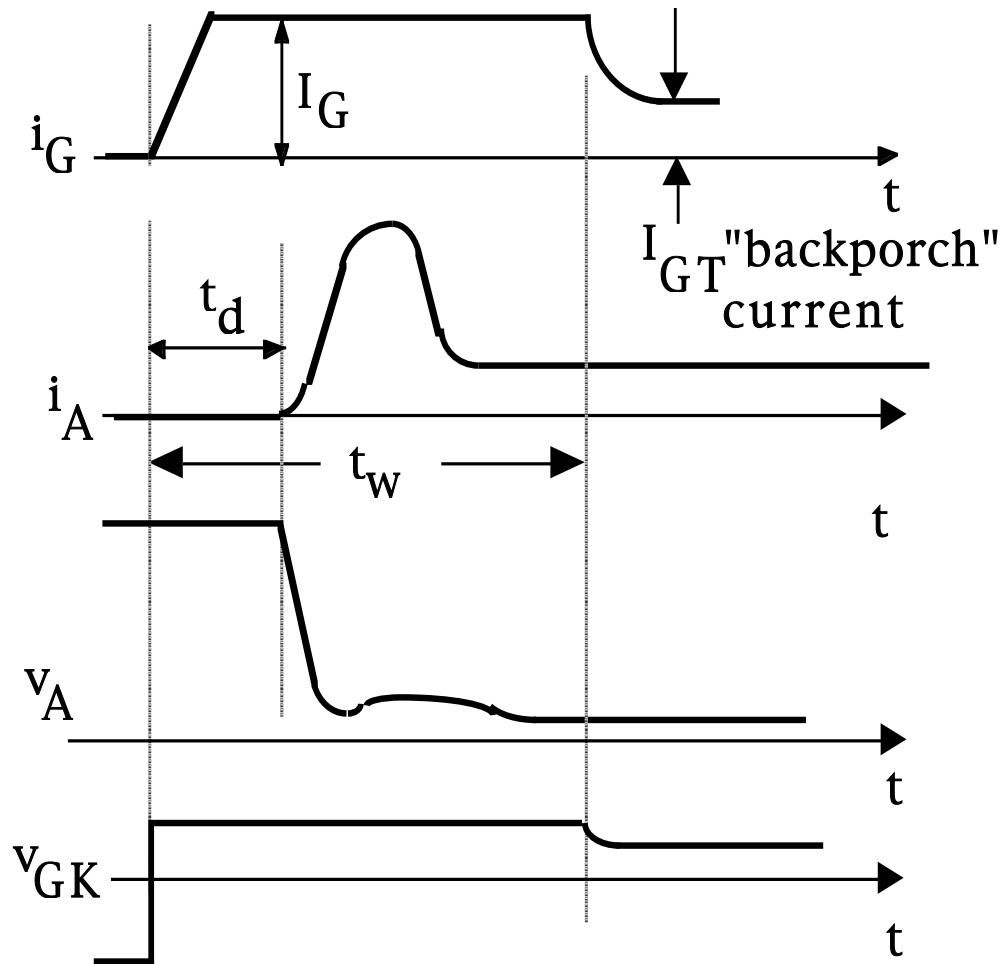

- GTO turn on essentially the same as for a standard thyristor
- Large I_{GM} and large rate-of-rise insure all cathode islands turn on together and have good current sharing.
- Backporch current I_{GT} needed to insure all cathode islands stay in conduction during entire on-time interval.
- Anode current overshoot caused by free-wheeling diode reverse recovery current.
- Anode-cathode voltage drops precipitously because of turn-on snubber

GTO Turn-off Waveforms

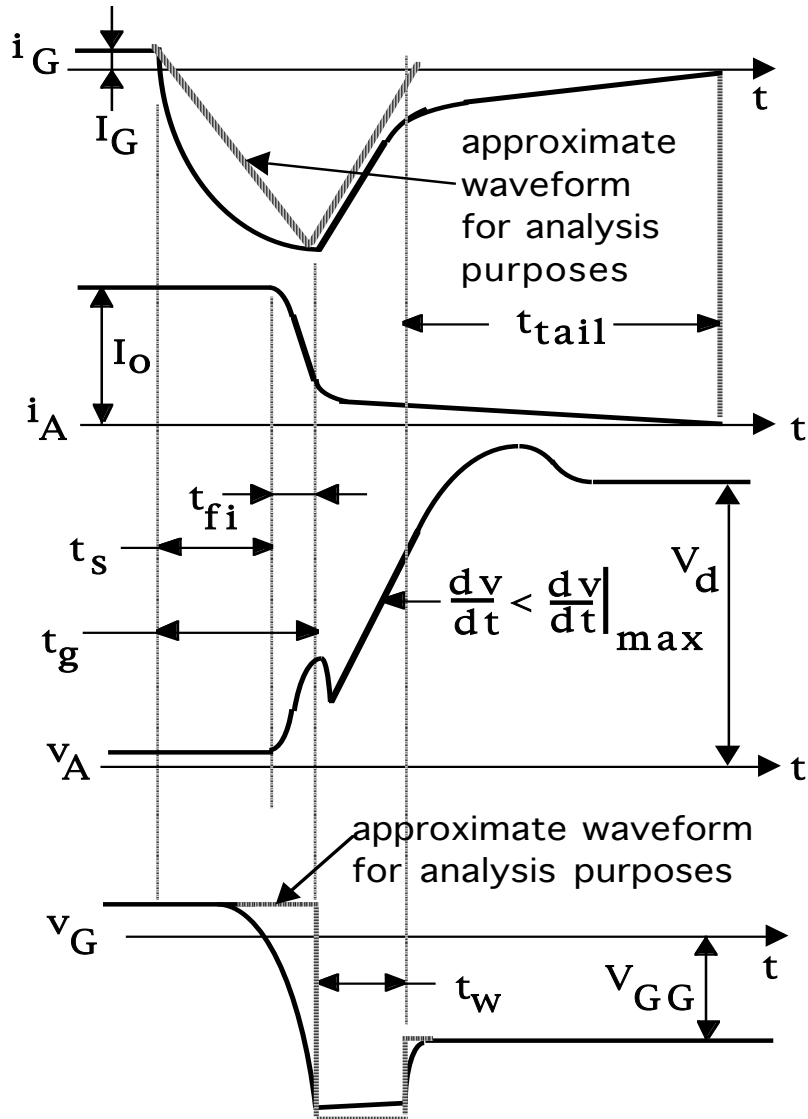

- t_s interval
Time required to remove sufficient stored charge to bring BJTs into active region and break latch condition
- t_{fi} interval
 1. Anode current falls rapidly as load current commutates to turn-off snubber capacitor
 2. Rapid rise in anode-cathode voltage due to stray inductance in turn-off snubber circuit
- t_{w2} interval
 1. Junction J_3 goes into avalanche breakdown because of inductance in trigger circuit. Permits negative gate current to continue flowing and sweeping out charge from p_2 layer.
 2. Reduction in gate current with time means rate of anode current commutation to snubber capacitor slows. Start of anode current tail.
- t_{tail} interval
 1. Junction J_3 blocking, so anode current = negative gate current. Long tailing time required to remove remaining stored charge.
 2. Anode-cathode voltage growth governed by turn-off snubber.
 3. Most power dissipation occurs during tailing time.