

Drive Circuits

Outline



- Drive circuit design considerations
- DC-coupled drive circuits
- Isolated drive circuits
- Protection measures in drive circuits
- Component/circuit layout considerations

Functionality of Gate/Base Drive Circuits

- Turn power switch from off-state to on-state
 - Minimize turn-on time through active region where power dissipation is large
 - Provide adequate drive power to keep power switch in on-state
- Turn power switch from on-state to off-state
 - Minimize turn-off time through active region where power dissipation is large
 - Provide bias to insure that power switch remains off
- Control power switch to protect it when overvoltages or overcurrents are sensed
- Signal processing circuits which generate the logic control signals not considered part of the drive circuit
 - Drive circuit amplifies control signals to levels required to drive power switch
 - Drive circuit has significant power capabilities compared to logic level signal processing circuits
- Provide electrical isolation when needed between power switch and logic level signal processing/control circuits


Drive Circuit Design Considerations

- Drive circuit topologies
 - Output signal polarity - unipolar or bipolar
 - AC or DC coupled
 - Connected in shunt or series with power switch
- Output current magnitude
 - Large I_{on} shortens turn-on time but lengthens turn-off delay time
 - Large I_{off} shortens turn-off time but lengthens turn-on delay time
- Provisions for power switch protection
 - Overcurrents
 - Blanking times for bridge circuit drives
- Waveshaping to improve switch performance
 - Controlled di_B/dt for BJT turn-off
 - Anti-saturation diodes for BJT drives
 - Speedup capacitors
 - Front-porch/backporch currents
- Component layout to minimize stray inductance and shielding from switching noise

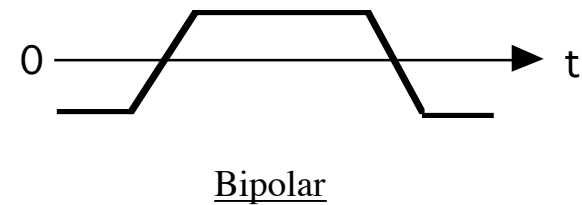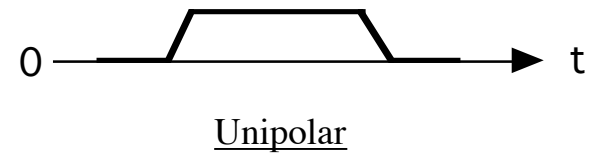


Unipolar DC-coupled Drive Circuit - BJT Example


- Circuit operation
 - $V_{\text{control}} > V_{\text{reference}}$ - BJT at comparator output on which puts Q_{pnp} and Q_{sw} on
 - $V_{\text{control}} < V_{\text{reference}}$ - BJT at comparator output off which turns Q_{pnp} off and thus Q_{sw} off
- Design procedure
 - $R_2 = \frac{V_{\text{BE,off}}}{I_{\text{B,off}}}$; $I_{\text{B,off}}$ based on desired turn-off time.
 - $I_{\text{pnp}} = I_{\text{B,on}} + \frac{V_{\text{BE,on}}}{R_2}$; $I_{\text{B,on}}$ value based on BJT beta and value of I_o .
 - $V_{\text{BB}} = V_{\text{CE,on}}(Q_{\text{pnp}}) + R_1 I_{\text{C,pnp}} + V_{\text{BE,on}}(Q_{\text{sw}})$
 - $V_{\text{BB}} = 8$ to 10 V ; compromise between larger values which minimize effects of V_{BE} variations and smaller values which minimize power dissipation in drive circuit

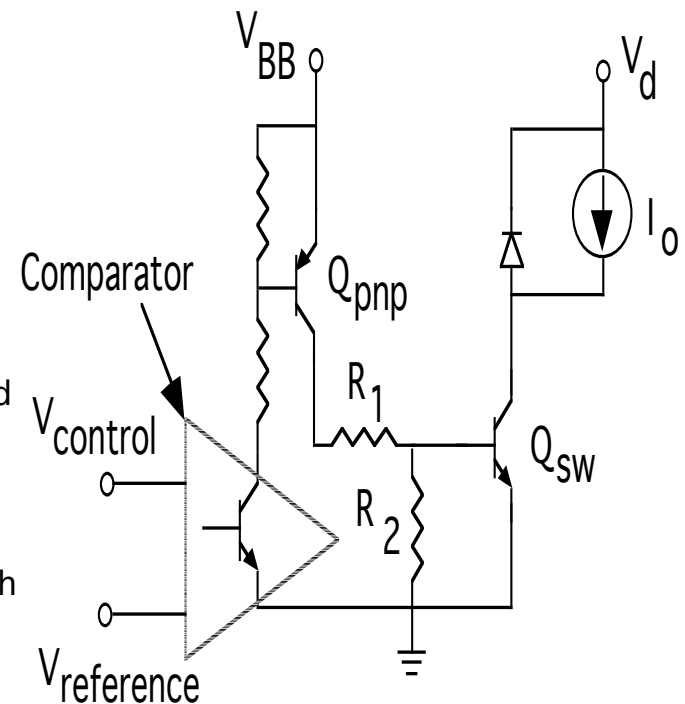

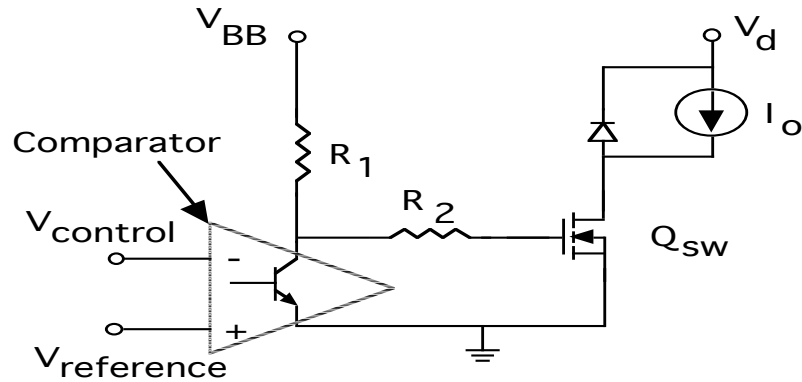
Unipolar DC-coupled Drive Circuits- MOSFET examples



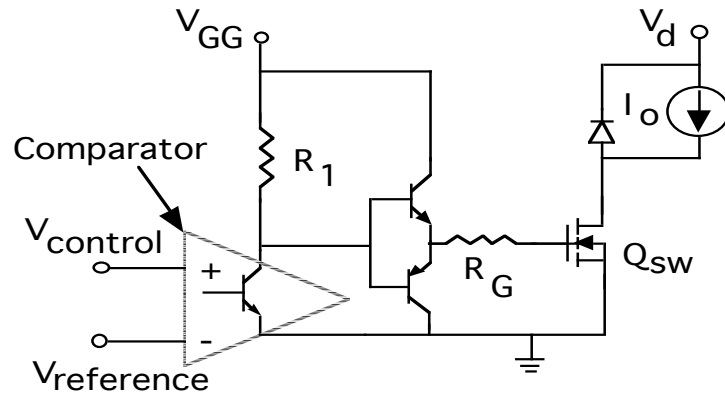
- $V_{\text{control}} > V_{\text{reference}}$
comparator output high and Q_{sw} on
- $V_{\text{control}} < V_{\text{reference}}$
comparator output low and Q_{sw} off



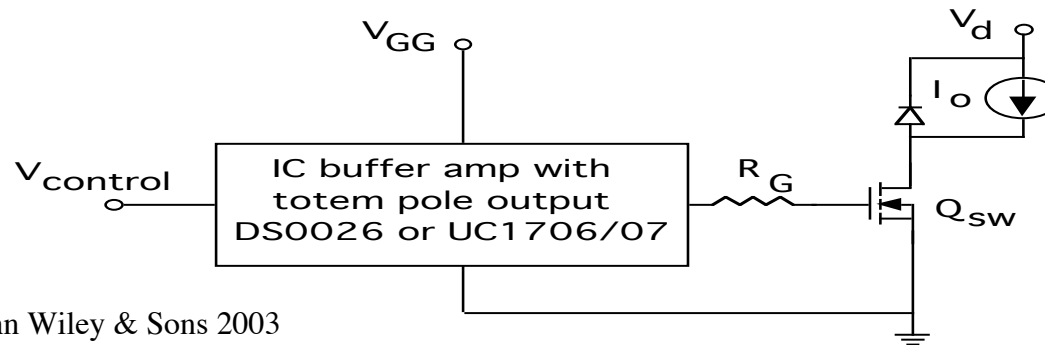- $V_{\text{control}} > V_{\text{reference}}$
comparator output high putting Q_{npn} on and thus Q_{sw} on
- $V_{\text{control}} < V_{\text{reference}}$
comparator output low putting Q_{pnp} on and thus Q_{sw} off




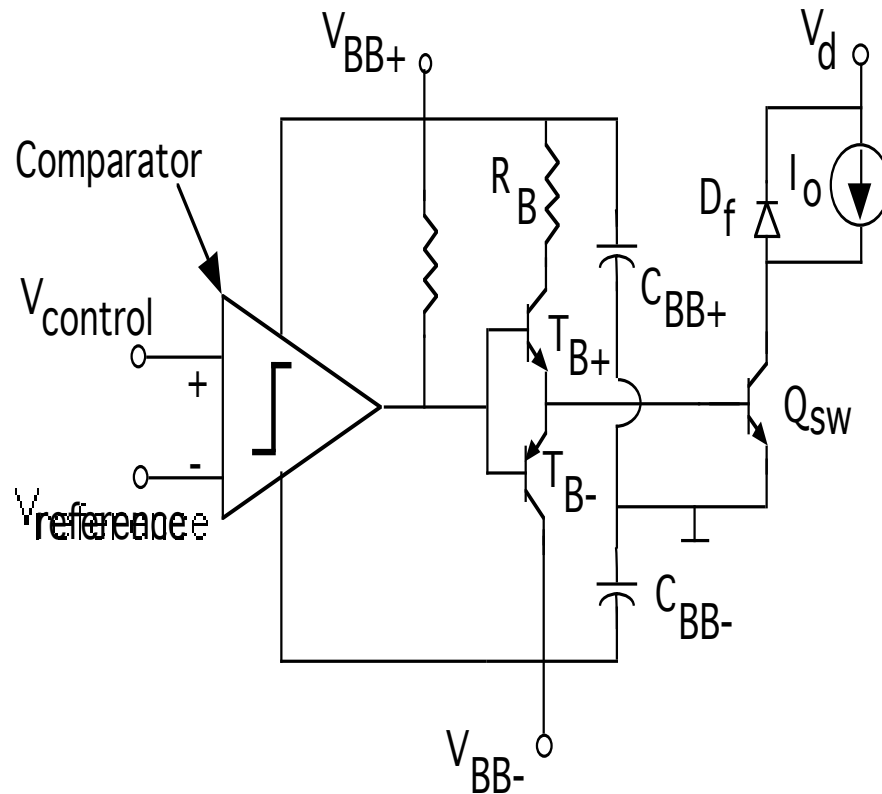Bipolar DC-coupled Drive Circuit- BJT Example




- $V_{control} < V_{reference}$ - comparator output low, T_{B-} on and Q_{sw} off.
- Large reverse base current flows to minimize turn-off time and base-emitter of Q_{sw} reversed biased to insure off-state.
- $V_{control} > V_{reference}$ - comparator output high, T_{B+} on and Q_{sw} on.
- Large forward base current to minimize turn-on time and to insure saturation of Q_{sw} for low on-state losses

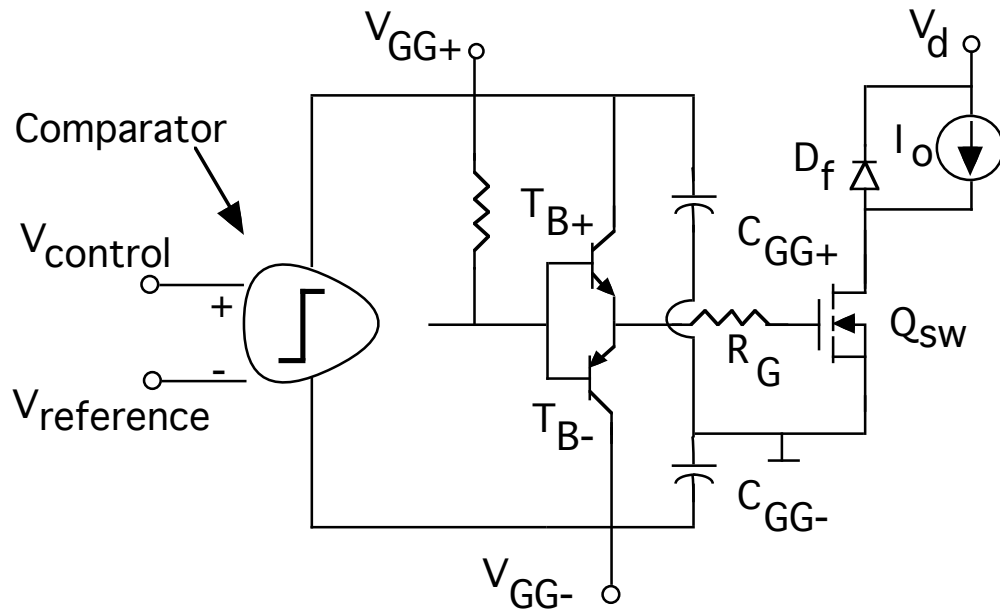Bipolar DC-coupled Drive Circuit- MOSFET Example



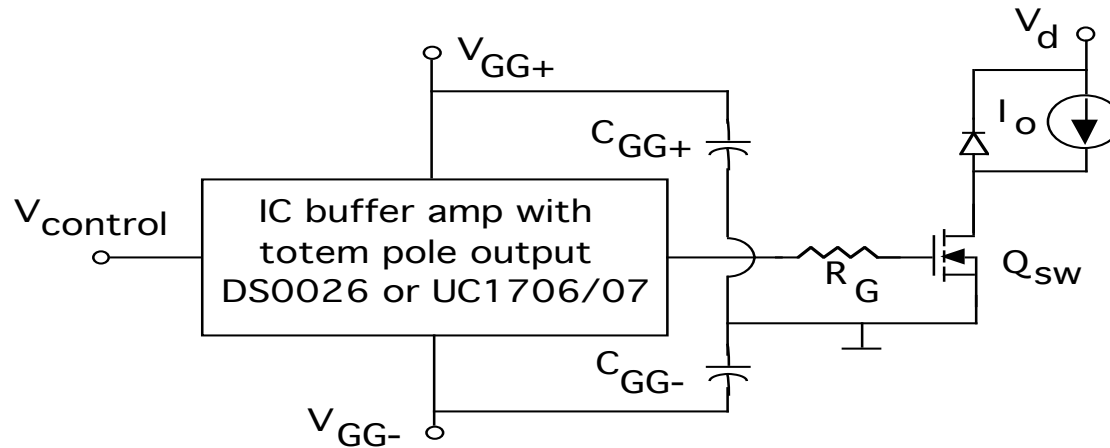
- Bipolar drive with substantial output current capability




- Simple bipolar drive circuit with moderate (1 amp) output current capability

Need for Electrical Isolation of Drive Circuits


- Negative half cycle of $v_s(t)$ - positive dc rail near safety ground potential. T_- emitter potential large and negative with respect to safety and logic ground
- Positive half cycle of $v_s(t)$ - negative dc rail near safety ground potential. T_+ emitter substantially positive with respect to safety ground if T_- is off
- Variation in emitter potentials with respect to safety and logic ground means that electrical isolation of emitters from logic ground is needed.

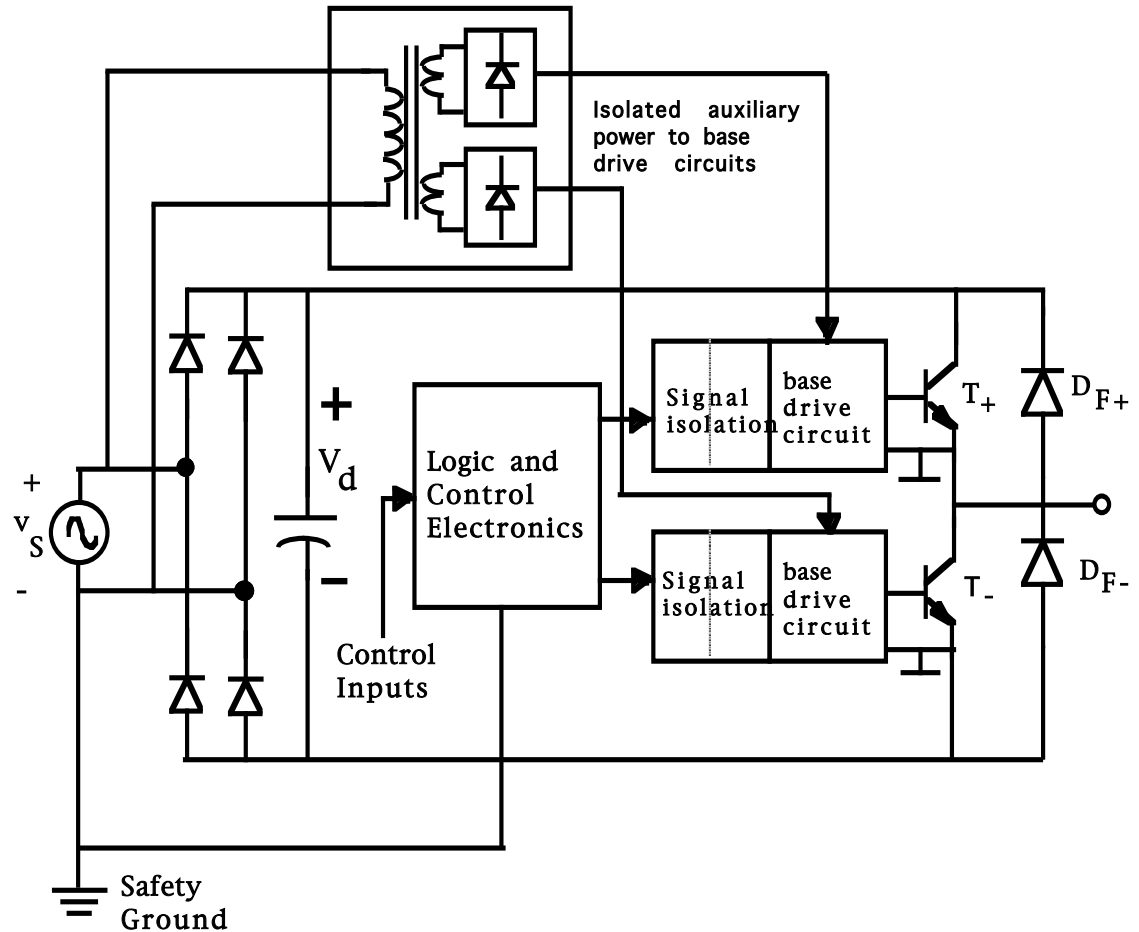


Methods of Control Signal Isolation

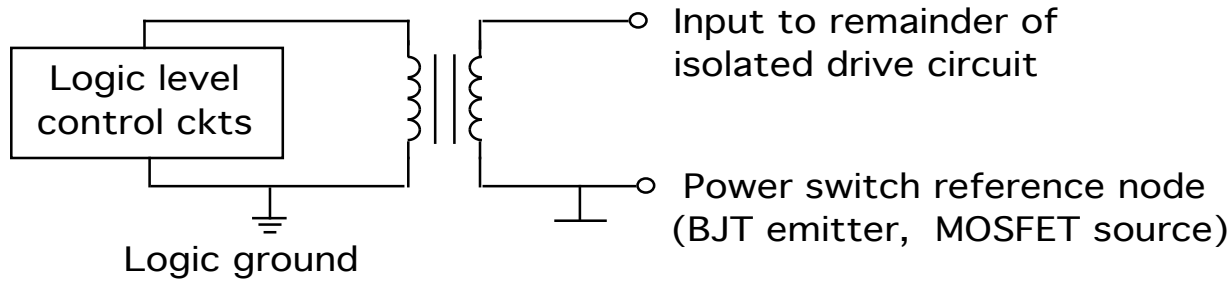

- Transformer isolation

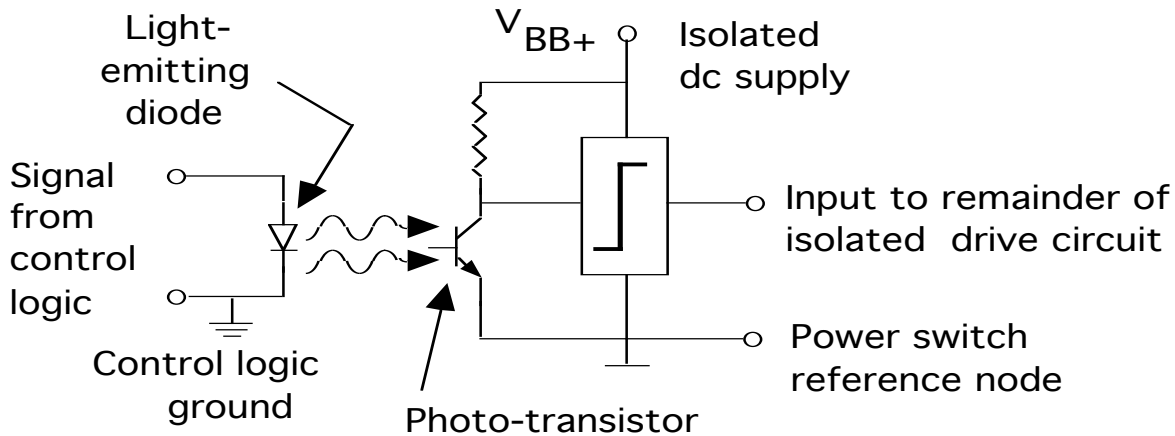


- Opto-coupler isolation


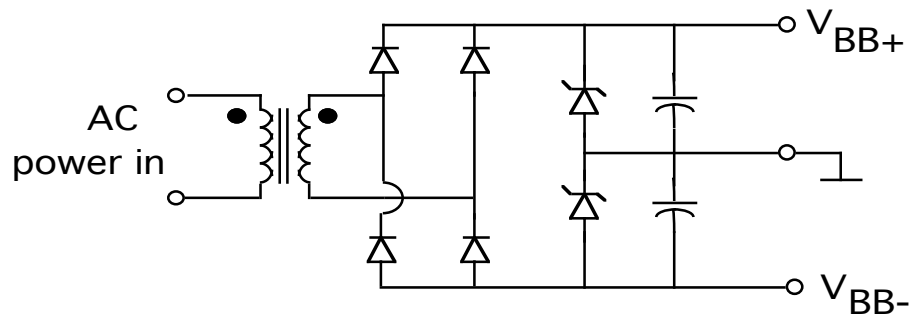


- Isolated dc power supplies for drive circuits



Opto-Coupler Isolated BJT Drive

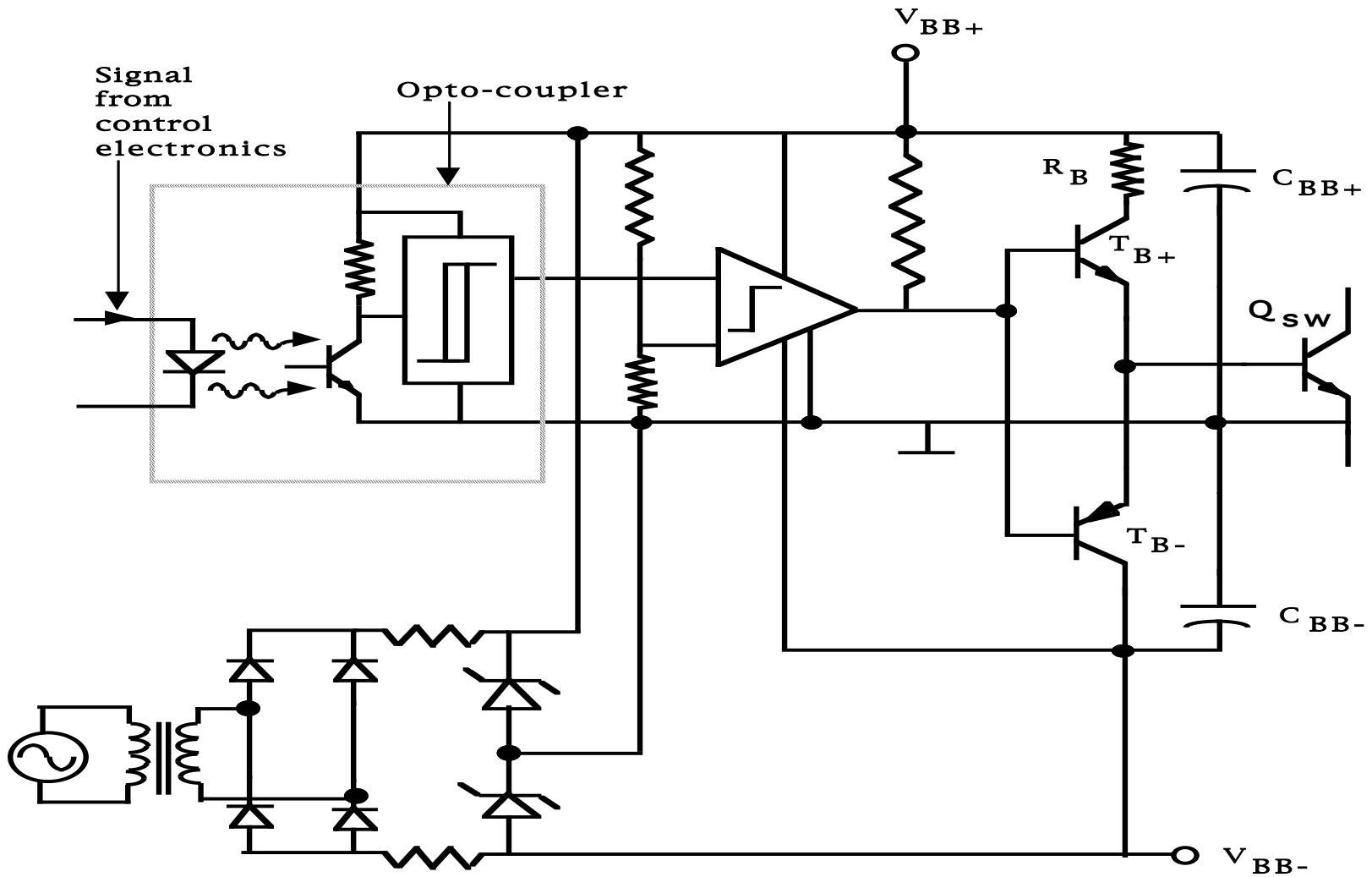


Transformer-coupled BJT Drive

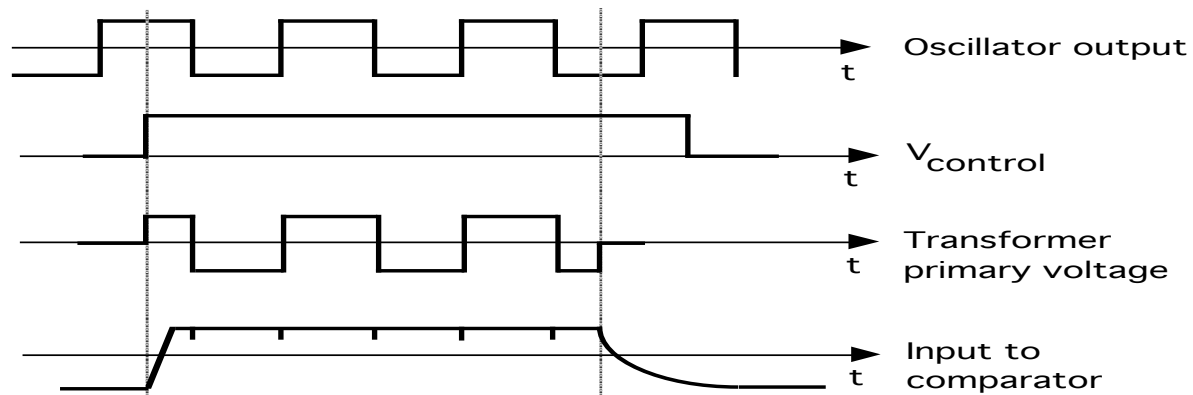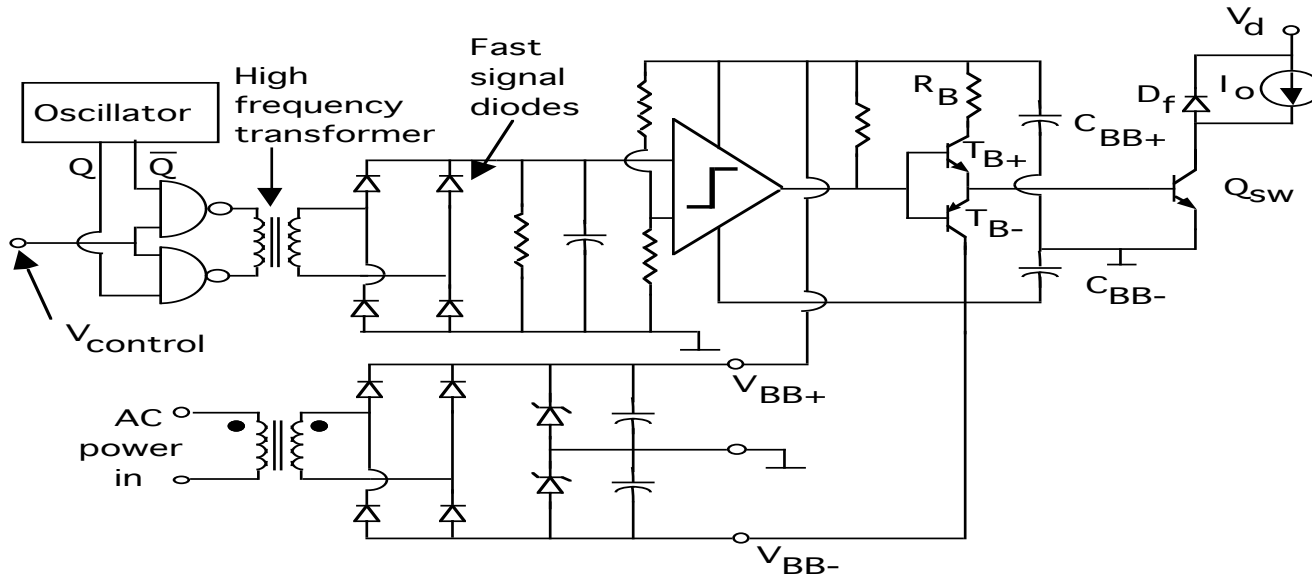

Opto-Coupler Isolated MOSFET Drives

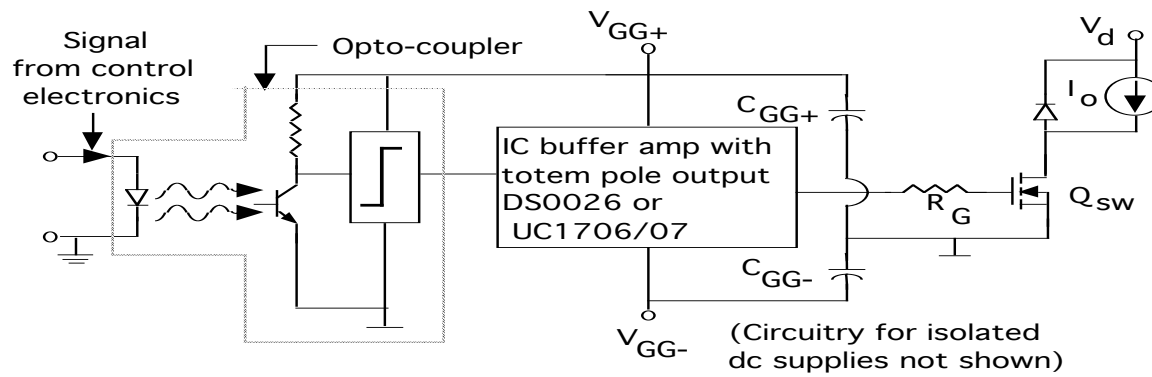
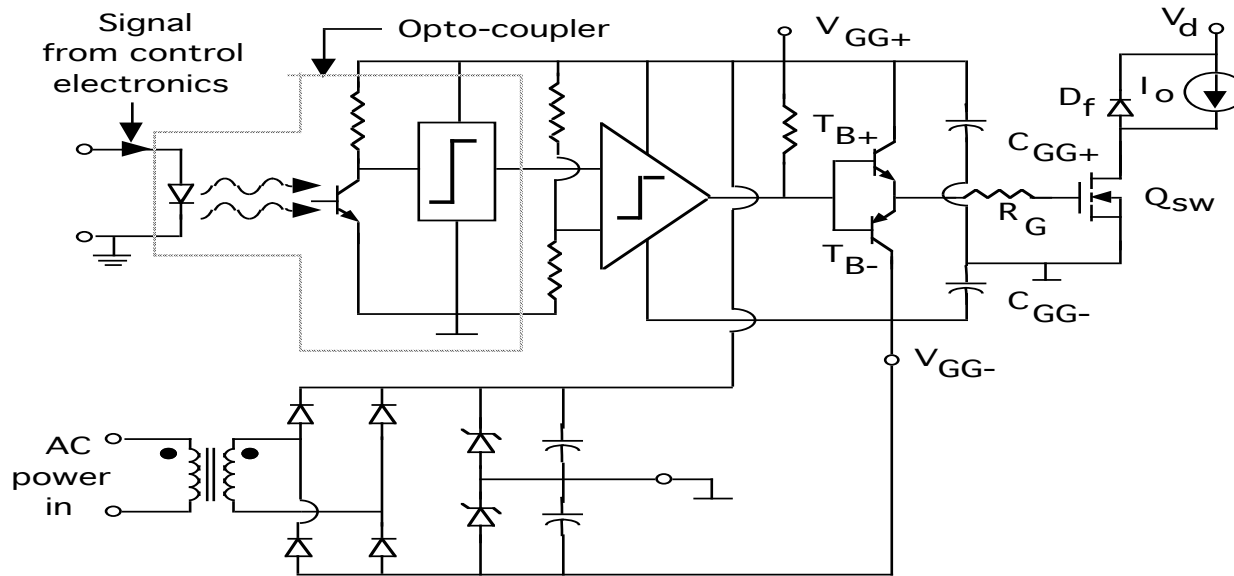


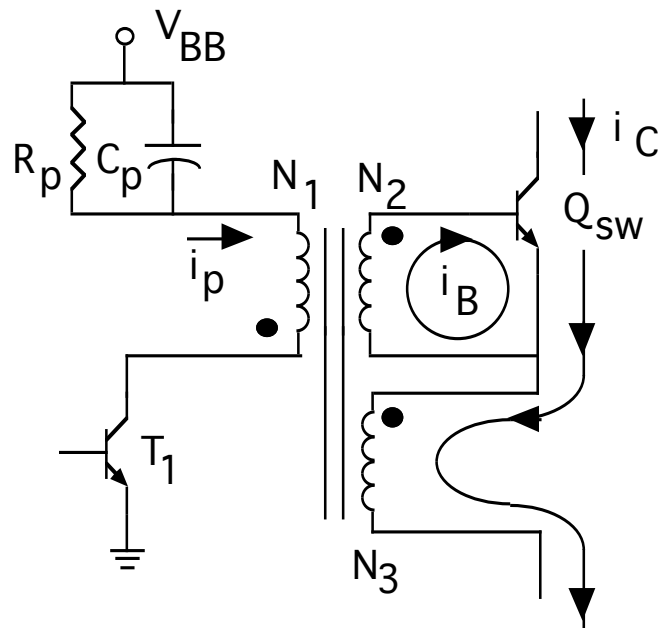Isolated Drives Without Auxiliary DC Supplies - Proportional Flyback BJT Example




- Regenerative circuit operation
 - T_1 on - current $i_p = V_{BB}/R_p$ and Q_{sw} off
 - T_1 turned off - stored energy in gapped transformer core induces positive base current i_B in Q_{sw} causing it to go active and collector current i_C begins to flow
 - Regenerative action of transformer connections supplies a base current $i_B = N_3 i_C / N_2$ which keeps Q_{sw} on even with $i_p = 0$
 - T_1 turned on - positive current i_p causes a base current $i_B = N_3 i_C / N_2 - N_1 i_p / N_2$ in Q_{sw}
 - Initially i_p quite large ($i_p(0^+) = \Delta i_{B1}(0^+)$) so Q_{sw} turned off
- Circuit design must insure turn-off i_B has adequate negative magnitude and duration
 - Best suited for high frequency operation - lower volt-second requirements on transformer.
 - Also best suited for limited variations in duty cycle

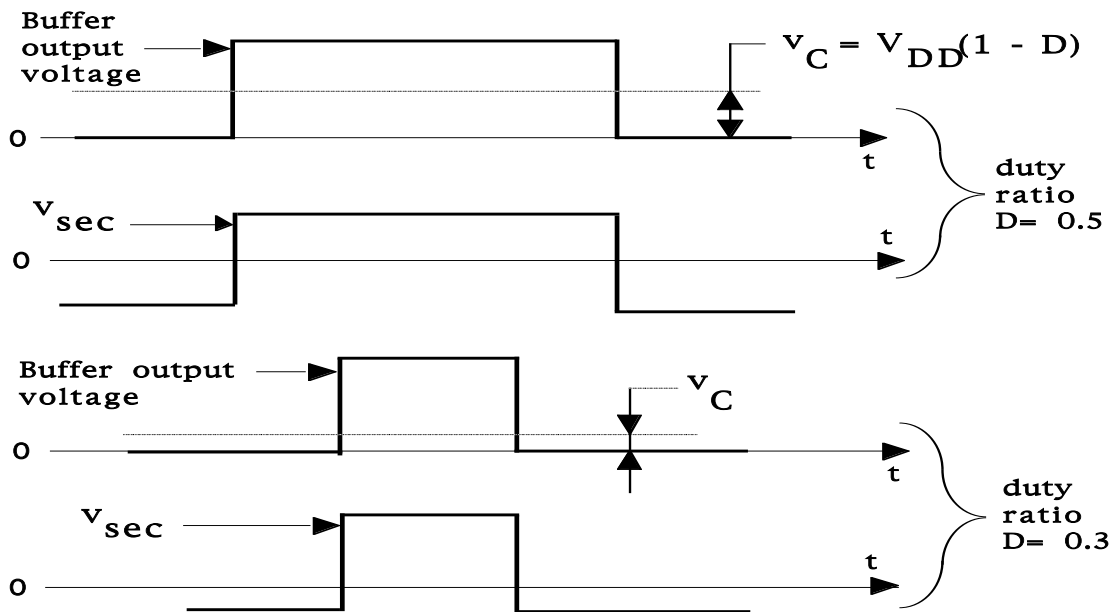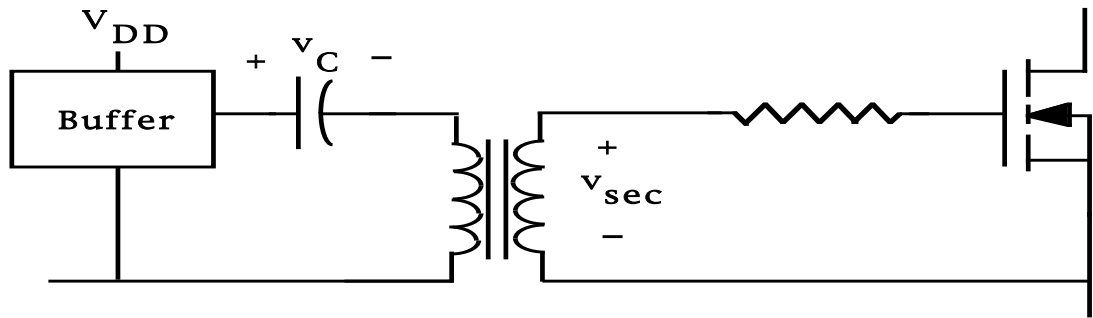Isolated Drives Without Auxiliary DC Supplies - MOSFET Example




Most suitable for applications where duty cycle D is 50% or less. Positive-going secondary voltage decreases as D increases.

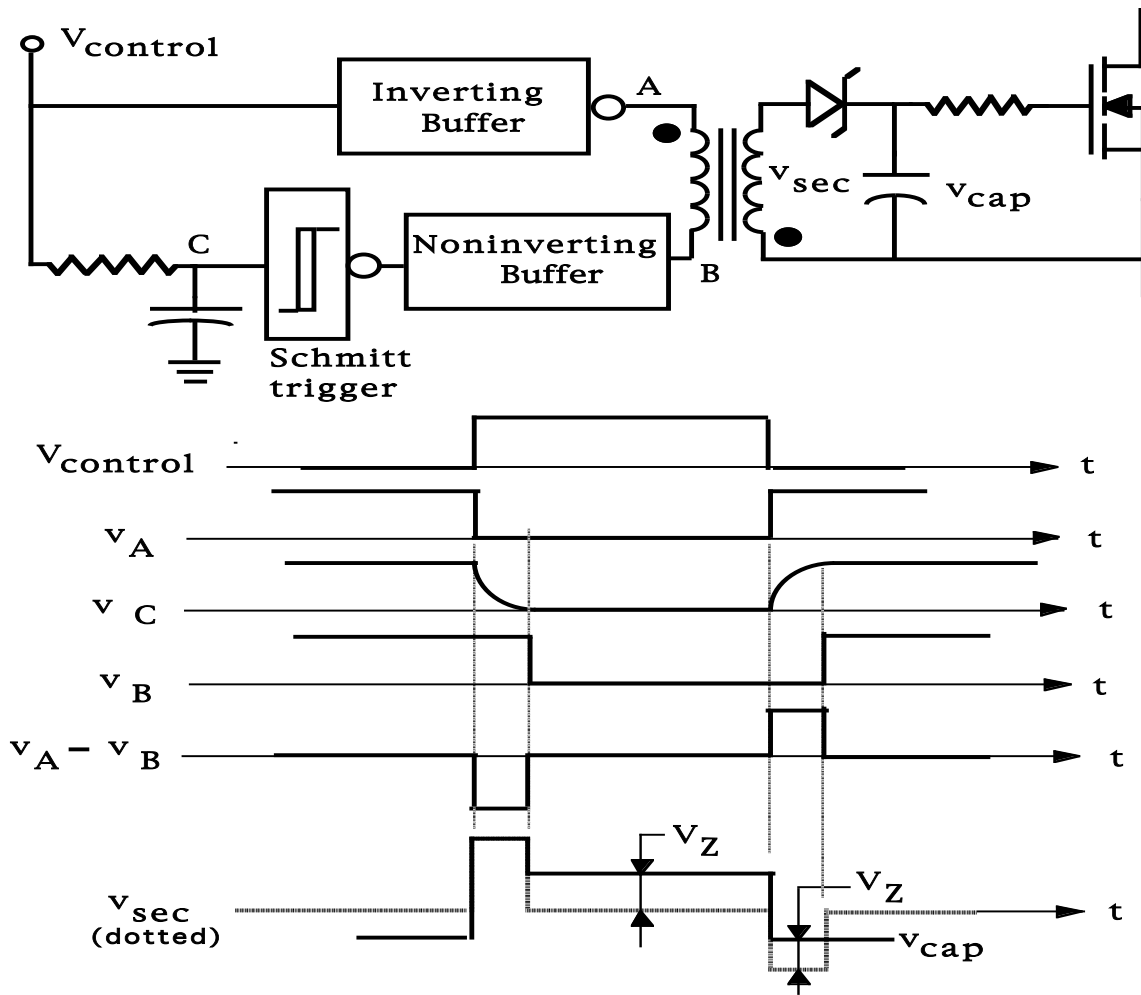Isolated Drive Without Auxiliary DC Supplies - MOSFET Example





Zener diode voltage V_Z must be less than negative pulse out of transformer secondary or pulse will not reach MOSFET gate to turn it off.

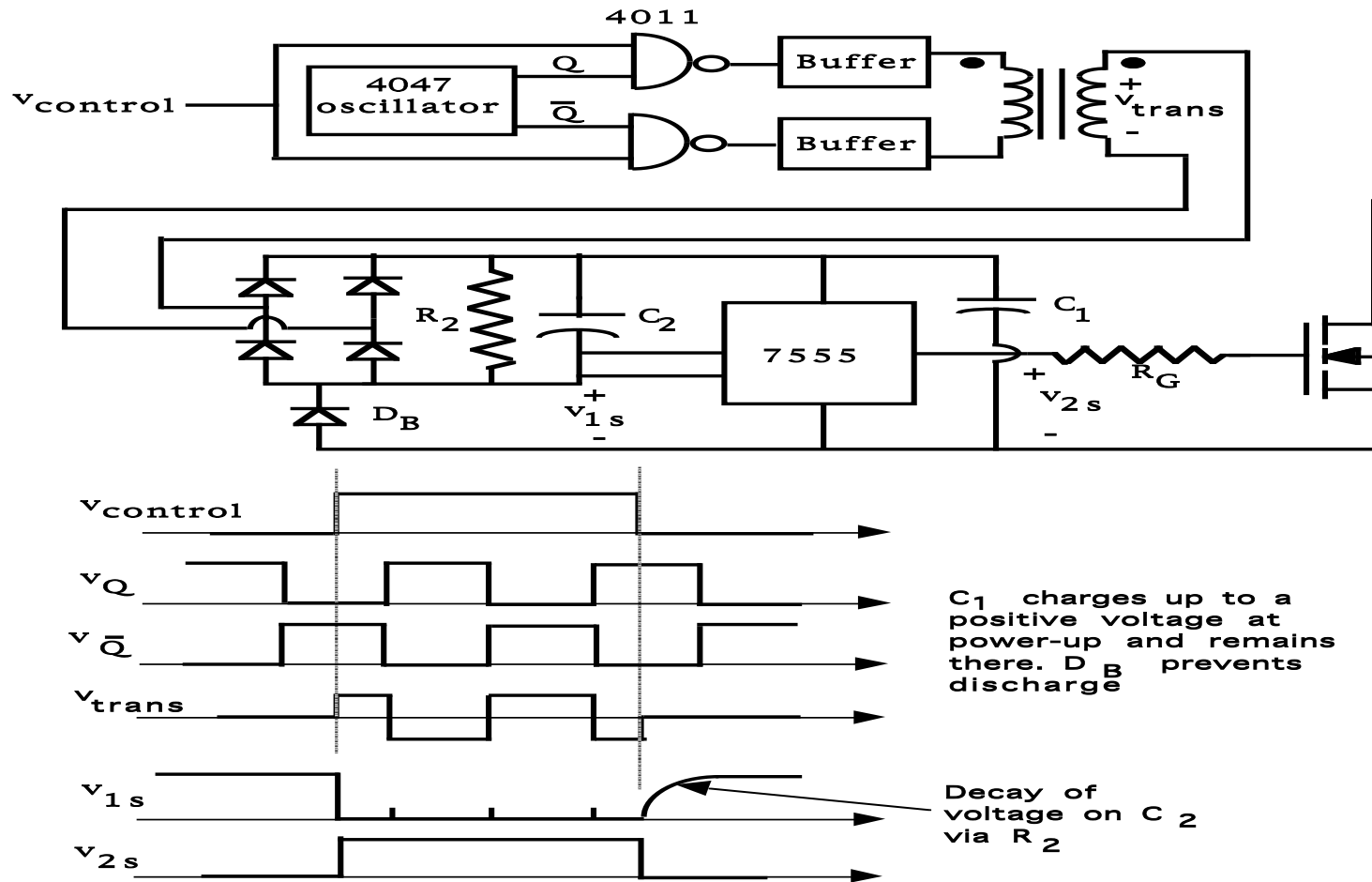Isolated Drive Without Auxiliary DC Supplies - MOSFET Example




Emitter-Open Switching of BJTs

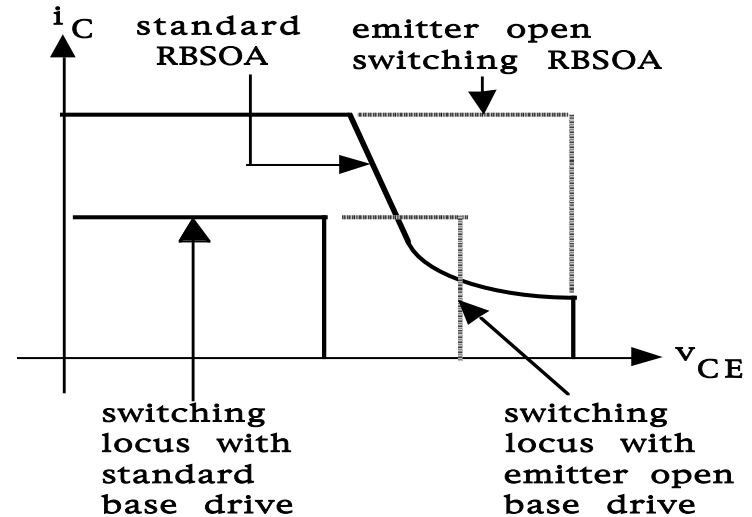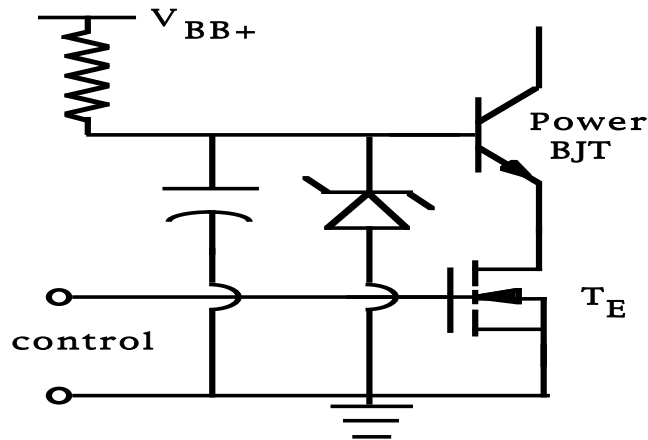


- Circuit operation
 - Turn on power BJT by turning on MOSFET T_E .
 - Turn off power BJT by turning off MOSFET T_E .
 - Collector current flows out base as negative base current.
 - Greater $i_B(\text{off})$ compared to standard drive circuits $i_C = \beta i_B(\text{off})$ removes stored charge much faster
 - Turn off times reduced (up to ten times).
- On-state losses of series combination of MOSFET and BJT minimized.
 - Low voltage MOSFET which has low losses can be used. Maximum off-state MOSFET voltage limited by Zener diode.
 - BJT base emitter junction reverse biased when T_E off so breakdown rating of BJT given by BV_{CBO} instead of BV_{CEO} . With lower BV_{CEO} rating, BJT losses in on-state reduced.
- Circuit also useful for GTOs and FCTs.

Thyristor Gate Drive Circuit

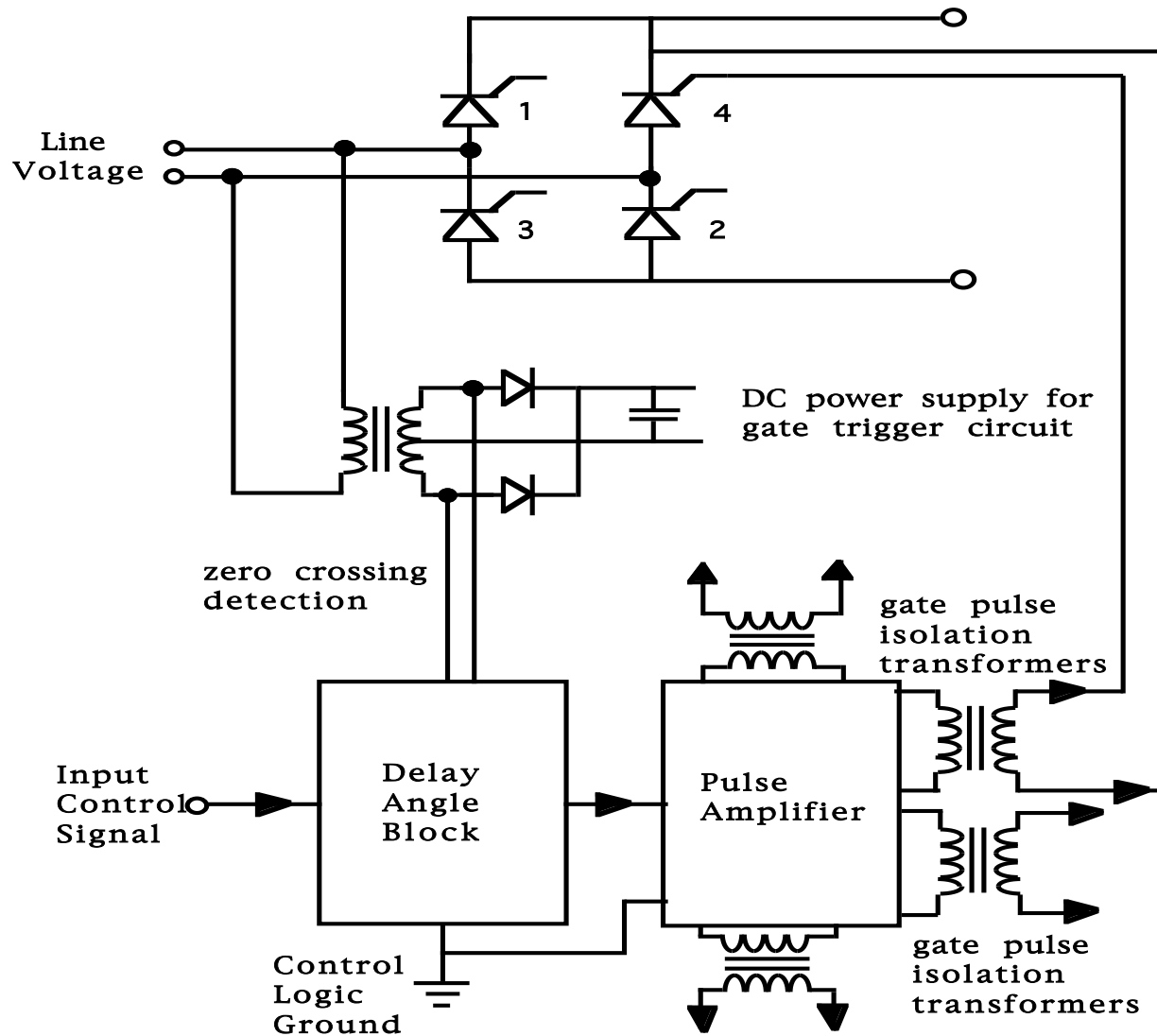


Delay angle block is commercially available integrated circuit - TCA780 circuit family

Thyristor Gate Drive Circuit (cont.)

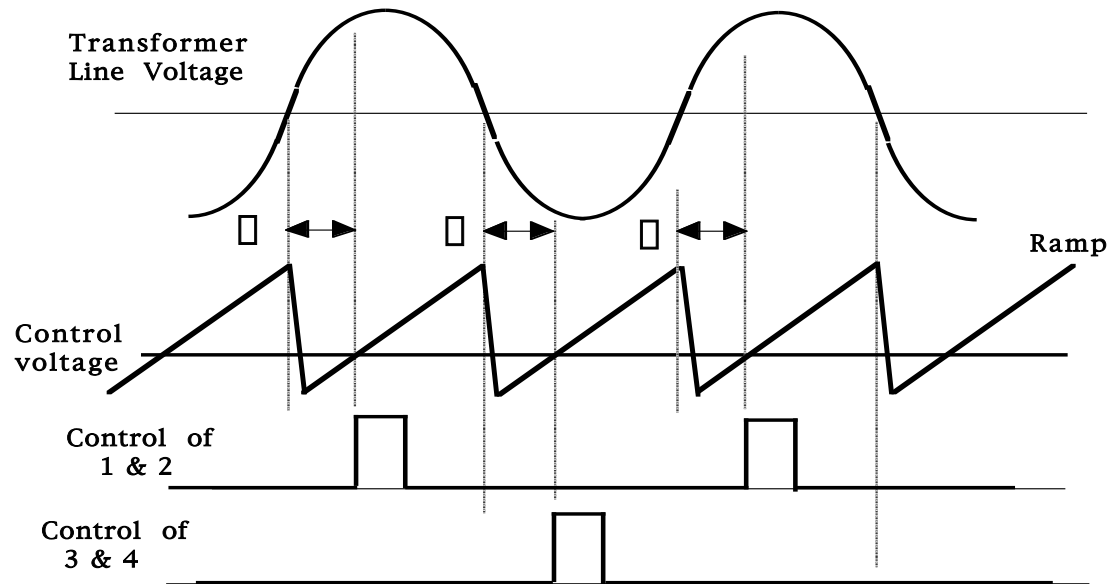


Thyristor gate drive waveforms

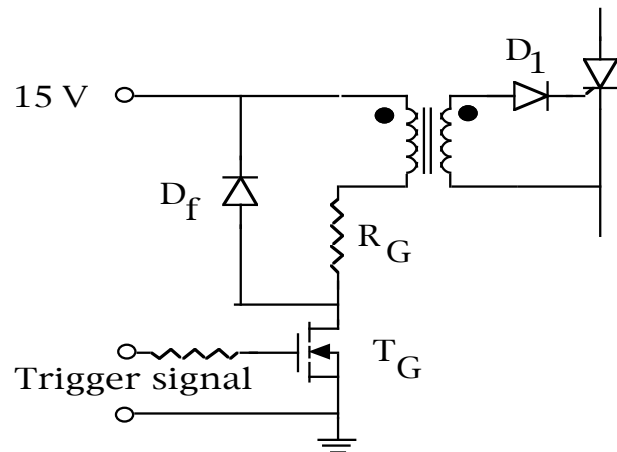


Gate pulse amplifier

GTO Gate Drive Circuit

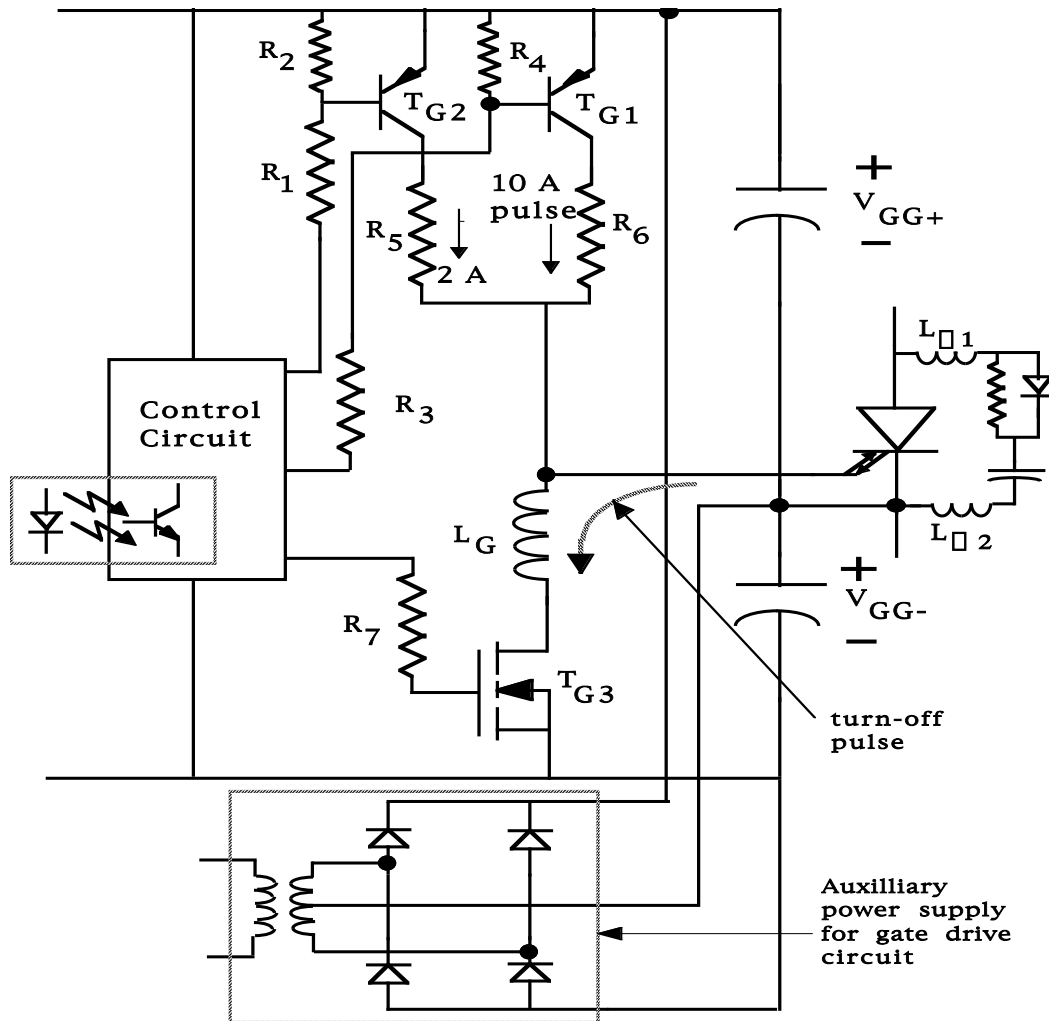


- Turn on T_{G1} and T_{G2} to get large front-porch current
- Turn off T_{G1} after some specified time to reduce total gate current to back-porch value.

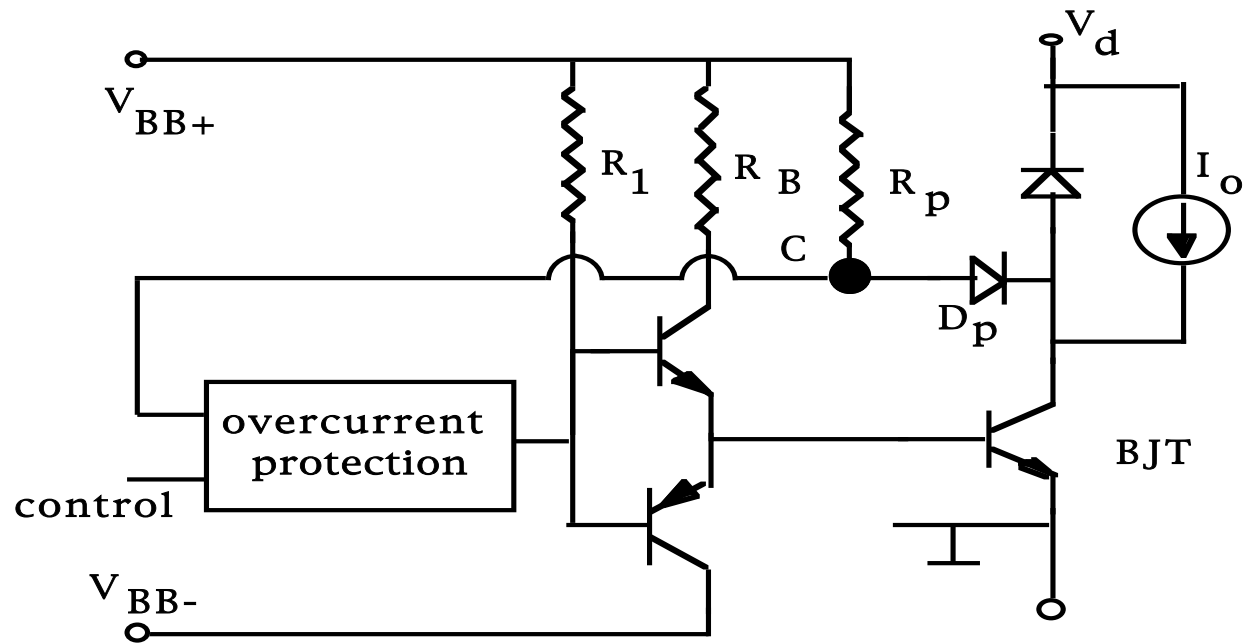Overcurrent Protection With Drive Circuits




- Point C one diode drop above $V_{CE(sat)}$ when BJT is on. Overcurrent will increase V_{CE} and thus potential at C.
- If C rises above a threshold value and control signal is biasing BJT on, overcurrent protection block will turn off BJT. Conservative design would keep BJT off until a manual reset had been done.

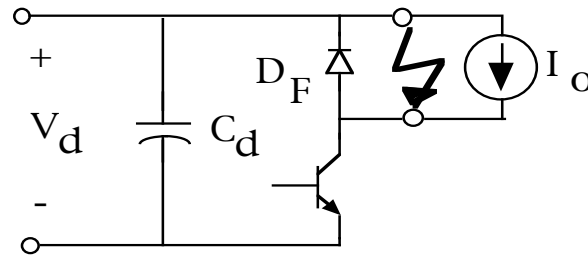Limiting Overcurrents by Limiting On-state Base Current




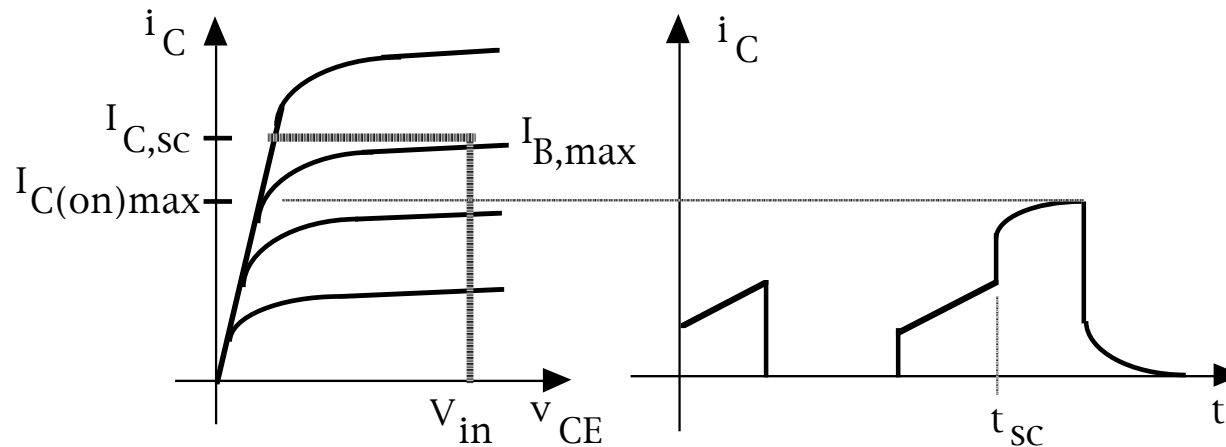- Stepdown converter with short circuit at $t = t_{sc}$





- Overcurrent limited to $I_{C(on)max} < I_{C,sc}$ by keeping $I_{B,max} < I_{C,sc}/b$
- $I_{C,sc}$ = maximum allowable instantaneous collector current
- Same approach can be used with MOSFETs and IGBTs. V_{GS} must be restricted to keep drain current to safe values.


Blanking Times in Bridge Circuit Drives

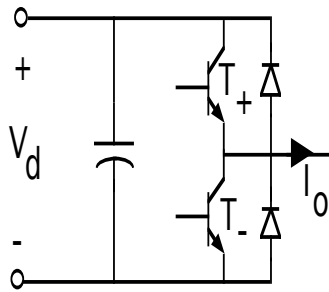

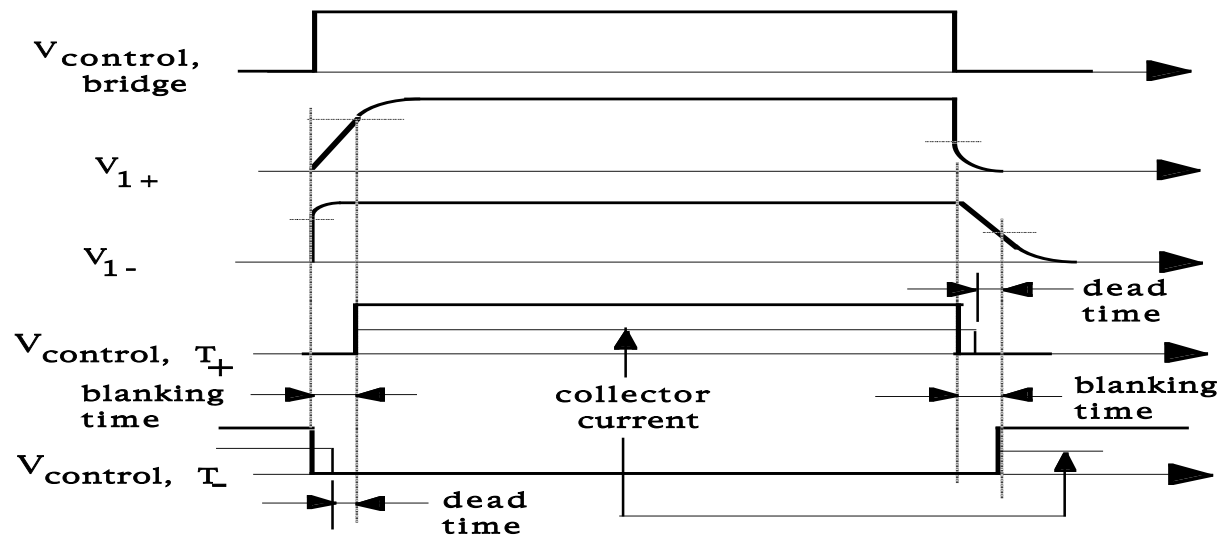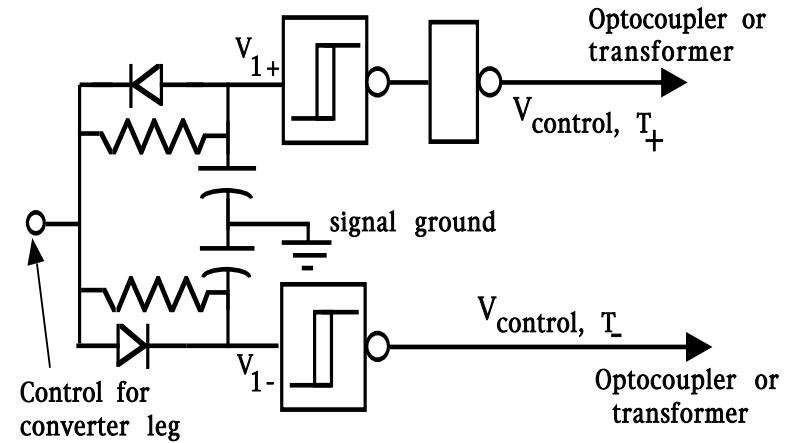- Turn off T_+ before turning on T_- in order to avoid cross-conduction (shorting out of V_d)





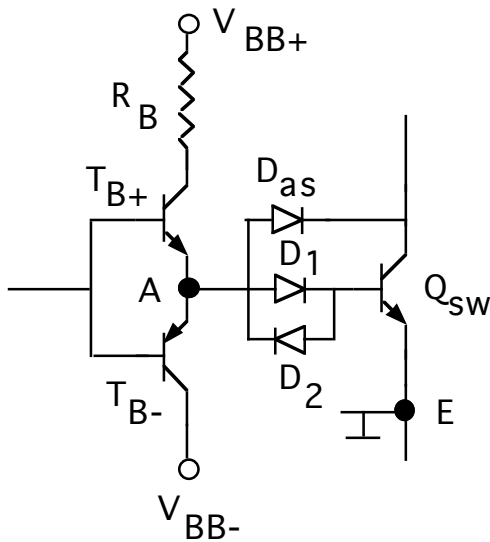Drive Circuit Waveshaping for Improved Operation




- Anti-saturation diode D_{as} keeps Q_{sw} active.
 - $V_{AE} = V_{BE(on)} + V_{D1} = V_{CE(on)} + V_{das}$
 - $V_{CE(on)} = V_{BE(on)} > V_{CE(sat)}$ because $V_{D1} = V_{das}$
- D_s provides path for negative base current at Q_{sw} turn-off.
- Storage delay time at turn-off reduced but on-state losses increase slightly.

Speed-up capacitors

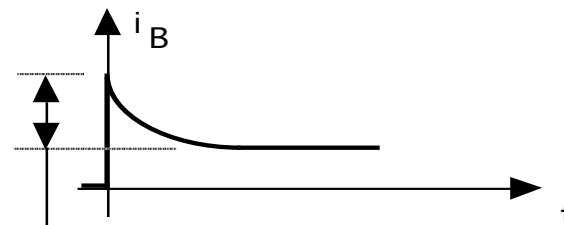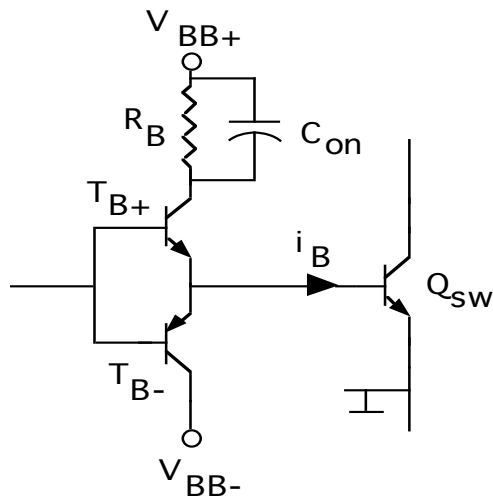



- Transient overdrive provided via C_{on} for faster turn-on of switch
- Same concept can be applied to MOSFET and IGBT drive circuits

Drive Circuit Waveshaping (cont.)

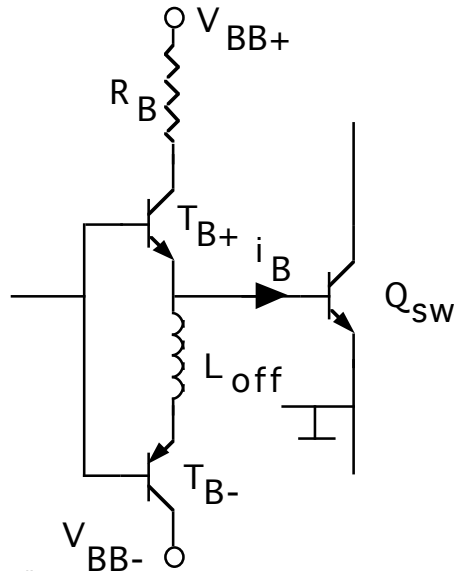

Controlled rate of change of turn-off base current

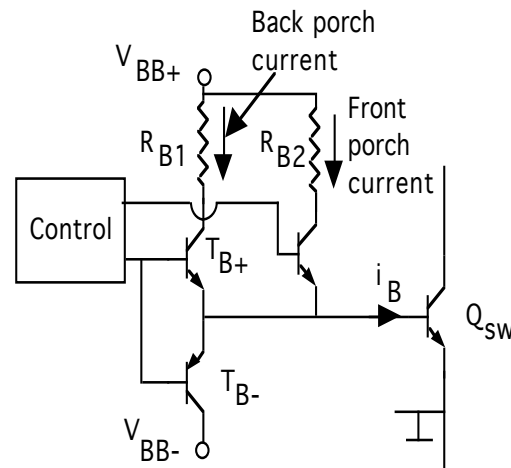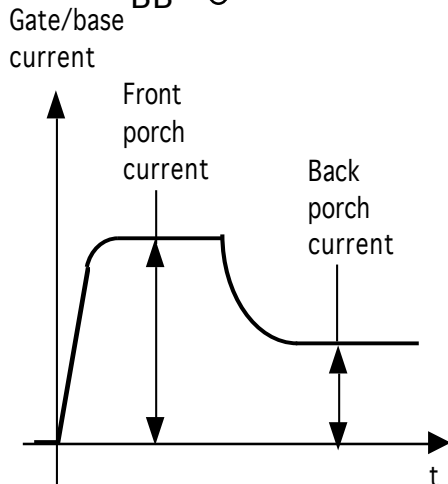
- Excessively long collector current tailing time at BJT turn-off if $di_B(\text{off})/dt$ is too large.
- Inductor L_{off} restricts $di_B(\text{off})/dt$ to $-V_{\text{BB-}}/L_{\text{off}}$



Front porch, back porch gate/base currents at turn-on

- Faster turn-on without putting device deeply into on-state where turn-off delay time will be substantially increased.
- Applicable to BJTs, MOSFETs, IGBTs, and GTOs.


Circuit/Component Layout Considerations

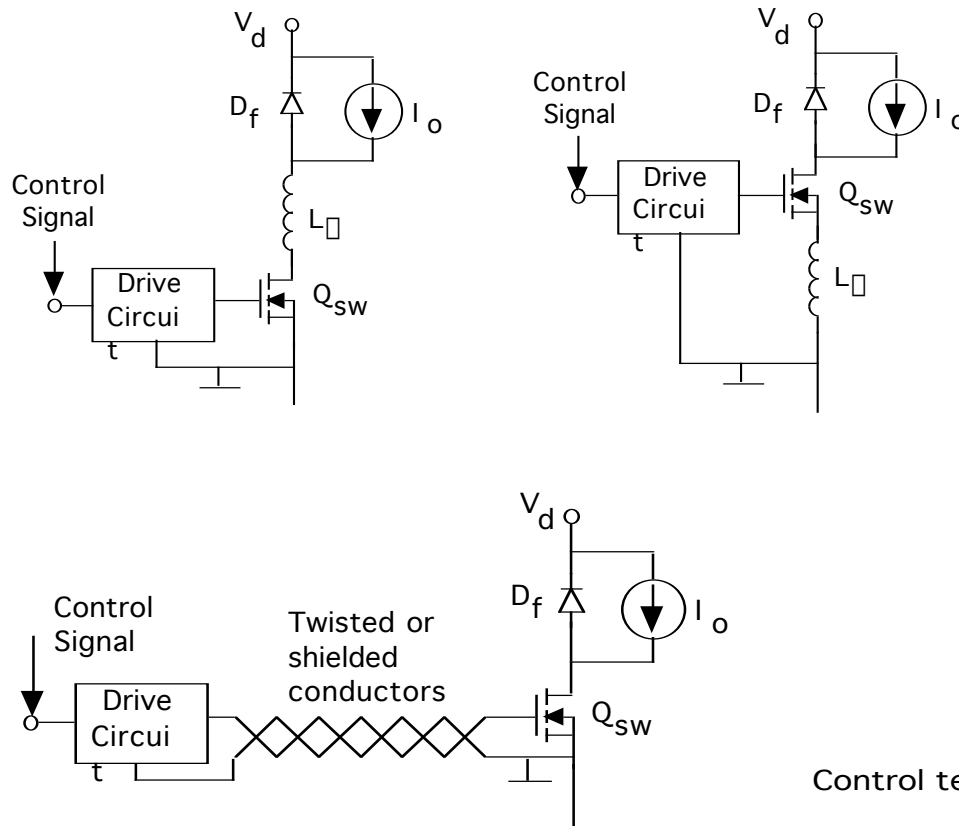

Use shielded conductors to connect drive circuit to power switch if there must be any appreciable separation (few cm or more) between them

Prime consideration is minimizing stray inductance

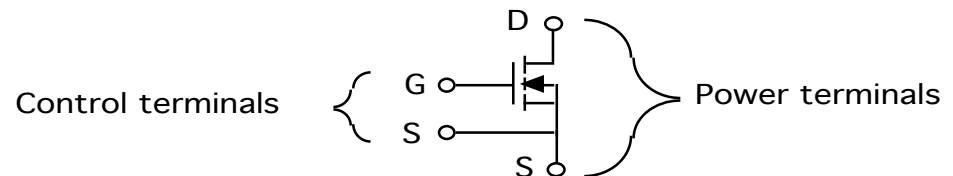- Stray inductance in series with high-voltage side of power device Q_{sw} causes overvoltage at turn-off.
- Stray inductance in series with low-voltage side power device Q_{sw} can cause oscillations at turn-on and turn-off.
- One cm of unshielded lead has about 5 nH of series inductance.
- Keep unshielded lead lengths to an absolute minimum.



Some power devices provided with four leads, two input leads and two power leads, to minimize stray inductance in input circuit.