

Chapter 3

Review of Basic Electrical and Magnetic Circuit Concepts

Chapter 3	Review of Basic Electrical and Magnetic Circuit Concepts	33
3-1	Introduction	33
3-2	Electric Circuits	33
3-3	Magnetic Circuits	46
	<i>Summary</i>	<i>57</i>
	<i>Problems</i>	<i>58</i>
	<i>References</i>	<i>60</i>

Symbols and Conventions

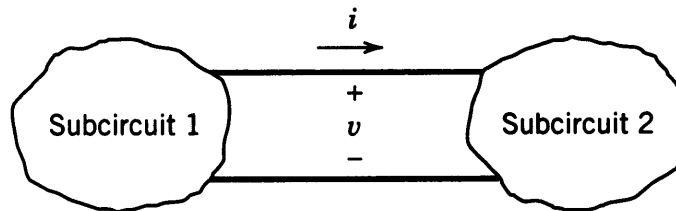


Figure 3-1 Instantaneous power flow.

- Symbols
- Polarity of Voltages; Direction of Currents
- MKS SI units

Sinusoidal Steady State

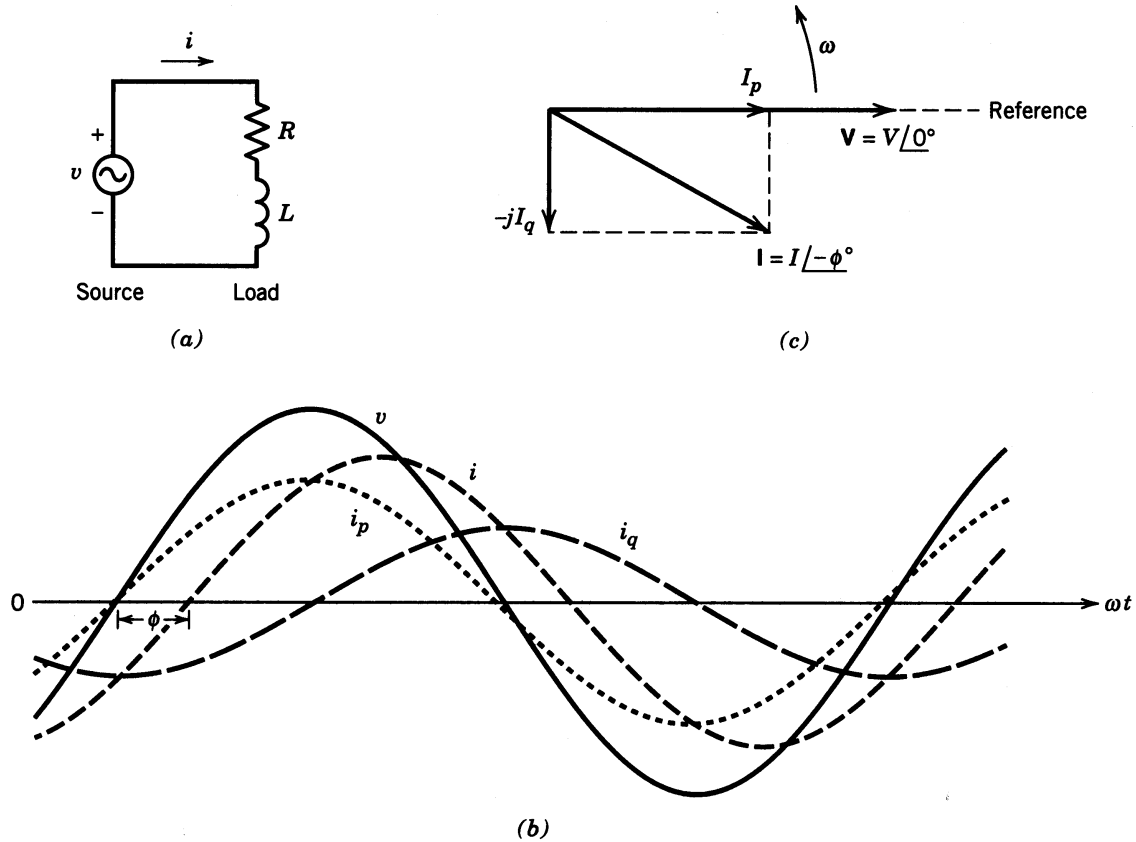


Figure 3-2 Sinusoidal steady state.

Three-Phase Circuit

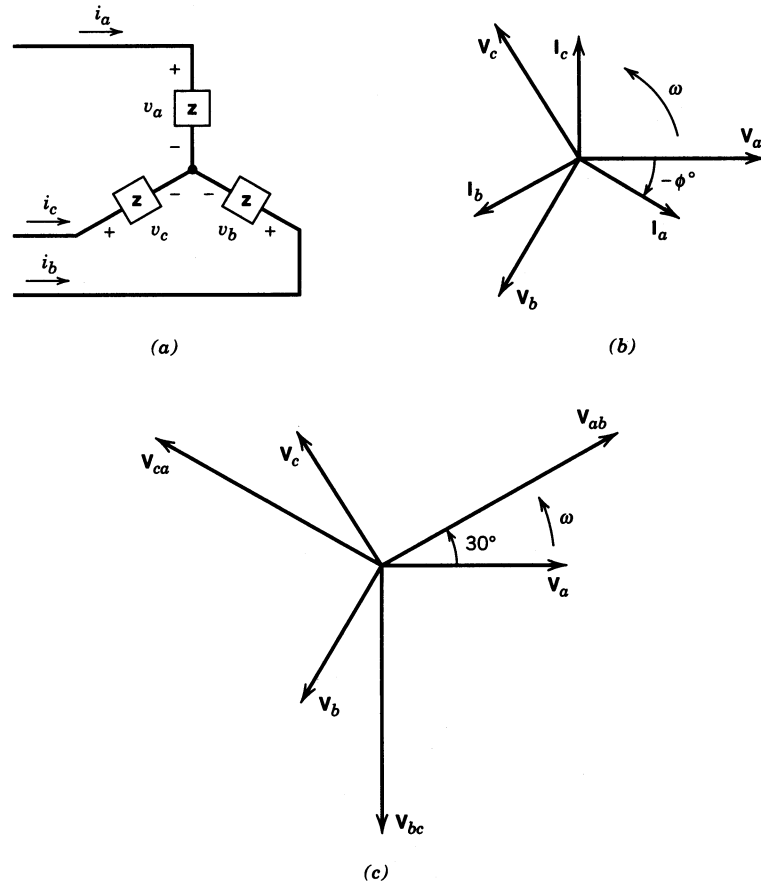


Figure 3-3 Three-phase circuit.

Steady State in Power Electronics

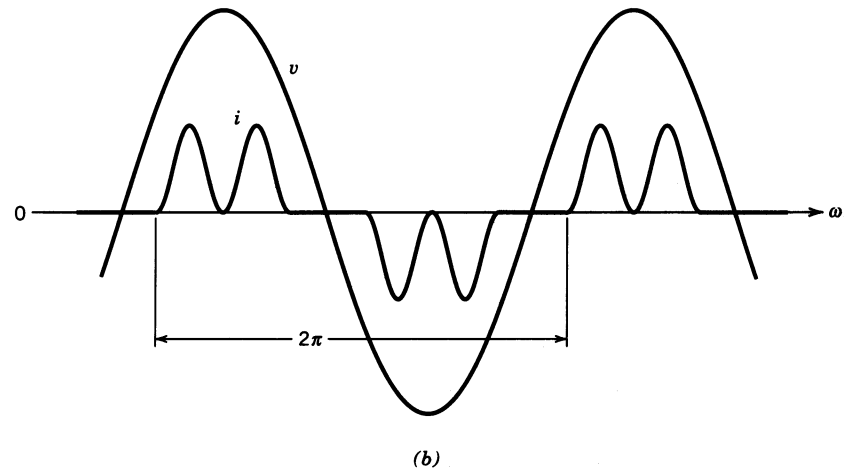
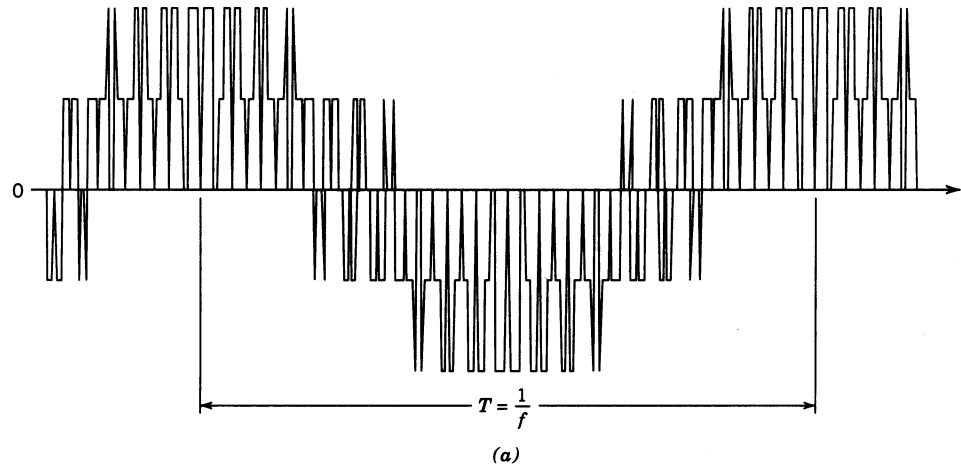


Figure 3-4 Nonsinusoidal waveforms in steady state.

Fourier Analysis

Table 3-1 Use of Symmetry in Fourier Analysis

<i>Symmetry</i>	<i>Condition Required</i>	<i>a_h and b_h</i>
Even	$f(-t) = f(t)$	$b_h = 0 \quad a_h = \frac{2}{\pi} \int_0^{\pi} f(t) \cos(h\omega t) d(\omega t)$
Odd	$f(-t) = -f(t)$	$a_h = 0 \quad b_h = \frac{2}{\pi} \int_0^{\pi} f(t) \sin(h\omega t) d(\omega t)$
Half-wave	$f(t) = -f(t + \frac{1}{2}T)$	$a_h = b_h = 0$ for even h $a_h = \frac{2}{\pi} \int_0^{\pi} f(t) \cos(h\omega t) d(\omega t)$ for odd h $b_h = \frac{2}{\pi} \int_0^{\pi} f(t) \sin(h\omega t) d(\omega t)$ for odd h
Even quarter-wave	Even and half-wave	$b_h = 0$ for all h $a_h = \begin{cases} \frac{4}{\pi} \int_0^{\pi/2} f(t) \cos(h\omega t) d(\omega t) & \text{for odd } h \\ 0 & \text{for even } h \end{cases}$
Odd quarter-wave	Odd and half-wave	$a_h = 0$ for all h $b_h = \begin{cases} \frac{4}{\pi} \int_0^{\pi/2} f(t) \sin(h\omega t) d(\omega t) & \text{for odd } h \\ 0 & \text{for even } h \end{cases}$

Distortion in the Input Current

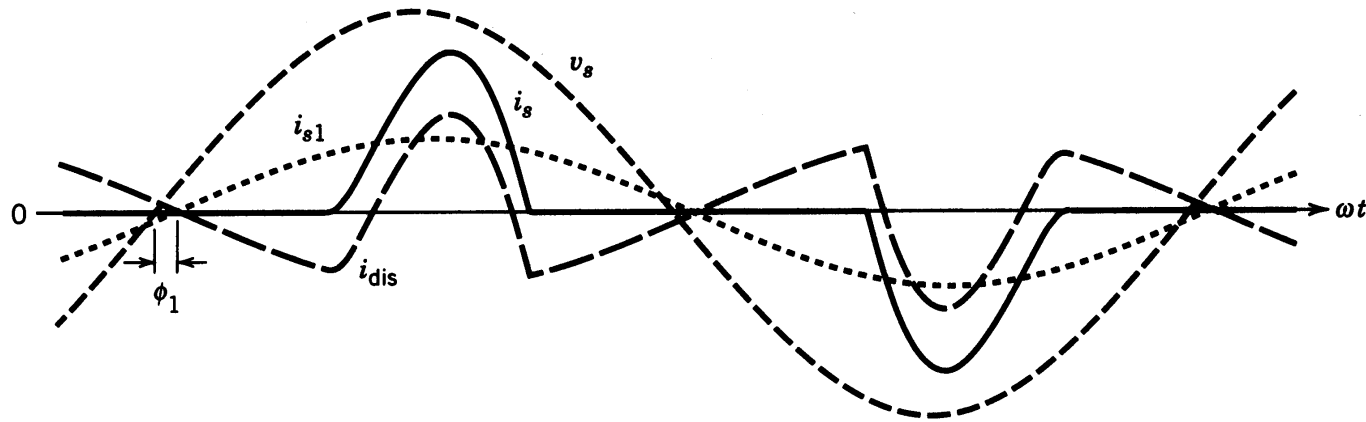


Figure 3-5 Line-current distortion.

- Voltage is assumed to be sinusoidal
- Subscript “1” refers to the fundamental
- The angle is between the voltage and the current fundamental

Phasor Representation

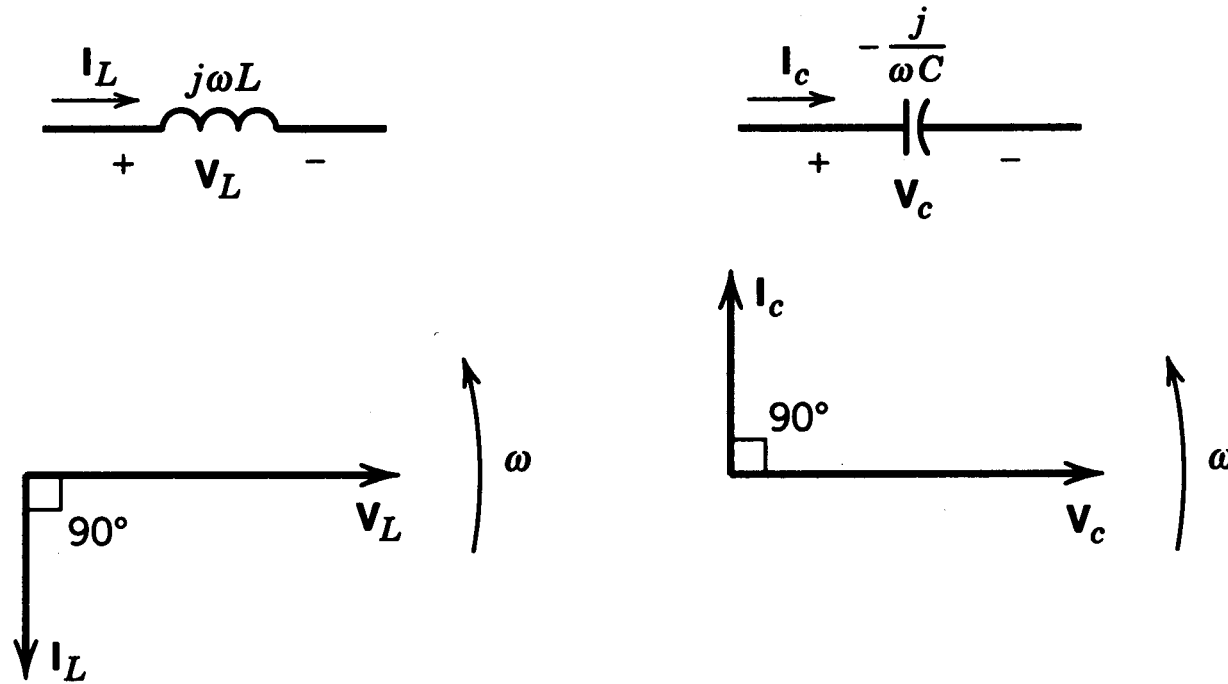


Figure 3-6 Phasor representation.

Response of L and C

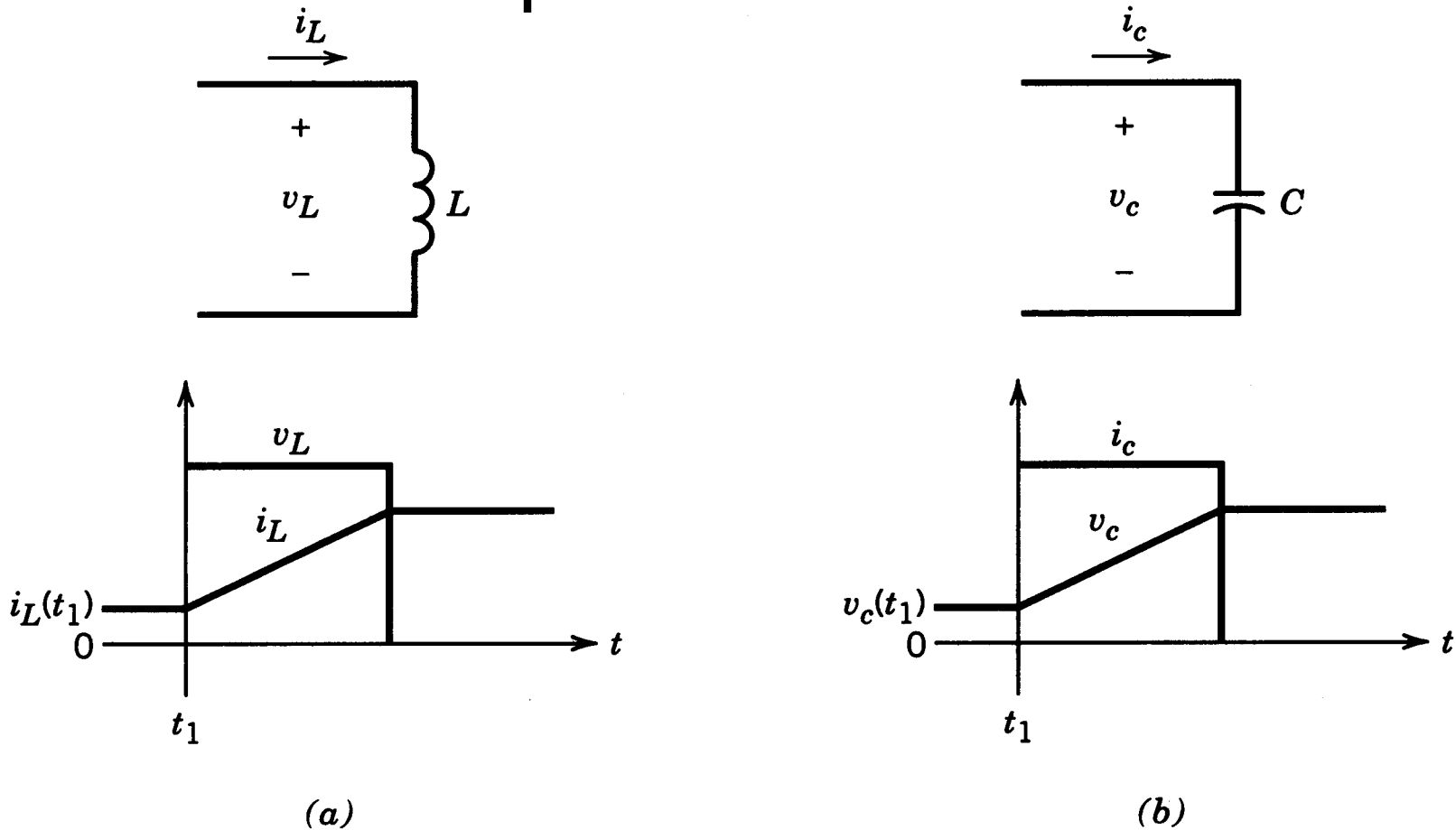


Figure 3-7 Inductor and capacitor response.

Inductor Voltage and Current in Steady State


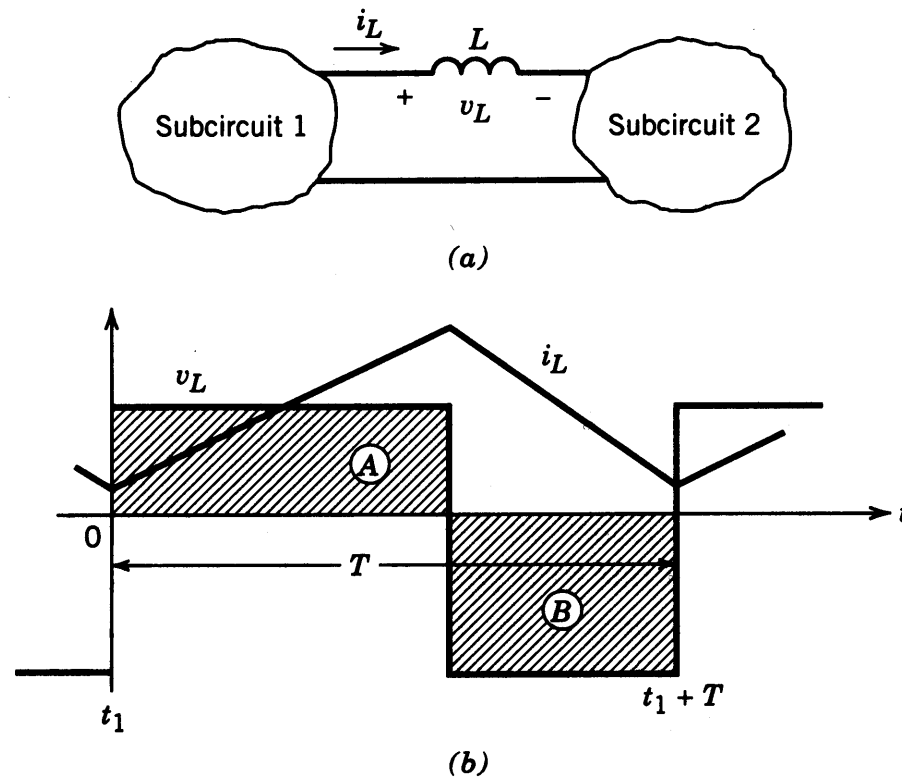


Figure 3-8 Inductor response in steady state.


- Volt-seconds over T equal zero.

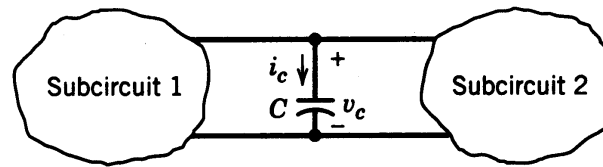Capacitor Voltage and Current in Steady State



(a)

- Amp-seconds over T equal zero.

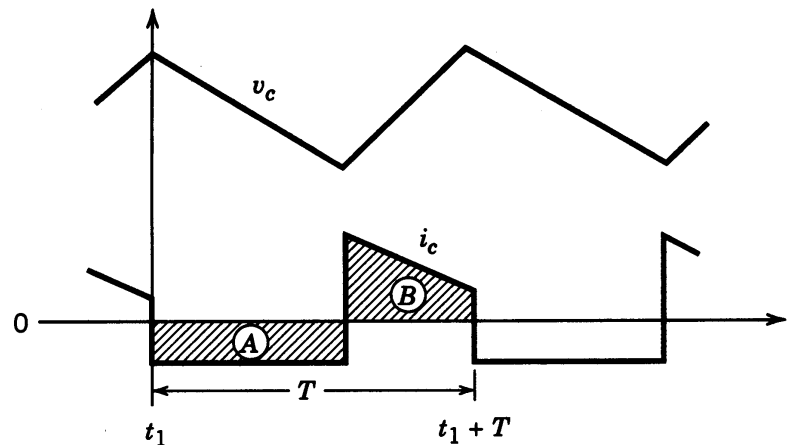

(b)

Figure 3-9 Capacitor response in steady state.

Ampere's Law

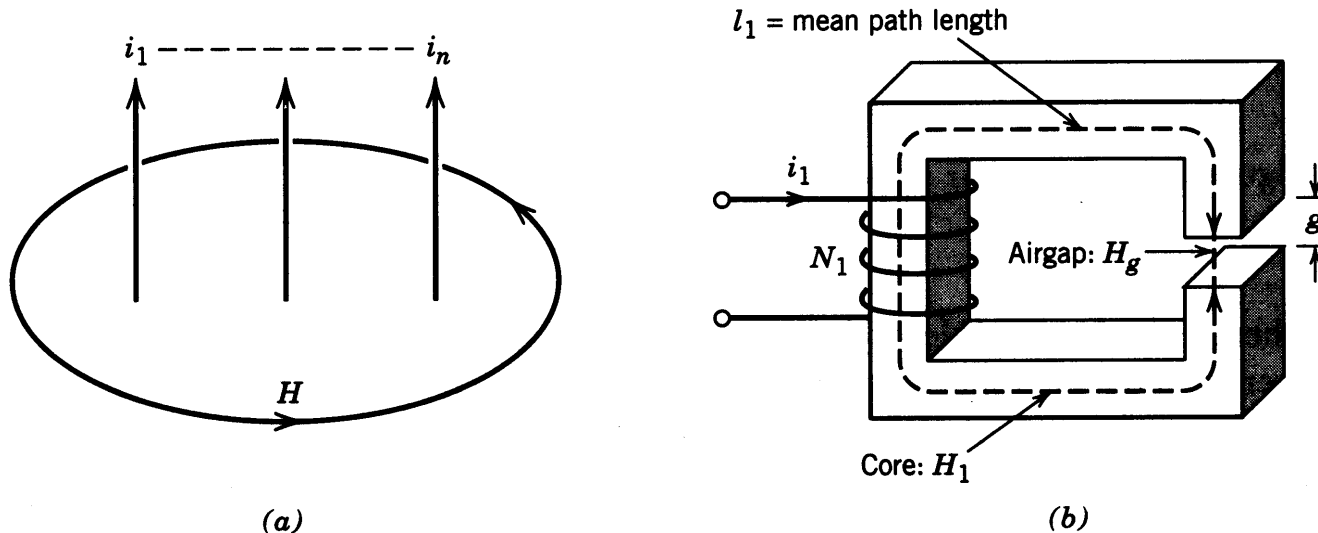


Figure 3-10 (a) General formulation of Ampere's law. (b) Specific example of Ampere's law in the case of a winding on a magnetic core with an airgap.

- Direction of magnetic field due to currents
- Ampere's Law: Magnetic field along a path

Direction of Magnetic Field

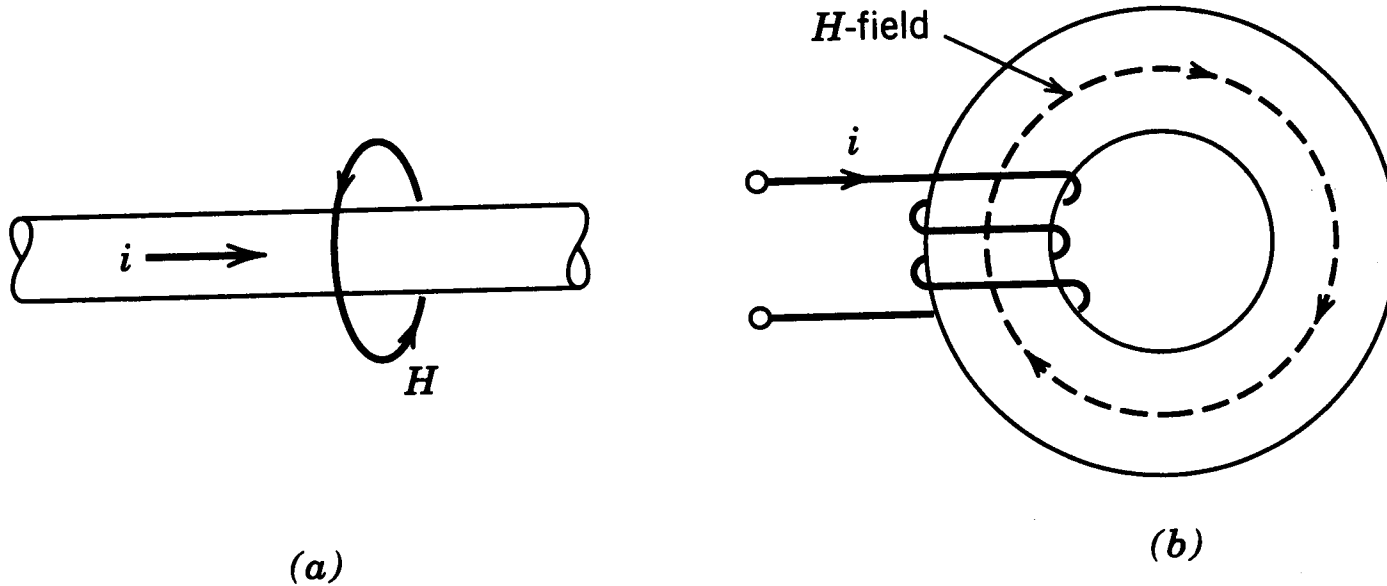


Figure 3-11 Determination of the magnetic field direction via the right-hand rule in (a) the general case and (b) a specific example of a current-carrying coil wound on a toroidal core.

B - H Relationship; Saturation

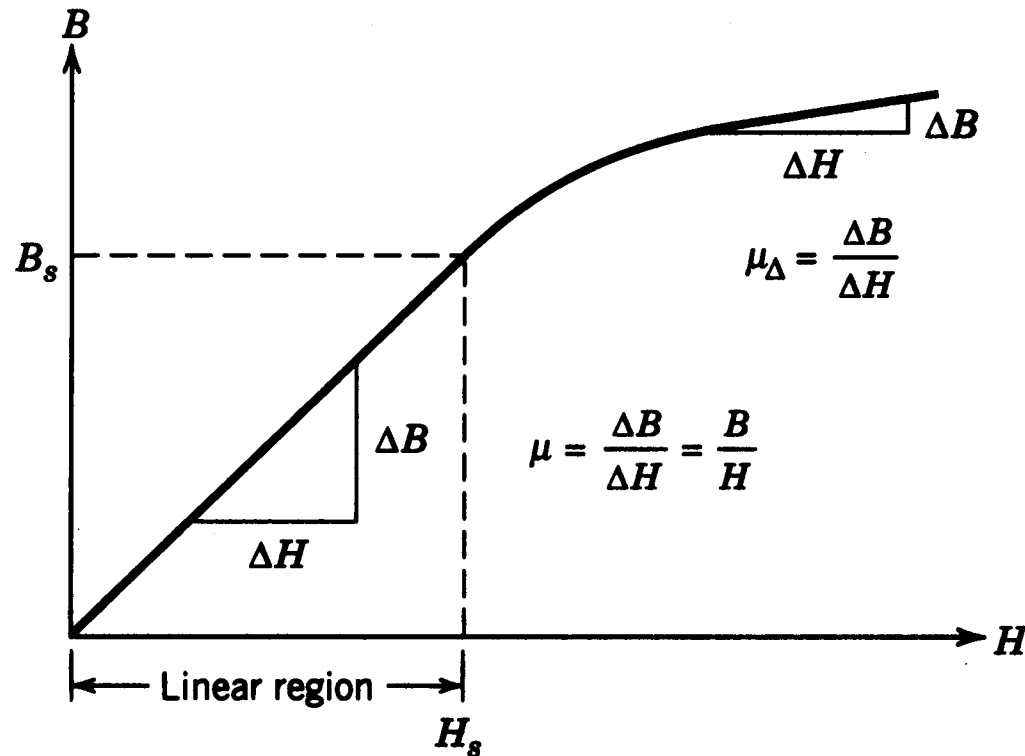


Figure 3-12 Relation between B - and H -fields.

- Definition of permeability

Continuity of Flux-Lines

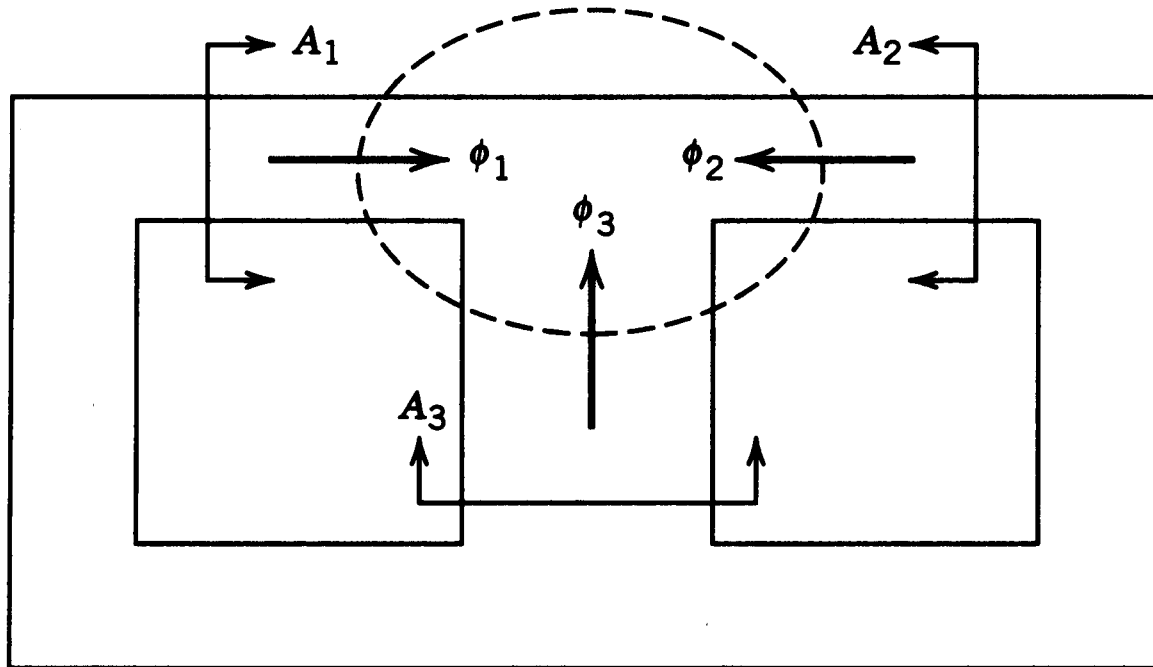


Figure 3-13 Continuity of flux.

$$\mathbf{f}_1 + \mathbf{f}_2 + \mathbf{f}_3 = 0$$

Concept of Magnetic Reluctance

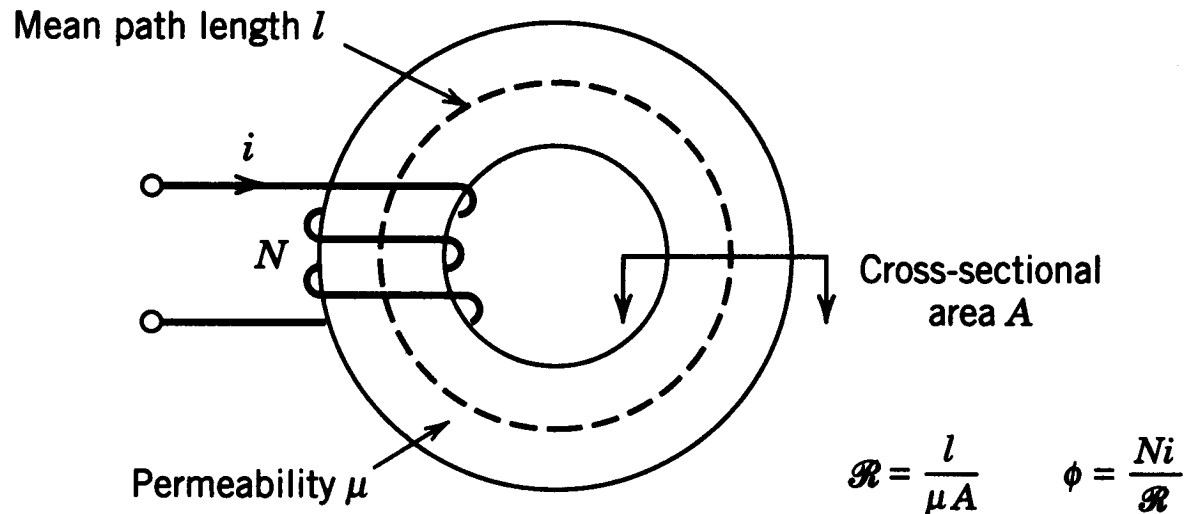


Figure 3-14 Magnetic reluctance.

- Flux is related to ampere-turns by reluctance

Analogy between Electrical and Magnetic Variables

Table 3-2 Electrical–Magnetic Analogy


<i>Magnetic Circuit</i>	<i>Electric Circuit</i>
mmf Ni	v
Flux ϕ	i
reluctance \mathcal{R}	R
permeability μ	$1/\rho$, where ρ = resistivity

Analogy between Equations in Electrical and Magnetic Circuits


Table 3-3 Magnetic–Electrical Circuit Equation Analogy

<i>Magnetic</i>	<i>Electrical (dc)</i>
$\frac{Ni}{\phi} = \mathcal{R} = \frac{l}{\mu A}$	Ohm's law: $\frac{v}{i} = R = \frac{l}{A/\rho}$
$\phi \sum_k \mathcal{R}_k = \sum_m N_m i_m$	Kirchhoff's voltage law: $i \sum_k R_k = \sum_m v_m$
$\sum \phi_k = 0$	Kirchhoff's current law: $\sum_k i_k = 0$

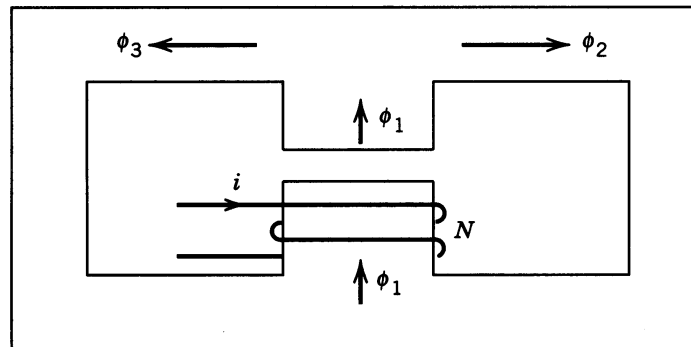Magnetic Circuit and its Electrical Analog



(a)

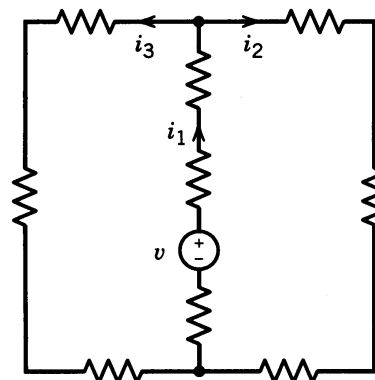

(b)

Figure 3-15 (a) Magnetic circuit. (b) An electrical analog.

Faraday's Law and Lenz's Law



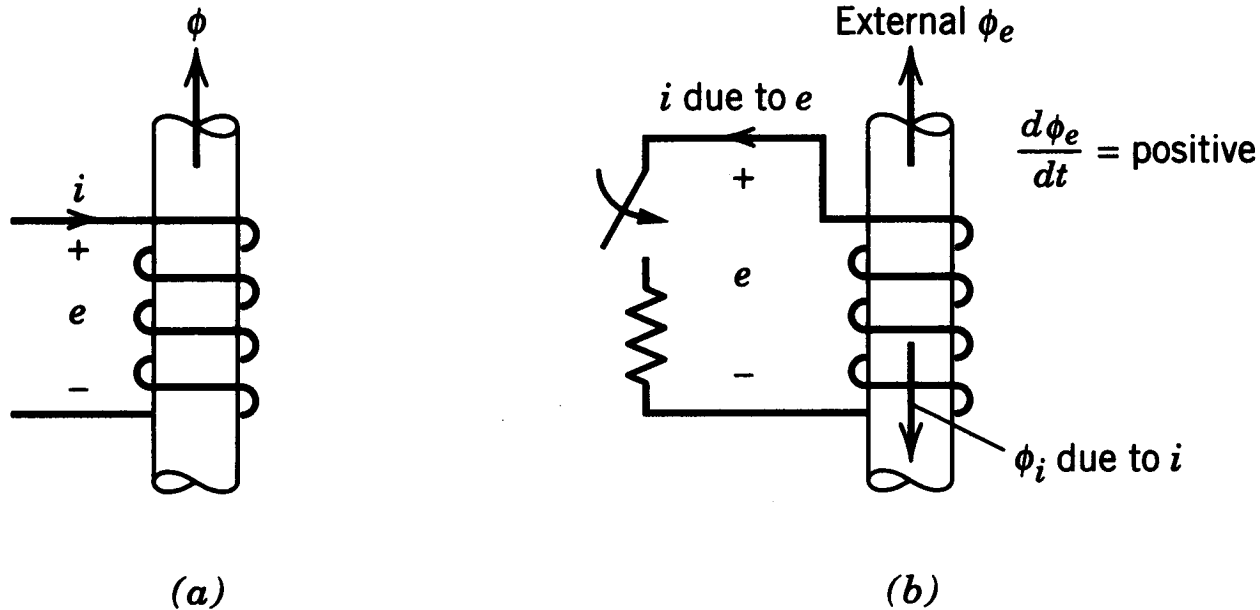


Figure 3-16 (a) Flux direction and voltage polarity.
(b) Lenz's law.

Inductance L

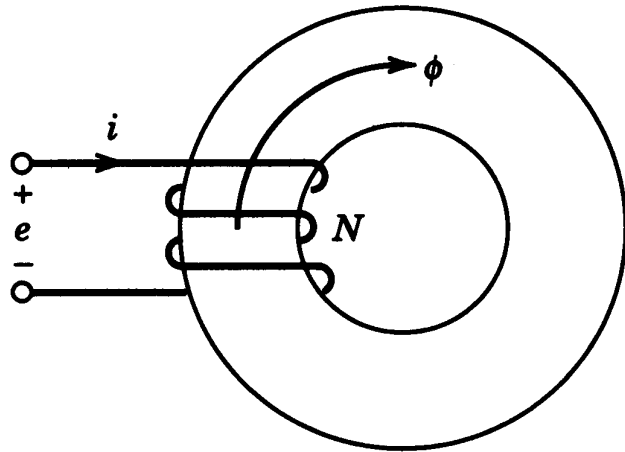

(a)

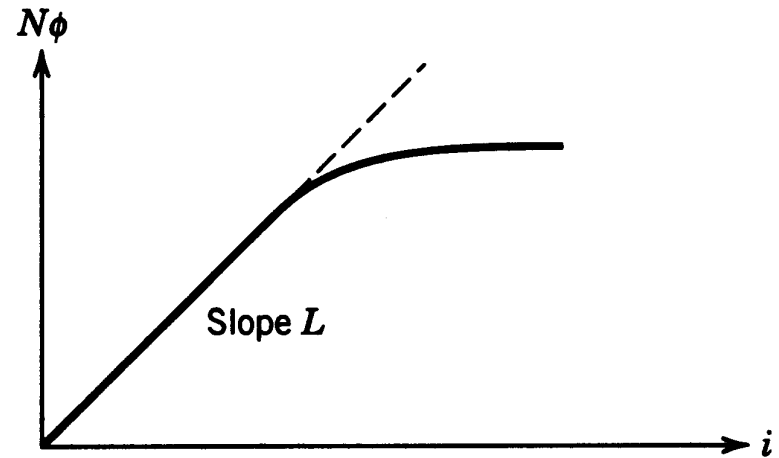

(b)

Figure 3-17 Self-inductance L .

- Inductance relates flux-linkage to current

Analysis of a Transformer



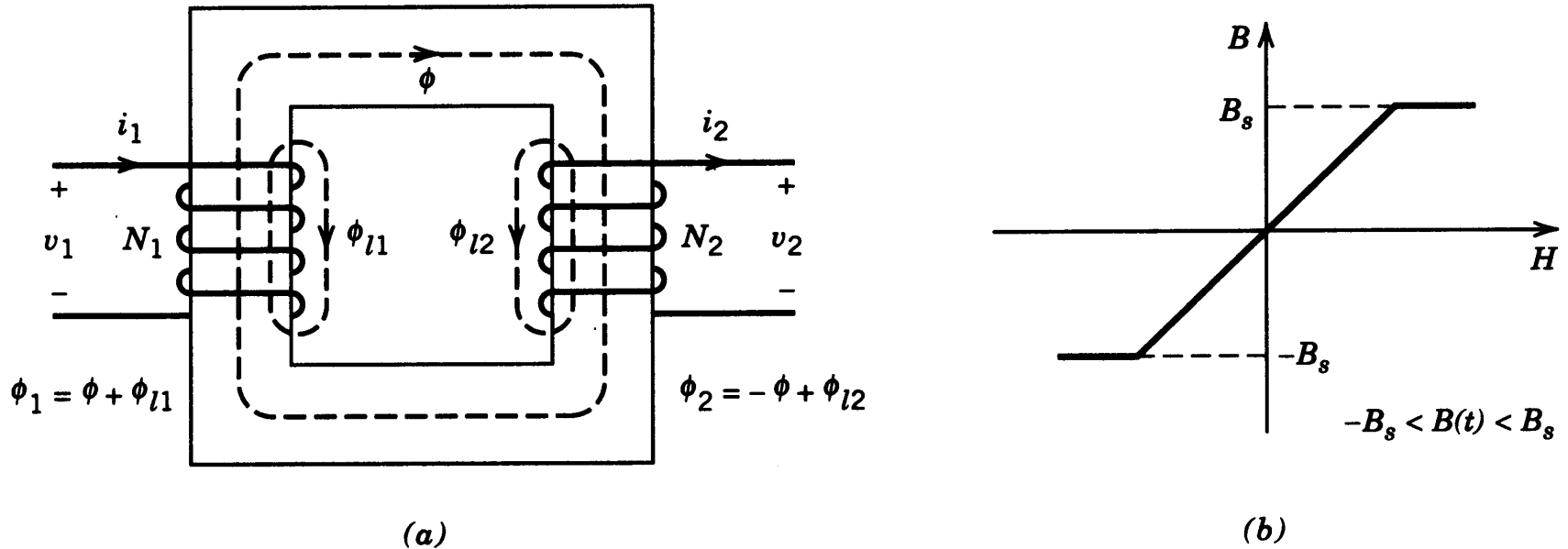


Figure 3-18 (a) Cross section of a transformer. (b) The $B-H$ characteristics of the core.

Transformer Equivalent Circuit

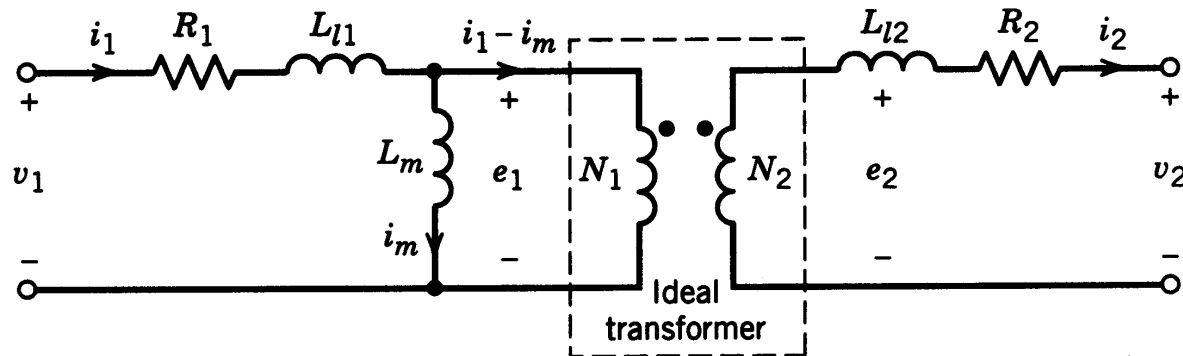


(a)

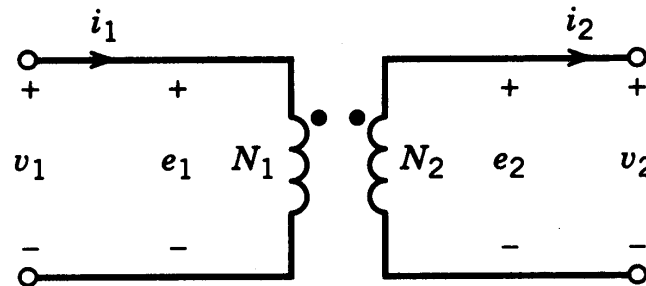


(b)

Figure 3-19 Equivalent circuit for (a) a physically realizable transformer wound on a lossless core and (b) an ideal transformer.

Including the Core Losses

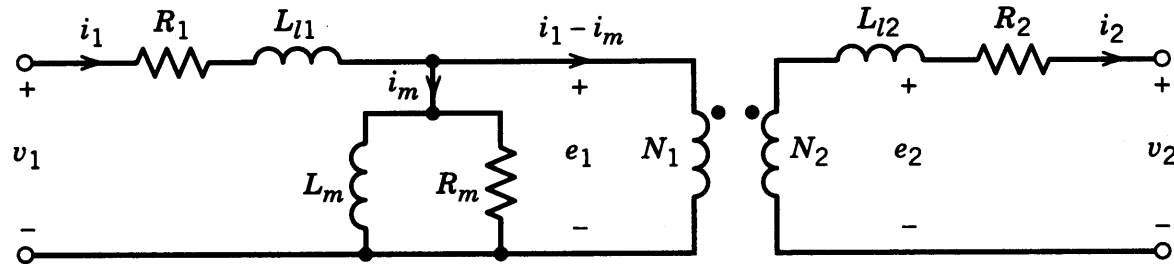

(a)

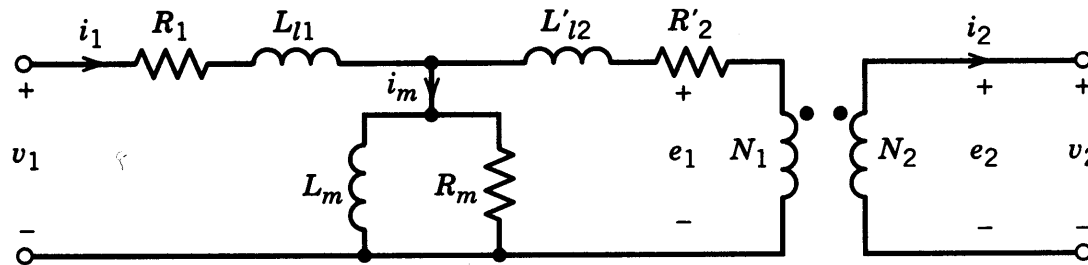

(b)

Figure 3-21 Equivalent circuit of a transformer including the effects of hysteresis loss. (a) Circuit components are on both sides (coil 1 and coil 2 sides) of the ideal transformer. (b) Components from the secondary (coil 2) side are reflected across the ideal transformer to the primary (coil 1) side.

Transformer Core Characteristic

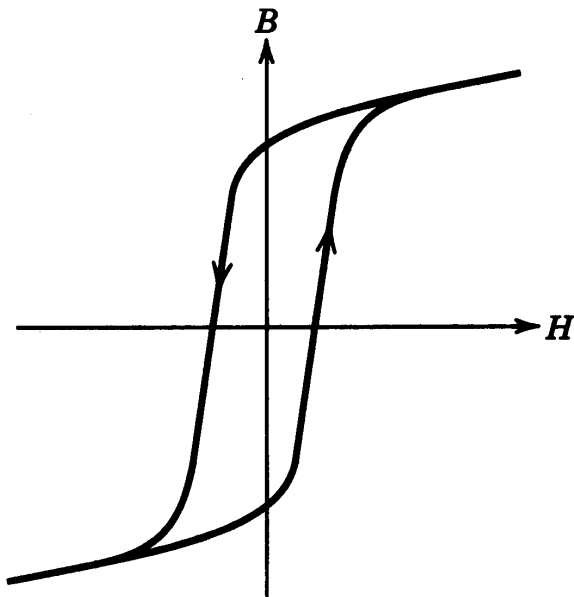


Figure 3-20 B - H characteristic of a transformer core having hysteresis and hence magnetic losses.