

Chapter 4

Computer Simulation

Chapter 4 Computer Simulation of Power Electronic Converters and Systems

61

4-1 Introduction	61
4-2 Challenges in Computer Simulation	62
4-3 Simulation Process	62
4-4 Mechanics of Simulation	64
4-5 Solution Techniques for Time-Domain Analysis	65
4-6 Widely Used, Circuit-Oriented Simulators	69
4-7 Equation Solvers	72
<i>Summary</i>	<i>74</i>
<i>Problems</i>	<i>74</i>
<i>References</i>	<i>75</i>

System to be Simulated

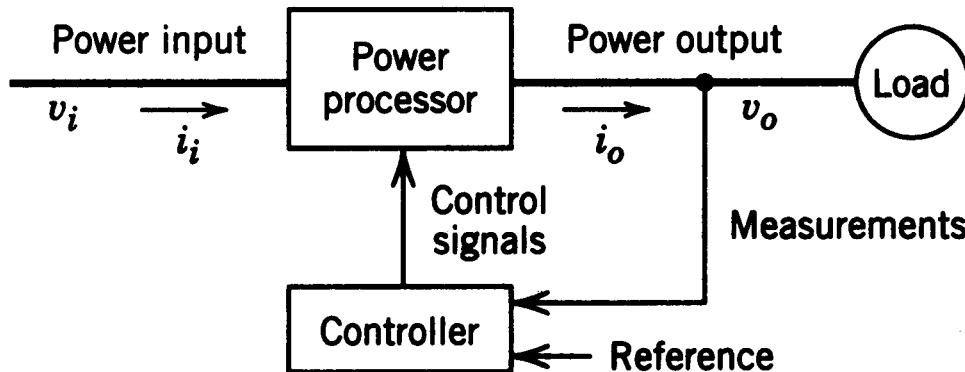


Figure 4-1 Power electronics system: a block diagram.

- Challenges in modeling power electronic systems

Large-Signal System Simulation

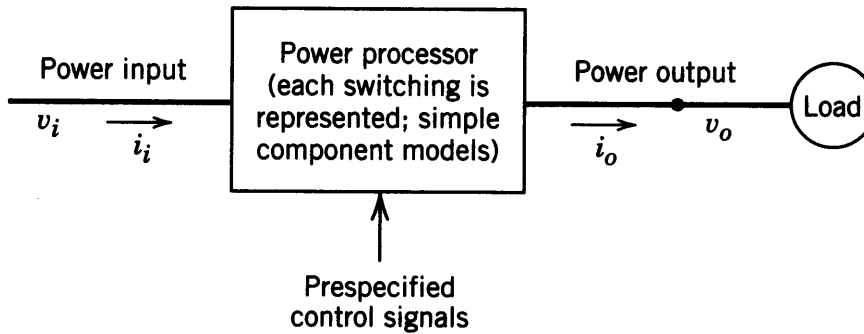


Figure 4-2 Open-loop, large-signal simulation.

- Simplest component models

Small-Signal Linearized Model for Controller Design

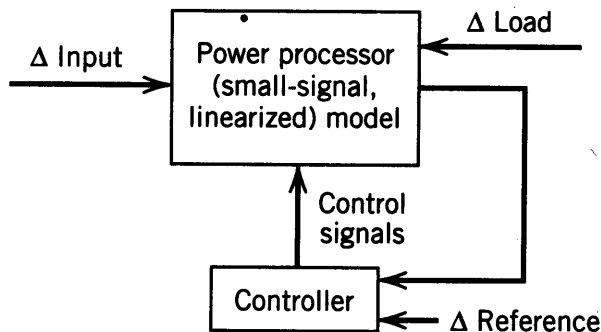


Figure 4-3 Small-signal (linear) model and controller design.

- System linearized around the steady-state point

Closed-Loop Operation: Large Disturbances

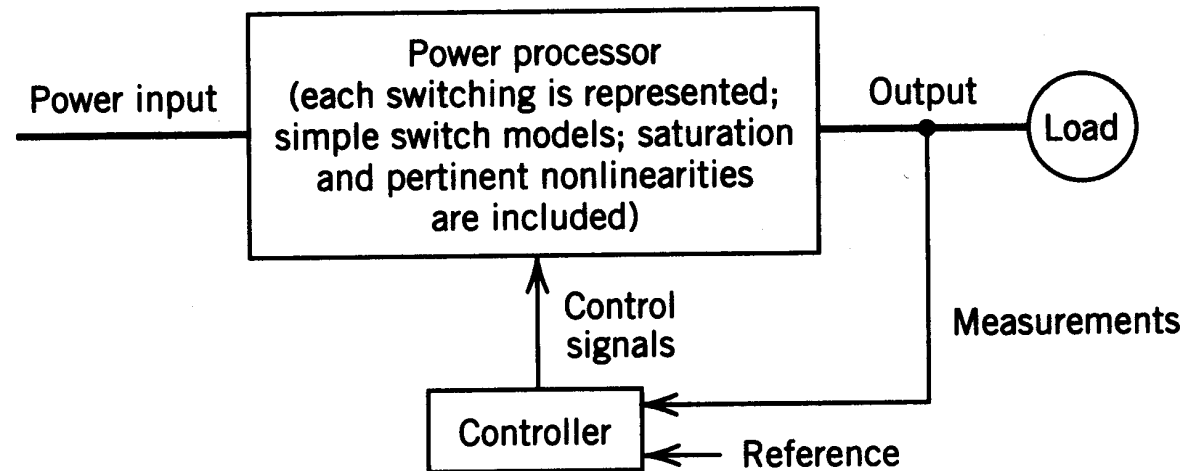


Figure 4-4 Closed-loop, large-signal system behavior.

- Simplest component models
- Nonlinearities, Limits, etc. are included

Modeling of Switching Operation


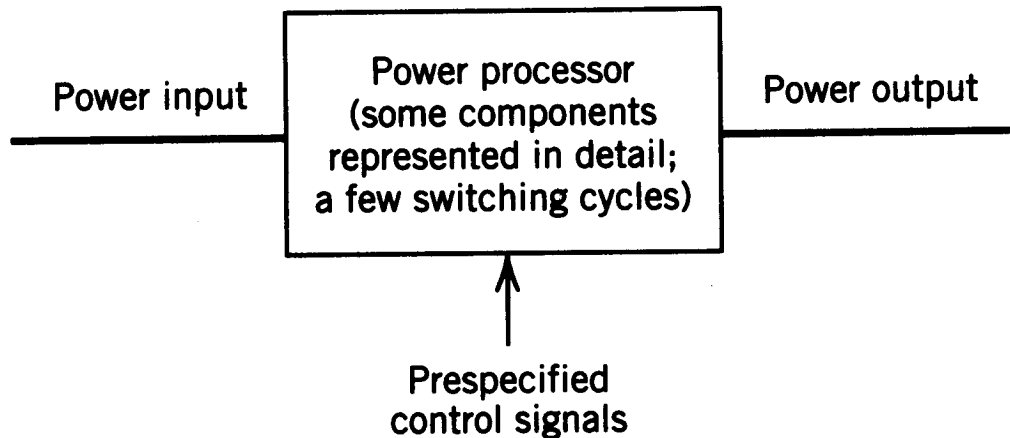



Figure 4-5 Switching details.

- Detailed device models
- Just a few switching cycles are studied

Modeling of a Simple Converter

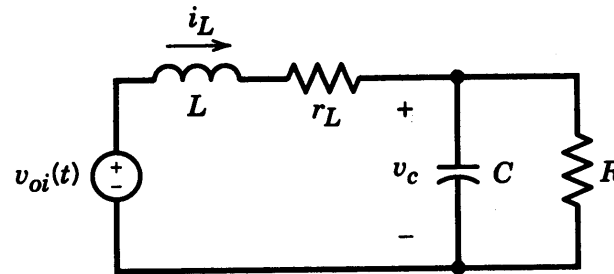

(a)

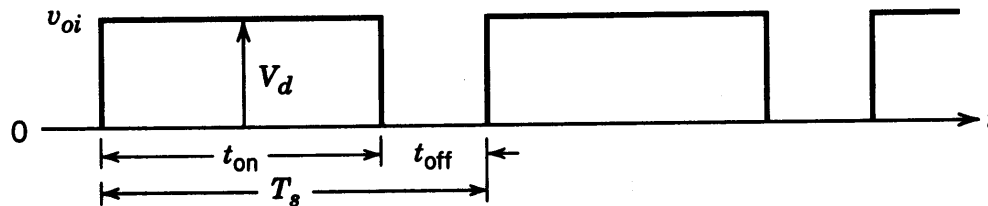

(b)

Figure 4-6 Simplified equivalent circuit of a switch-mode, regulated dc power supply (same as in Fig. 1-3).

- Input voltage takes on two discrete values

Trapezoidal Method of Integration


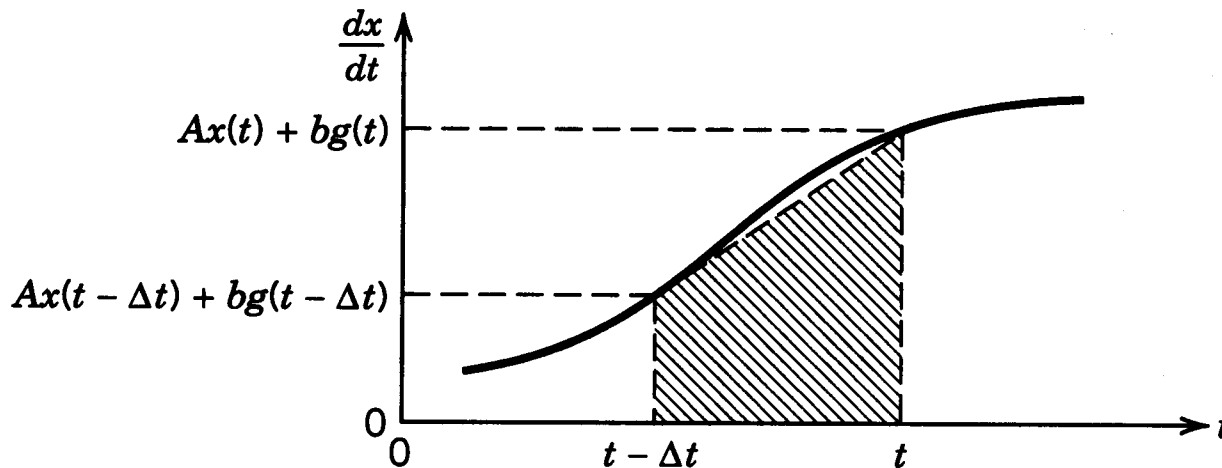



Figure 4-7
Trapezoidal method
of integration.

- The area shown above represents the integral

A Simple Example

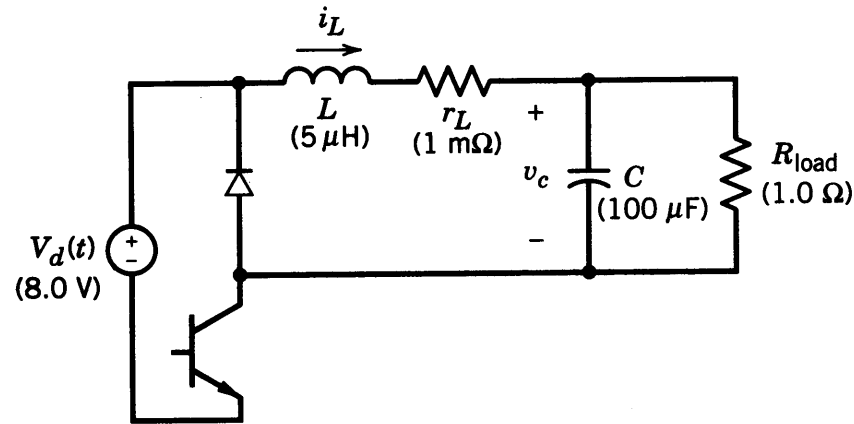

(a)

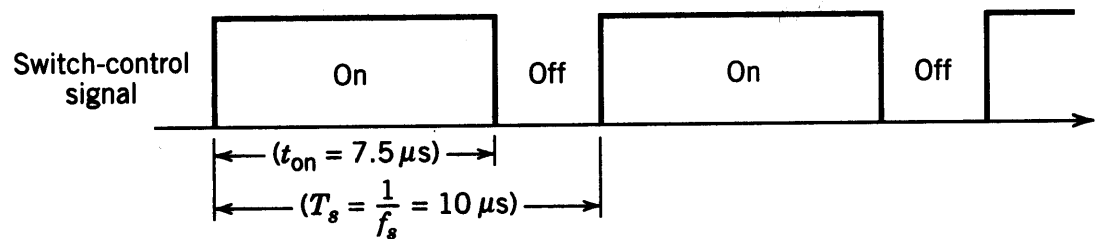


(b)

Figure 4-8 (a) Circuit for simulation. (b) Switch control waveform.

- The input voltage takes on two discrete values

Modeling using PSpice

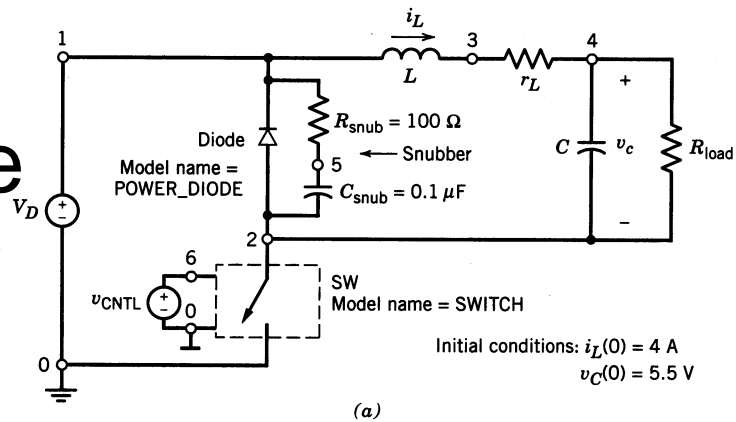

PSpice Example

```

*
DIODE 2 1 POWER_DIODE
Rsnub 1 5 100.0
Csnub 5 2 0.1uF
*
SW 2 0 6 0 SWITCH
VCNTL 6 0 PULSE(0V,1V,0s,1ns,1ns,7.5us,10us)
*
L 1 3 5uH IC=4A
rL 3 4 1m
C 4 2 100uF IC=5.5V
RLOAD 4 2 1.0
*
VD 1 0 8.0V
*
.MODEL POWER_DIODE D(RS=0.01,CJO=10pF)
.MODEL SWITCH VSWITCH(ROn=0.01)
.TRAN 10us 500.0us 0s 0.2us uic
.PROBE
.END

```

(b)

Figure 4-9 PSpice simulation of circuit in Fig. 4-8.

- Schematic approach is far superior

PSpice-based Simulation


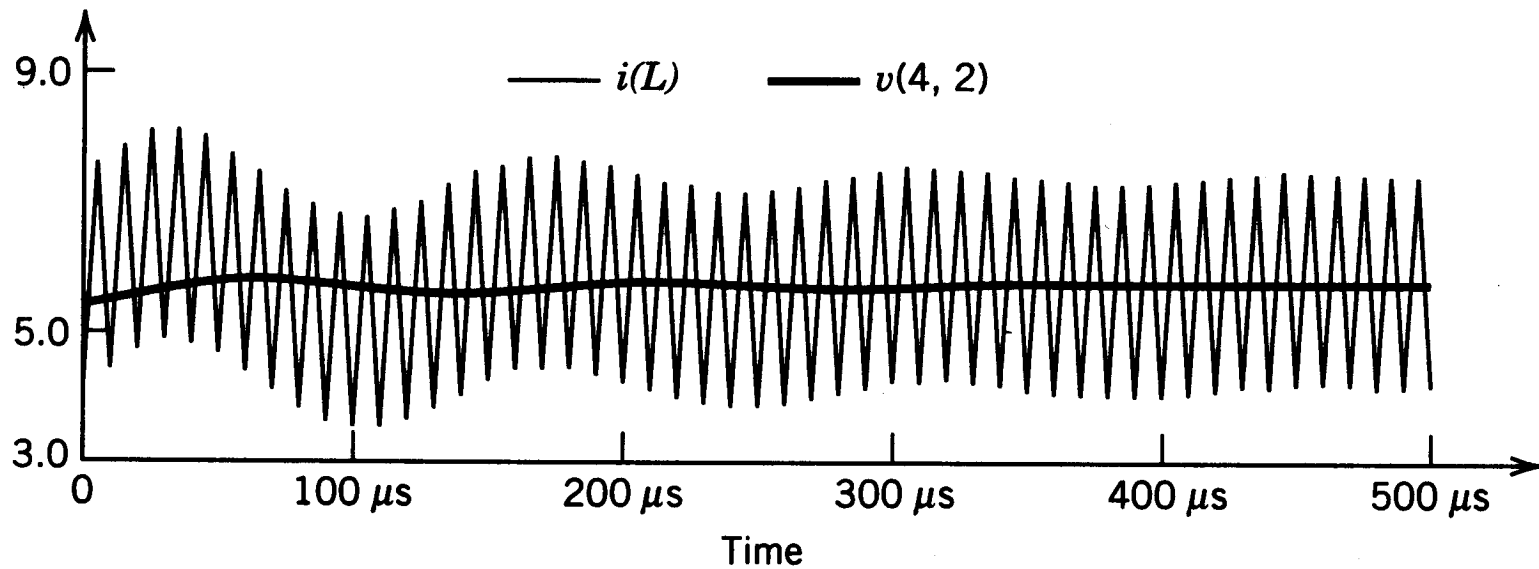


Figure 4-10 Results of PSpice simulation: i_L and v_c .

- Simulation results

Simulation using MATLAB

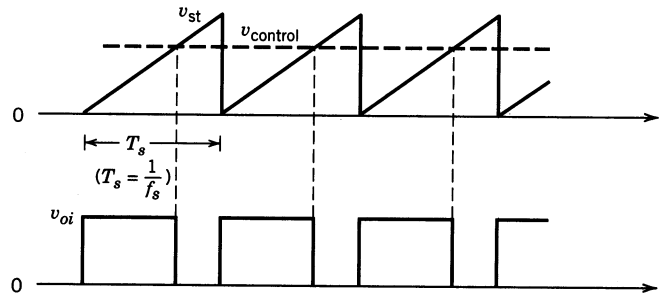

(a)

```

% Solution of the Circuit in Fig. 4-6 using Trapezoidal Method of Integration.
clc, clg, clear
% Input Data
Vd=8; L=5e-6; C=100e-6; rL=1e-3; R=1.0; fs=100e3; Vcontrol=0.75;
Ts=1/fs; tmax=50*Ts; deltat=Ts/50;
%
time= 0:deltat:tmax;
vst= time/Ts - fix(time/Ts);
voi= Vd * (Vcontrol > vst);
%
A=[-rL/L -1/L; 1/C -1/(C*R)];
b=[1/L 0]';
MN=inv(eye(2) - deltat/2 * A);
M=MN * (eye(2)+ deltat/2 * A);
N=MN * deltat/2 * b;
%
iL(1)=4.0; vC(1)=5.5;
timelength=length(time);
%
for k = 2:timelength
x = M * [iL(k-1) vC(k-1)]' + N * (voi(k) + voi(k-1));
iL(k) = x(1); vC(k) = x(2);
end
%
plot(time,iL,time,vC)
meta Example
    
```

(b)

Figure 4-11 MATLAB simulation of circuit in Fig. 4-6.

MATLAB-based Simulation

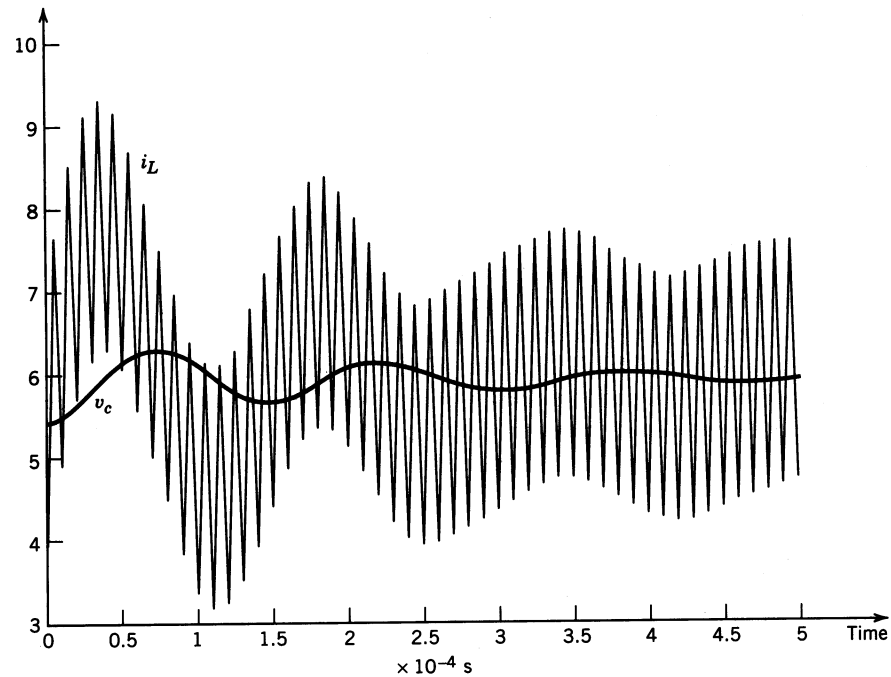


Figure 4-12 MATLAB simulation results.

- Simulation results