

Chapter 6

Thyristor Converters

Chapter 6	Line-Frequency Phase-Controlled Rectifiers and Inverters: Line-Frequency ac ↔ Controlled dc	121
6-1	Introduction	121
6-2	Thyristor Circuits and Their Control	122
6-3	Single-Phase Converters	126
6-4	Three-Phase Converters	138
6-5	Other Three-Phase Converters	153
	<i>Summary</i>	<i>153</i>
	<i>Problems</i>	<i>154</i>
	<i>References</i>	<i>157</i>
	<i>Appendix</i>	<i>158</i>

- Controlled conversion of ac into dc

Thyristor Converters

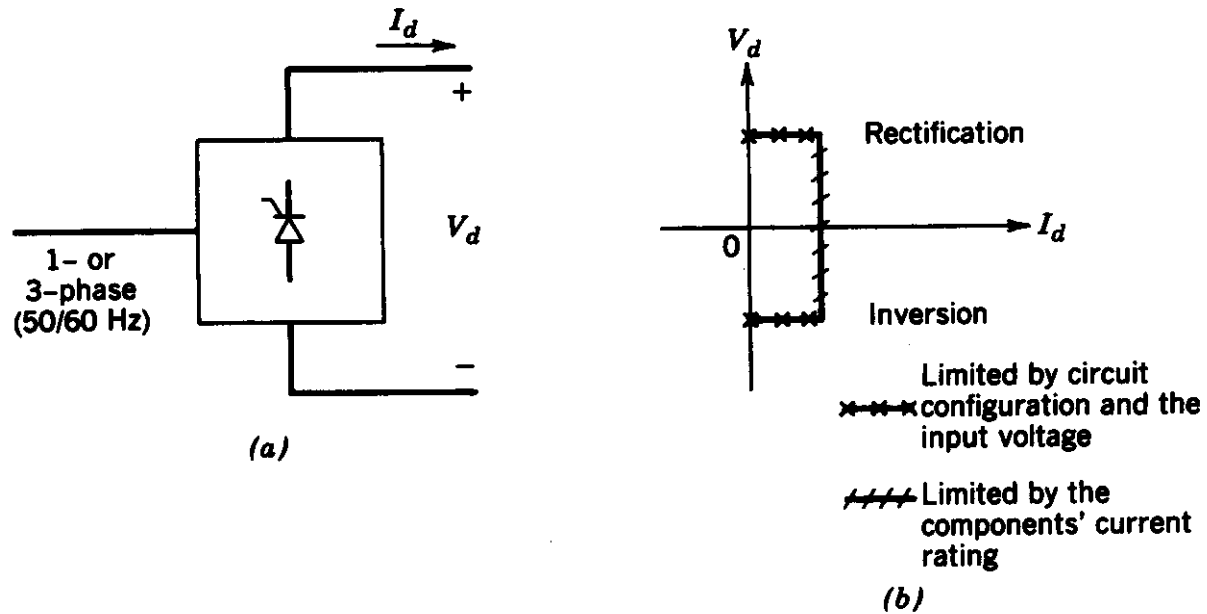


Figure 6-1 Line-frequency controlled converter.

- Two-quadrant conversion

Primitive circuits with thyristors

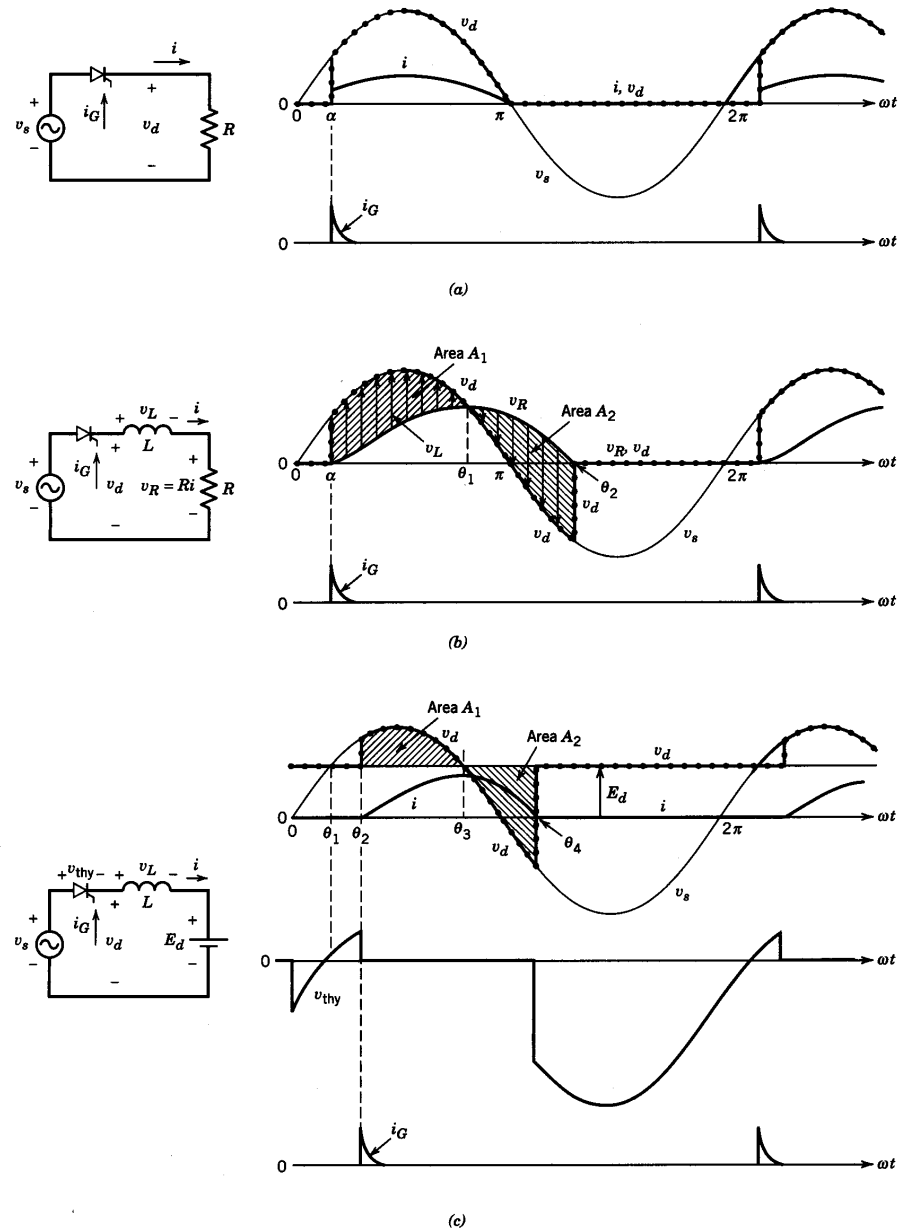


Figure 6-2 Basic thyristor converters.

Thyristor Triggering

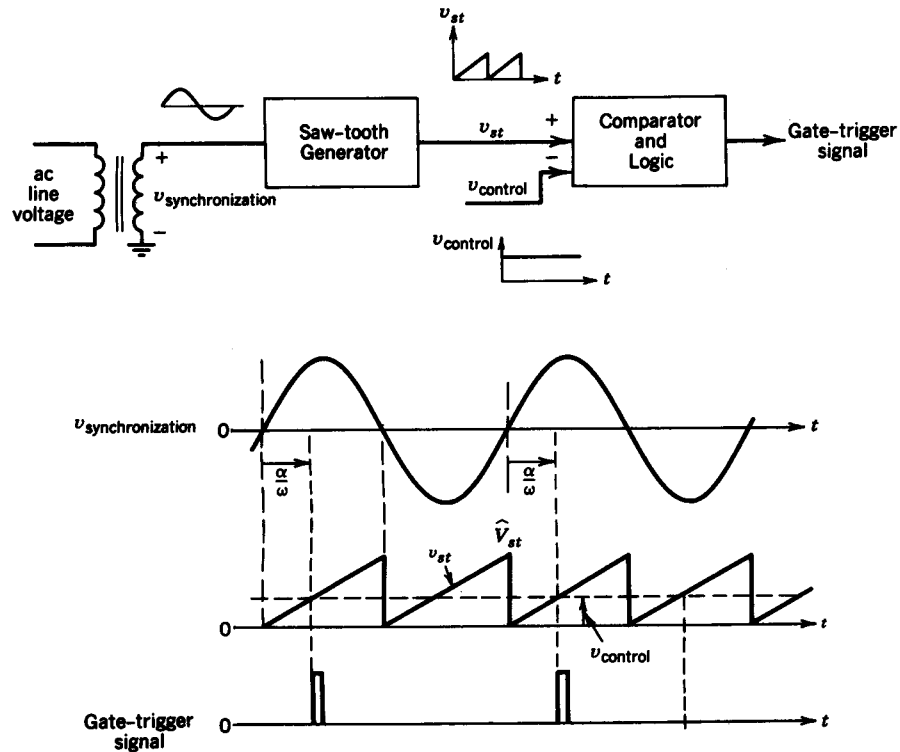


Figure 6-3 Gate trigger control circuit.

- ICs available

Full-Bridge Thyristor Converters

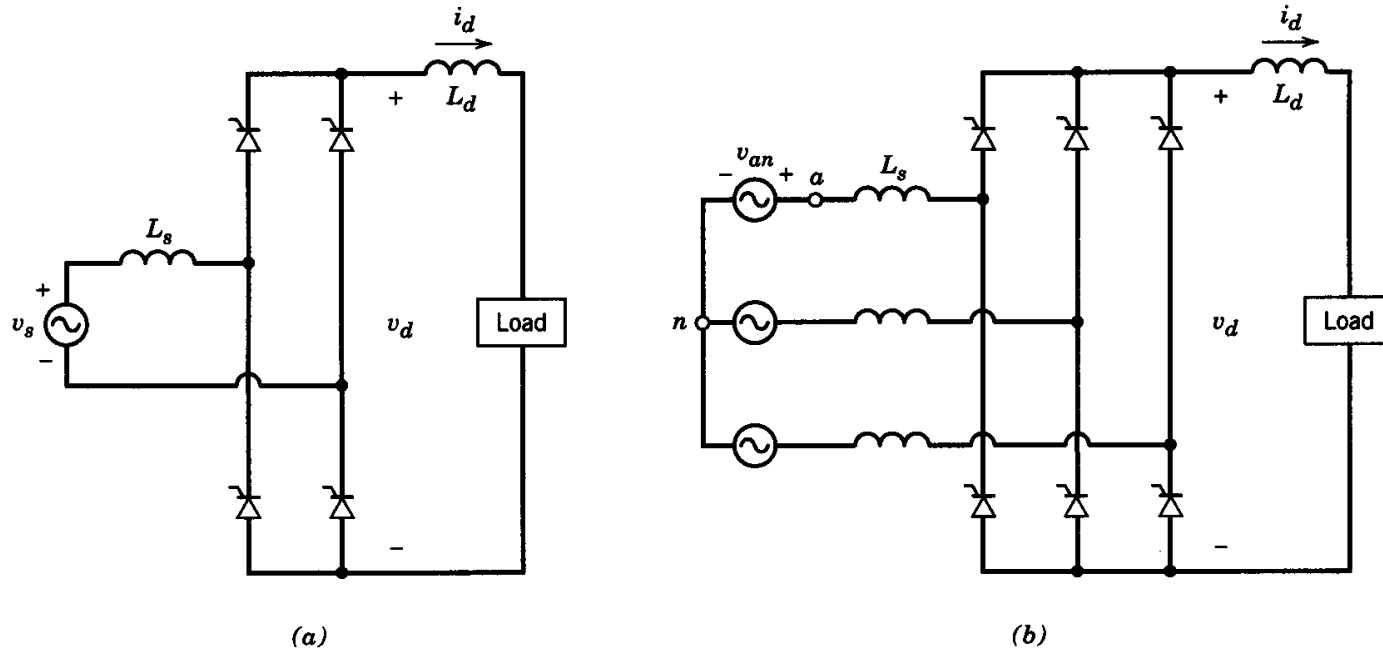


Figure 6-4 Practical thyristor converters.

- Single-phase and three-phase

Single-Phase Thyristor Converters

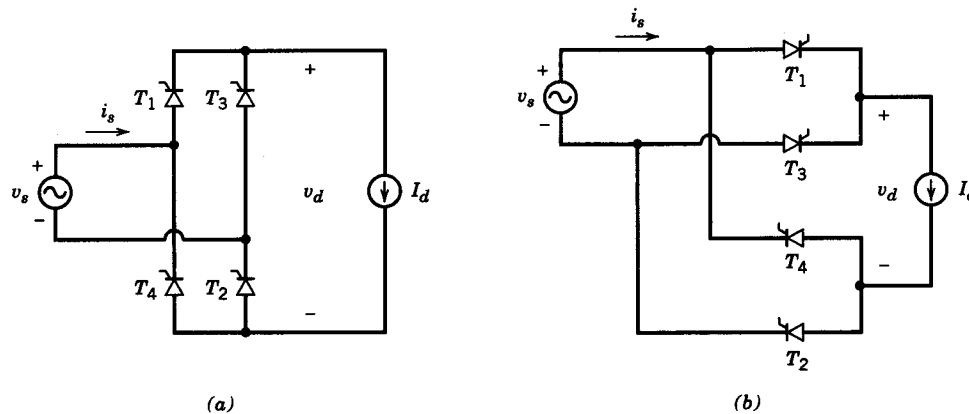


Figure 6-5 Single-phase thyristor converter with $L_s = 0$ and a constant dc current.

- Two groups with two thyristor each

1-Phase Thyristor Converter Waveforms

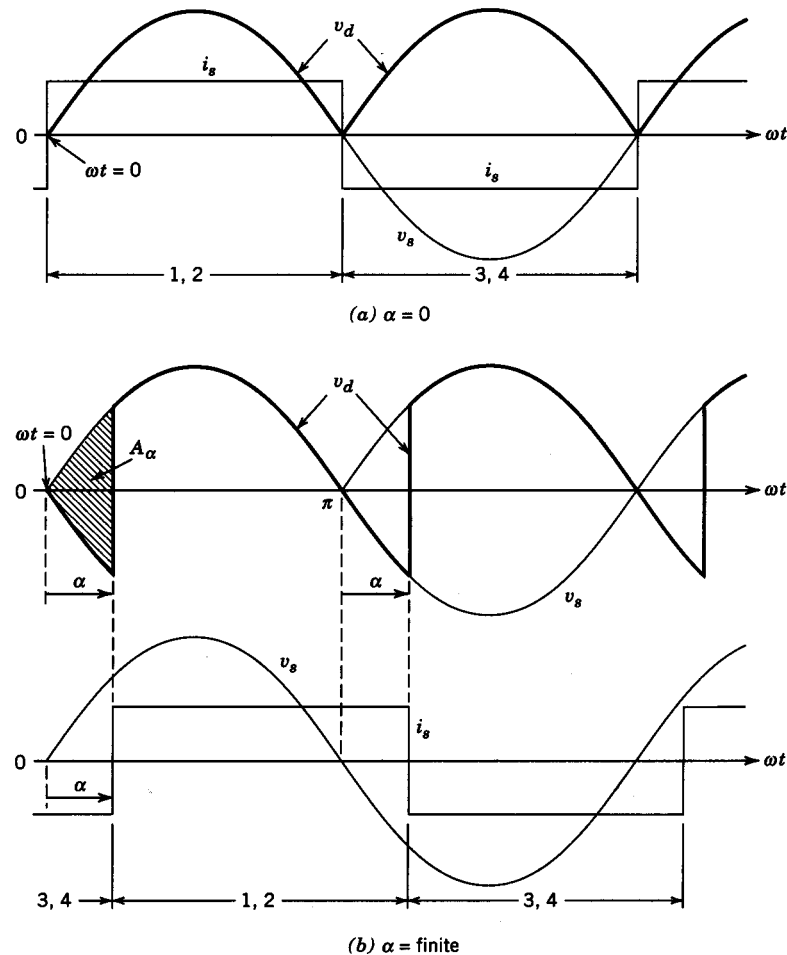


Figure 6-6 Waveforms in the converter of Fig. 6-5.

- Assuming zero ac-side inductance

Average DC Output Voltage

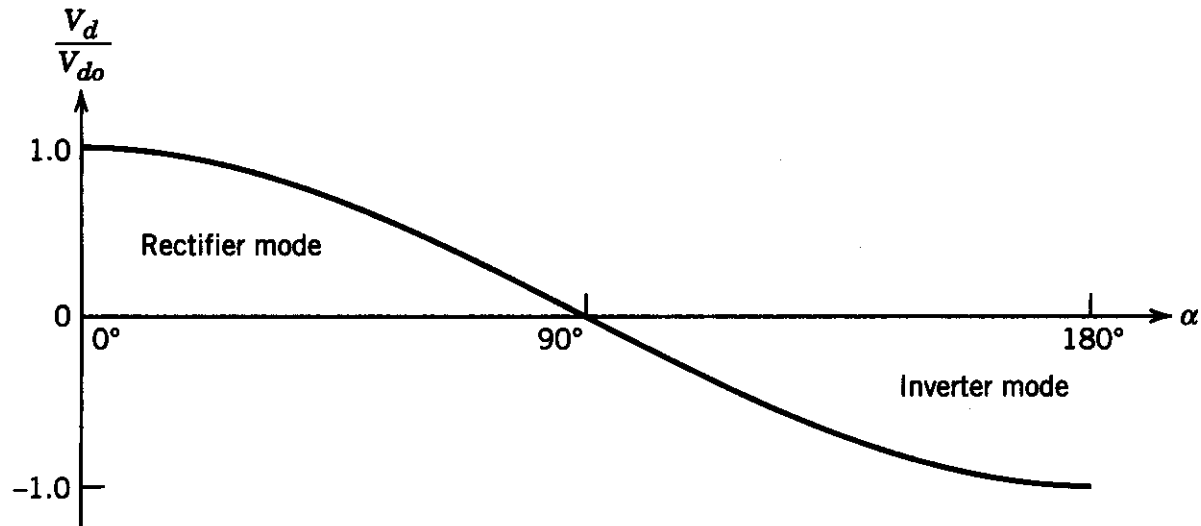


Figure 6-7 Normalized V_d as a function of α .

- Assuming zero ac-side inductance

Input Line-Current Waveforms

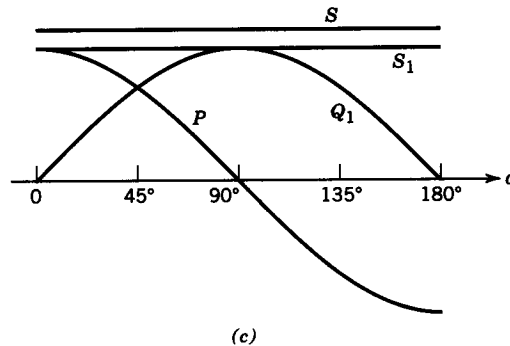
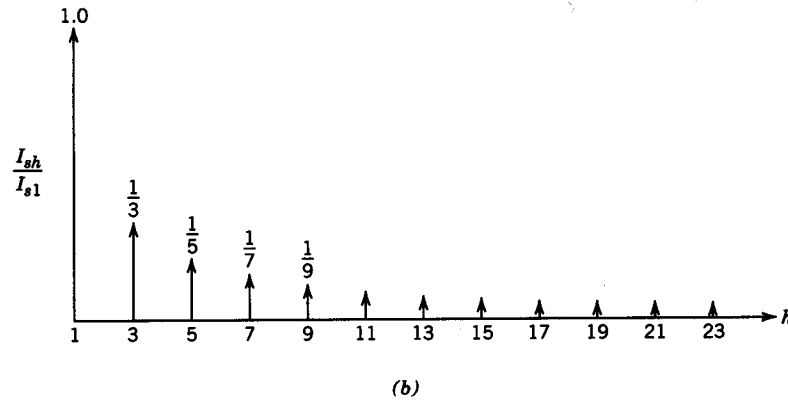
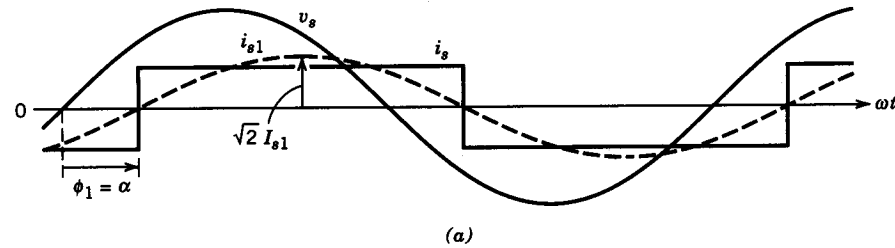


Figure 6-8 The ac-side quantities in the converter of Fig. 6-5.

- Harmonics, power and reactive power

1-Phase Thyristor Converter

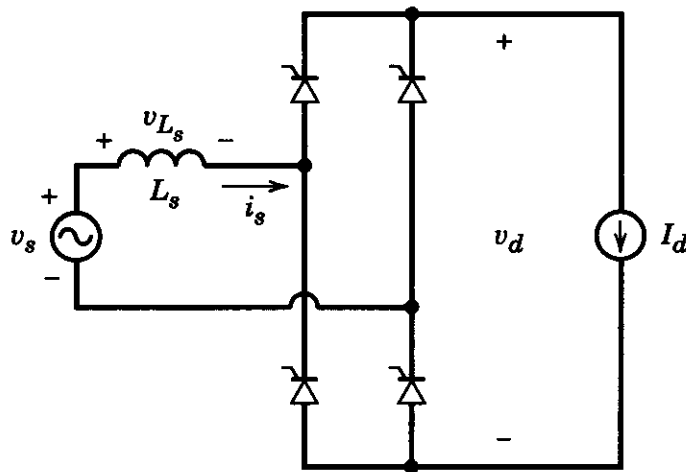


Figure 6-9 Single-phase thyristor converter with a finite L_s and a constant dc current.

- Finite ac-side inductance; constant dc output current

Thyristor Converter Waveforms

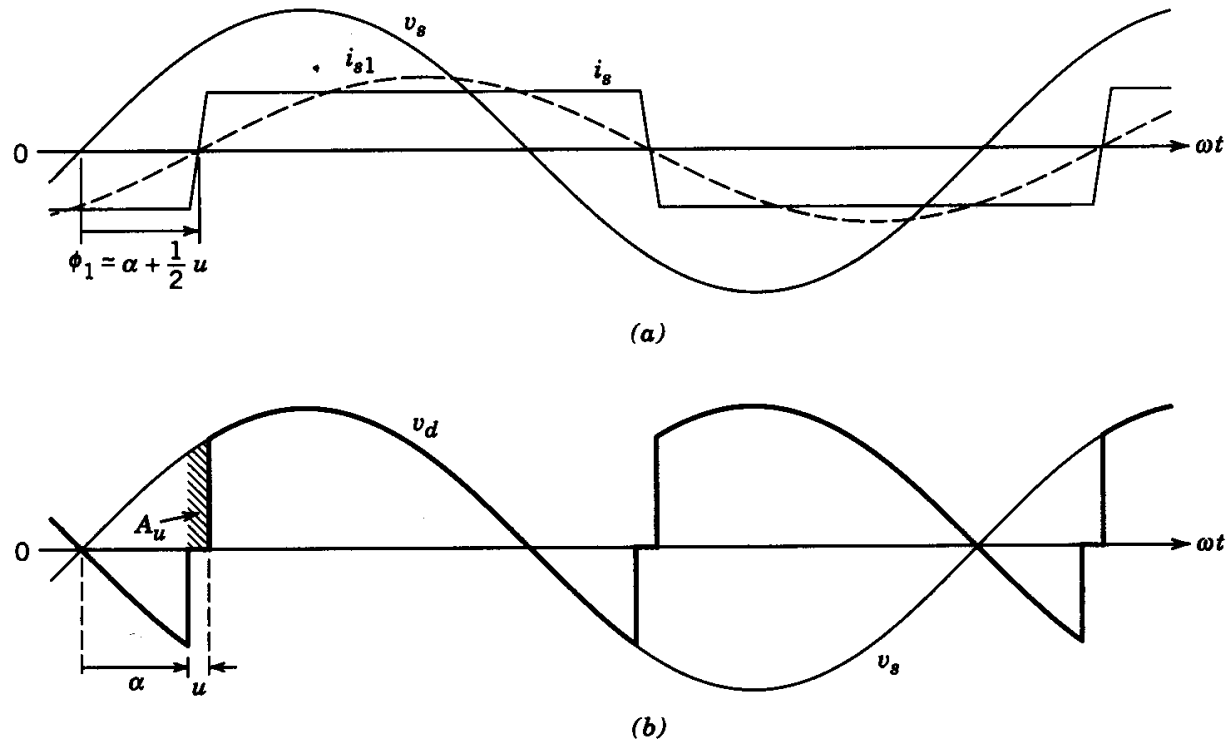


Figure 6-10 Waveforms in the converter of Fig. 6-9.

- Finite ac-side inductance

Thyristor Converter: Discontinuous Mode

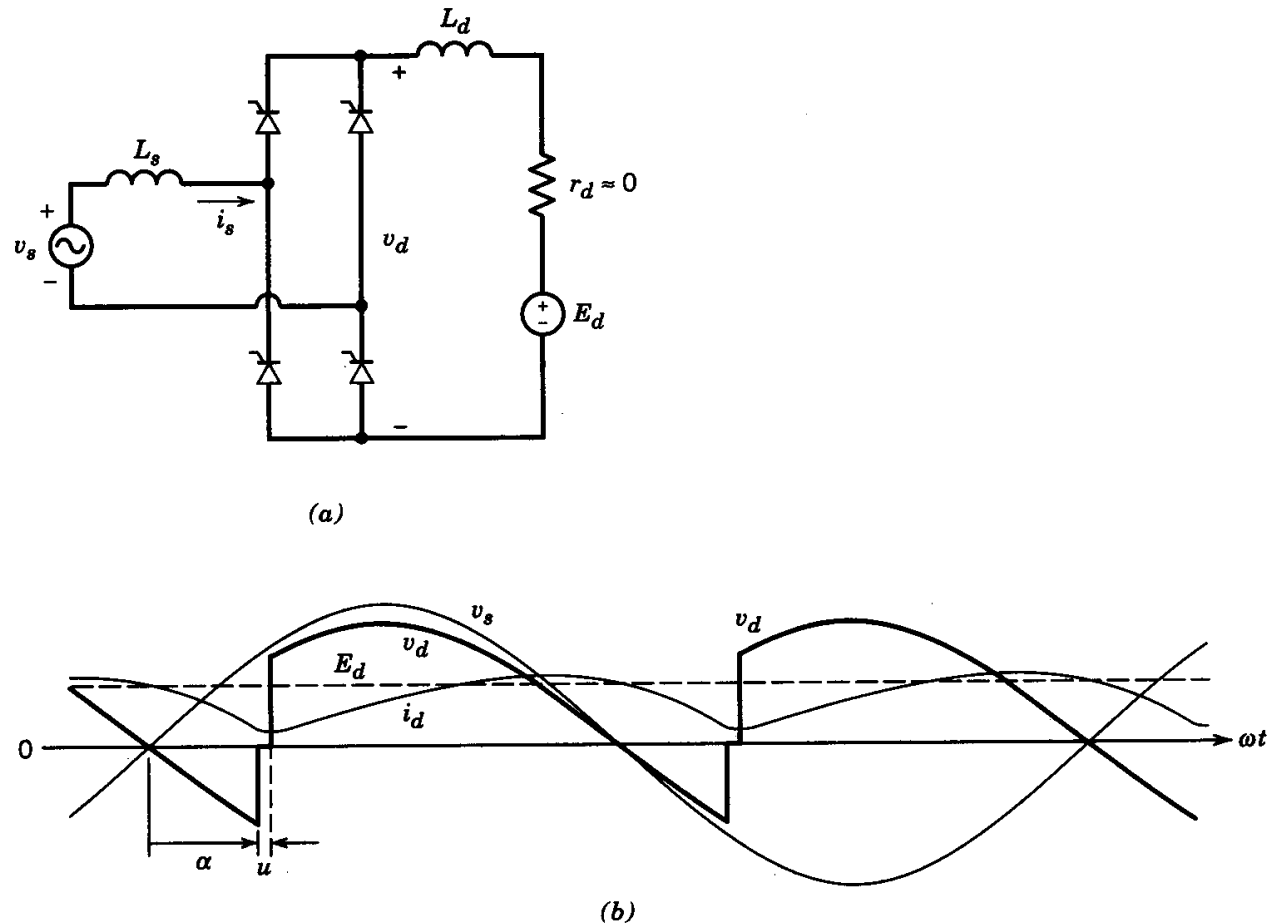


Figure 6-11 (a) A practical thyristor converter. (b) Waveforms.

- This mode can occur in a dc-drive at light loads

Thyristor Converter Waveforms

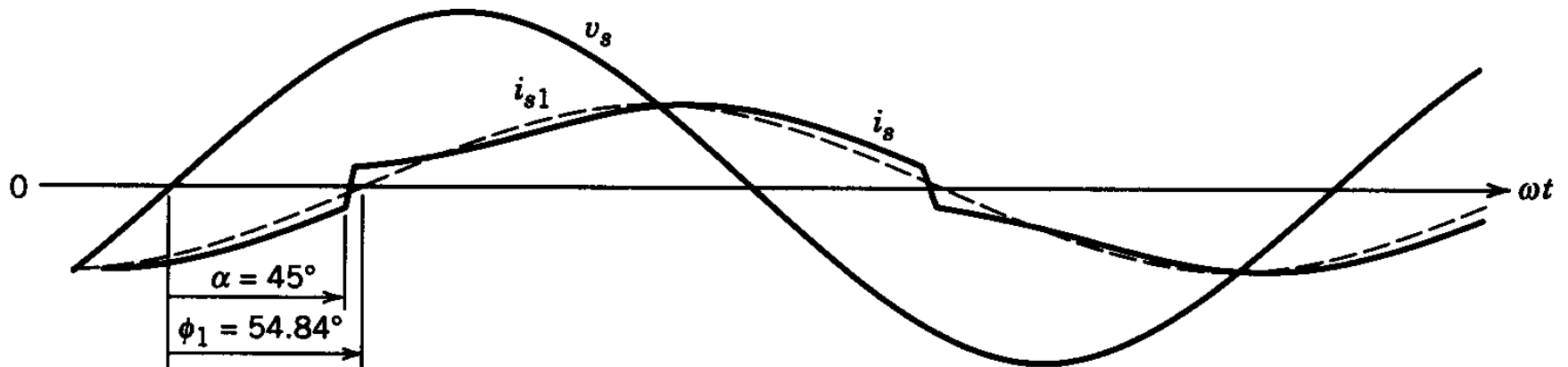


Figure 6-12 Waveforms in Example 6-2 for the circuit of Fig. 6-11a.

- PSpice-based simulation

Thyristor Converter Waveforms: Discontinuous Conduction Mode

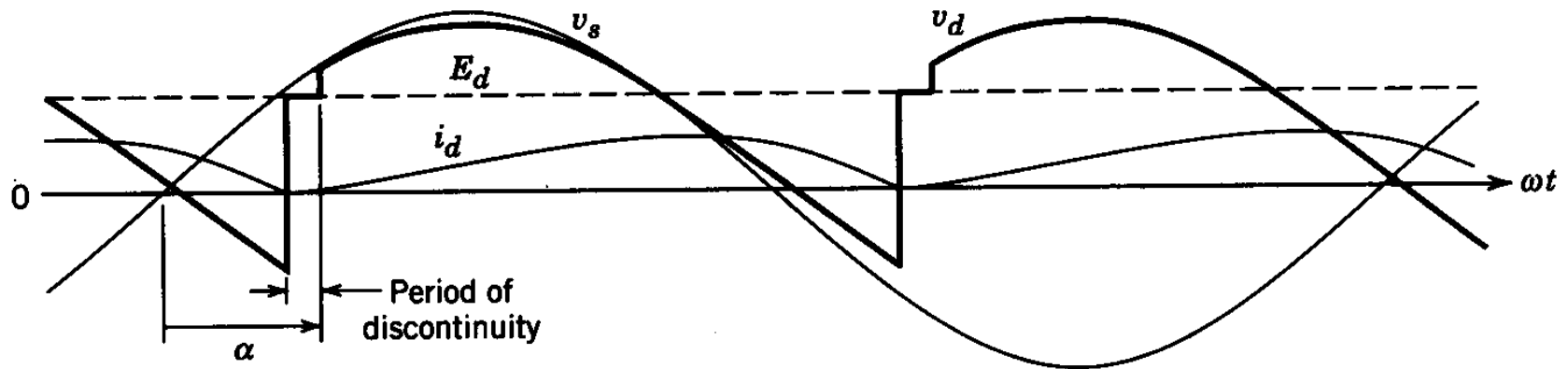


Figure 6-13 Waveforms in a discontinuous-current-conduction mode.

- PSpice-based simulation

DC Voltage versus Load Current


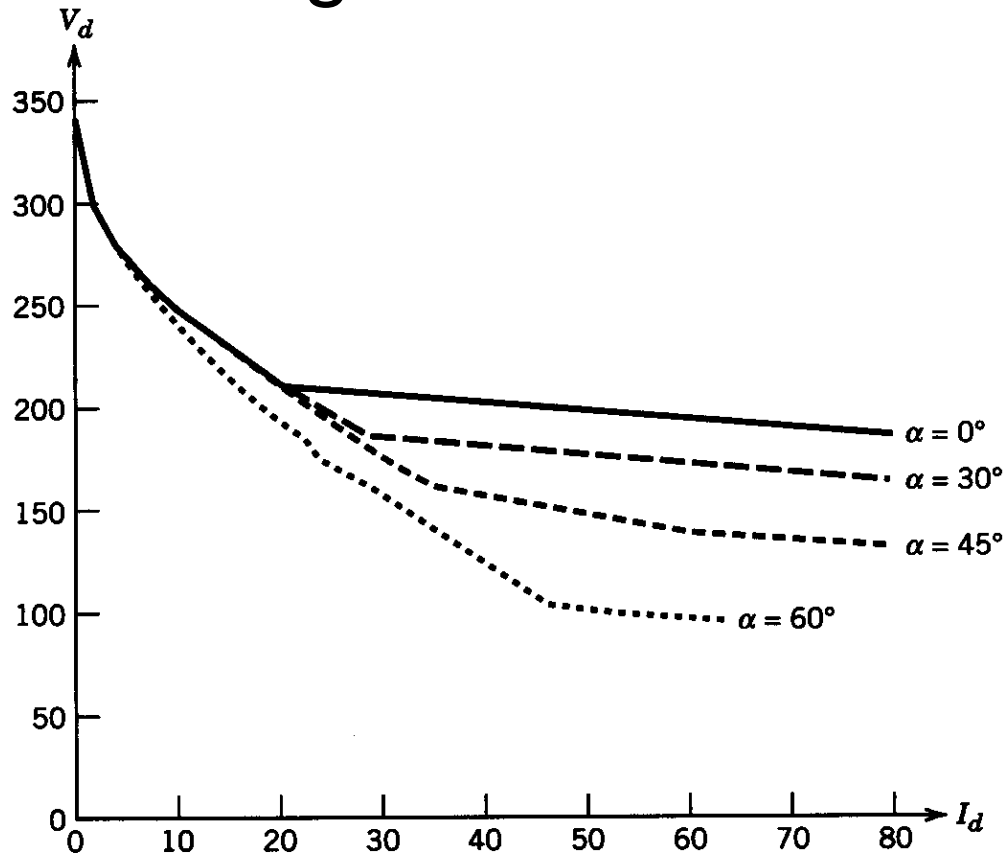



Figure 6-14 V_d versus I_d in the single-phase thyristor converter of Fig. 6-11a.

- Various values of delay angle

Thyristor Converters: Inverter Mode

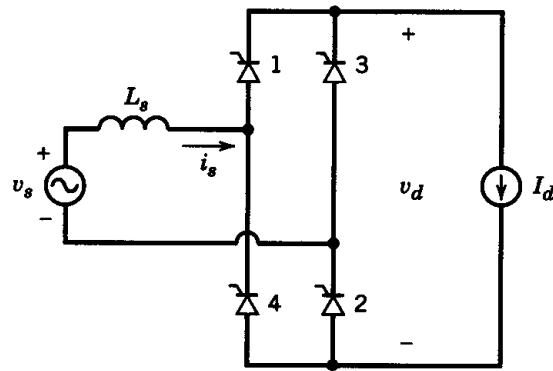

(a)

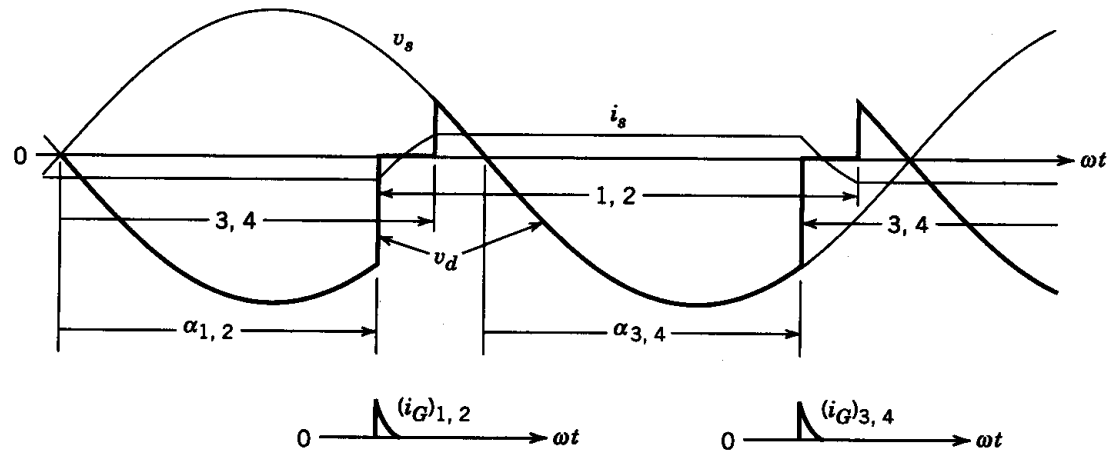

(b)

Figure 6-15 (a) Inverter, assuming a constant dc current. (b) Waveforms.

- Assuming the ac-side inductance to be zero

Thyristor Converters: Inverter Mode

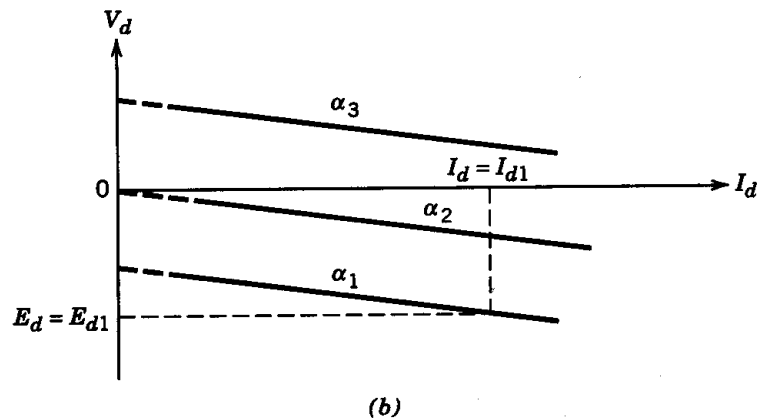
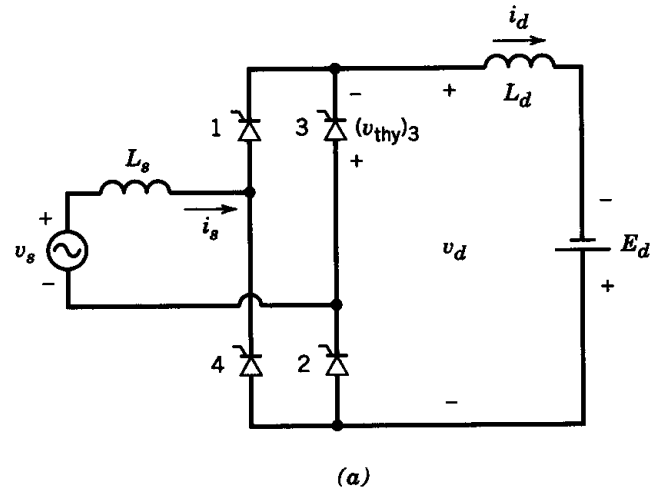


Figure 6-16 (a) Thyristor inverter with a dc voltage source. (b) V_d versus I_d .

- Family of curves at various values of delay angle

Thyristor Converters: Inverter Mode

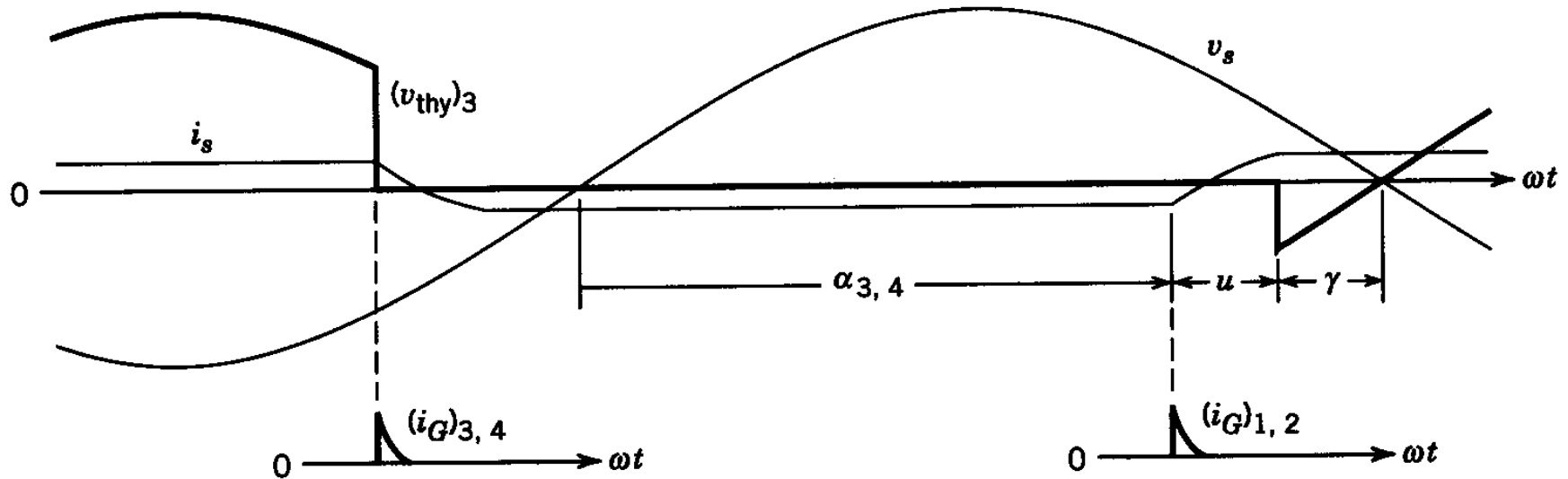


Figure 6-17 Voltage across a thyristor in the inverter mode.

- Importance of extinction angle in inverter mode

Thyristor Converters: Inverter Mode

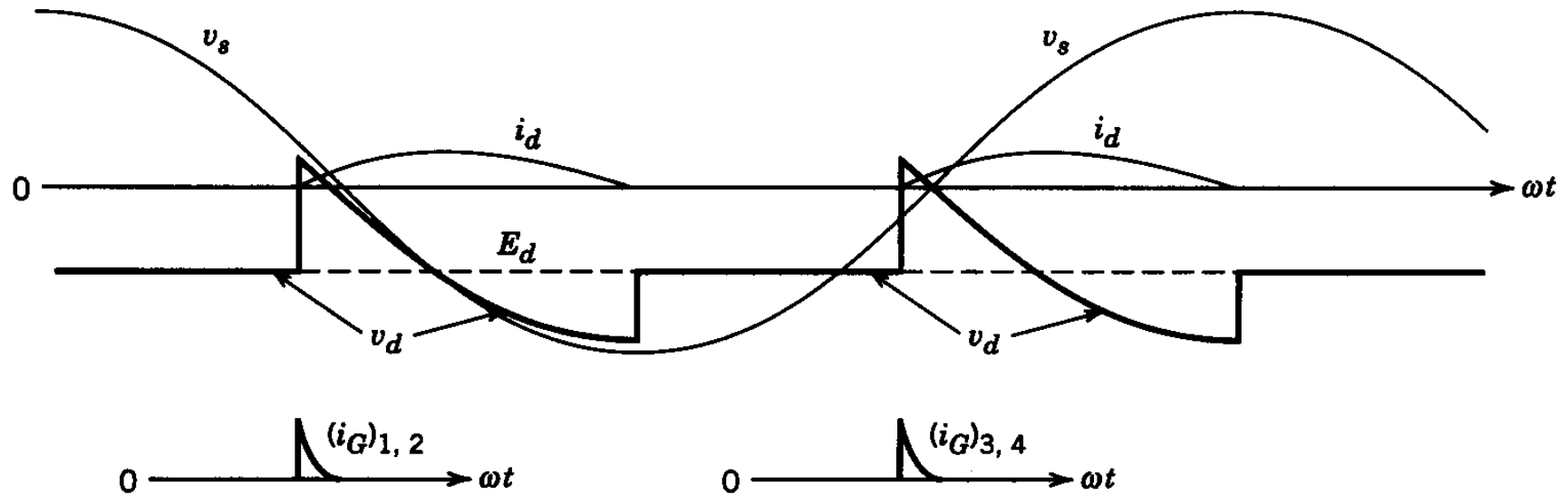


Figure 6-18 Waveforms at inverter start-up.

- Waveforms at start-up

3-Phase Thyristor Converters

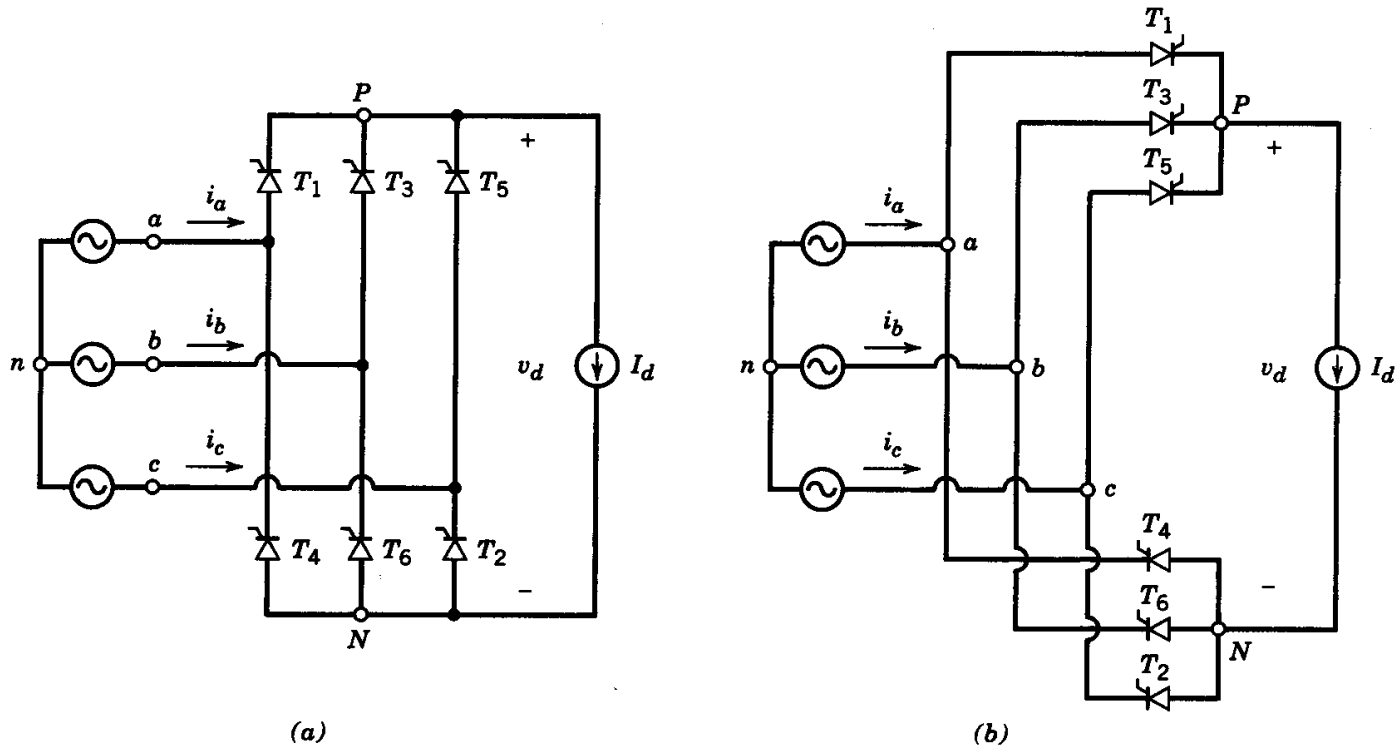


Figure 6-19 Three-phase thyristor converter with $L_s = 0$ and a constant dc current.

- Two groups of three thyristors each

3-Phase Thyristor Converter Waveforms

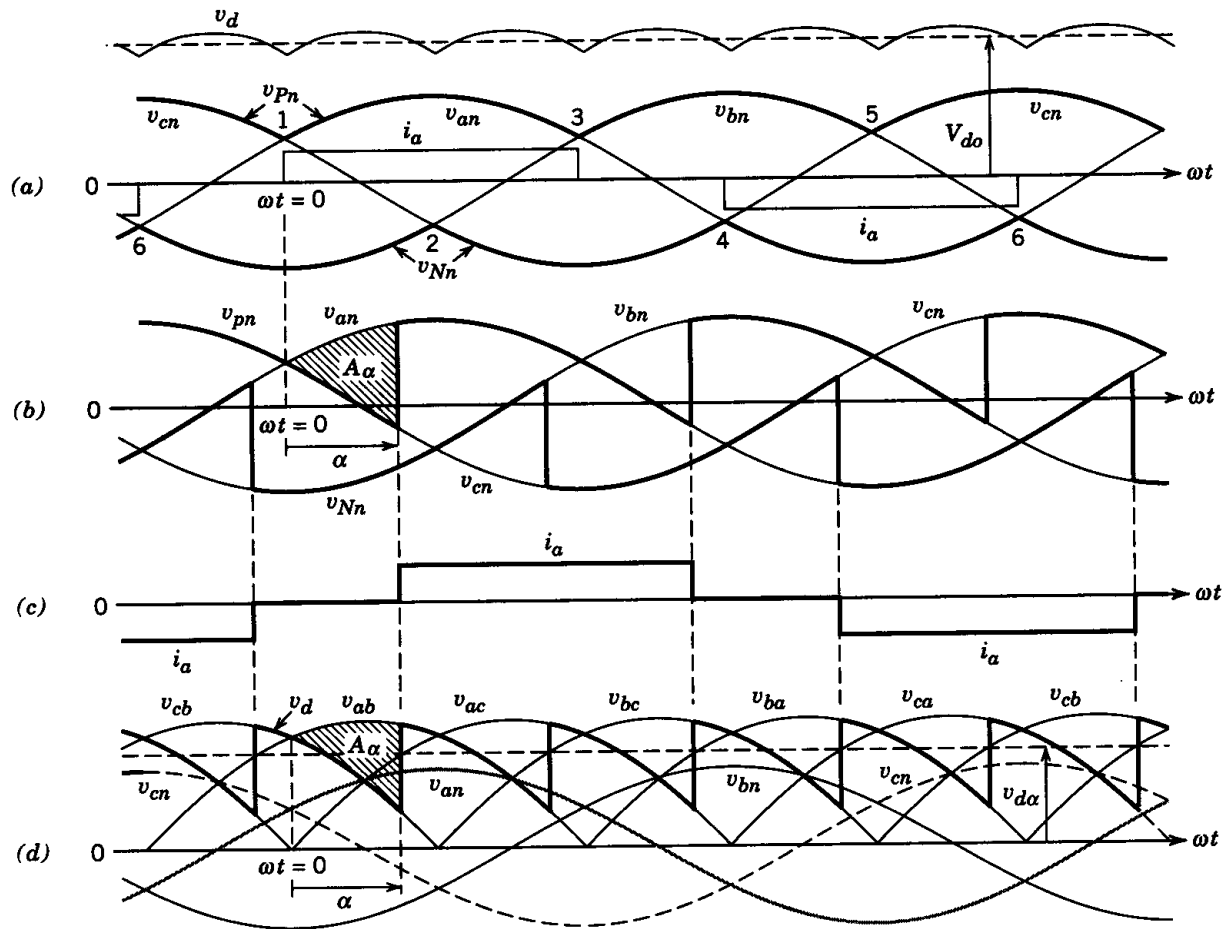


Figure 6-20 Waveforms in the converter of Fig. 6-19.

- Zero ac-side inductance; purely dc current

DC-side voltage waveforms assuming zero ac-side inductance

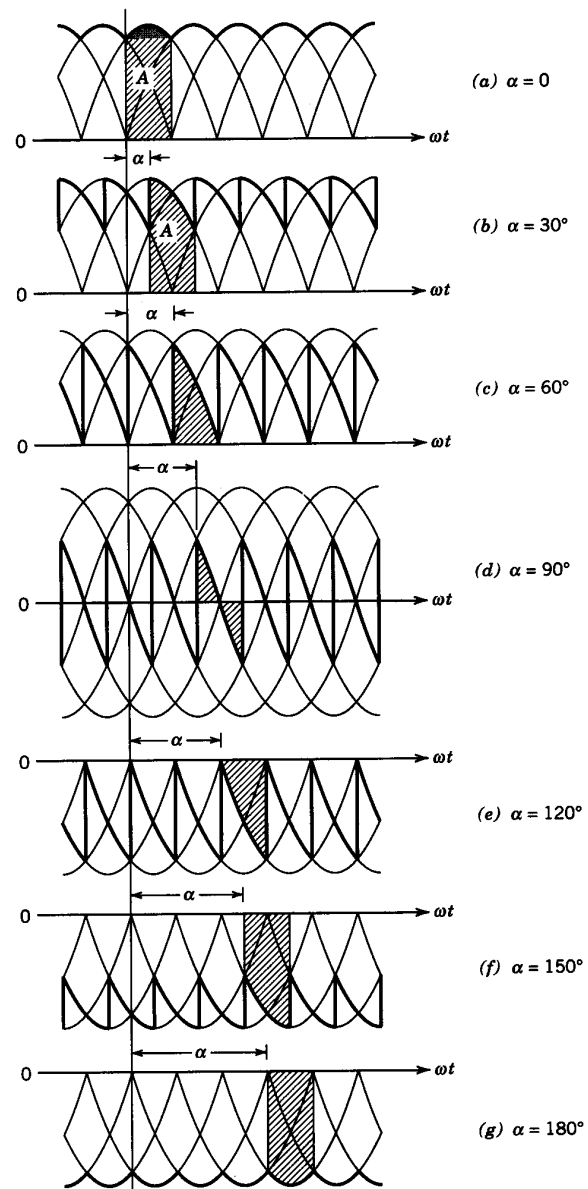


Figure 6-21 The dc-side voltage waveforms as a function of α where $V_{d\alpha} = A/(\pi/3)$. (From ref. 2 with permission.)

Input Line-Current Waveform

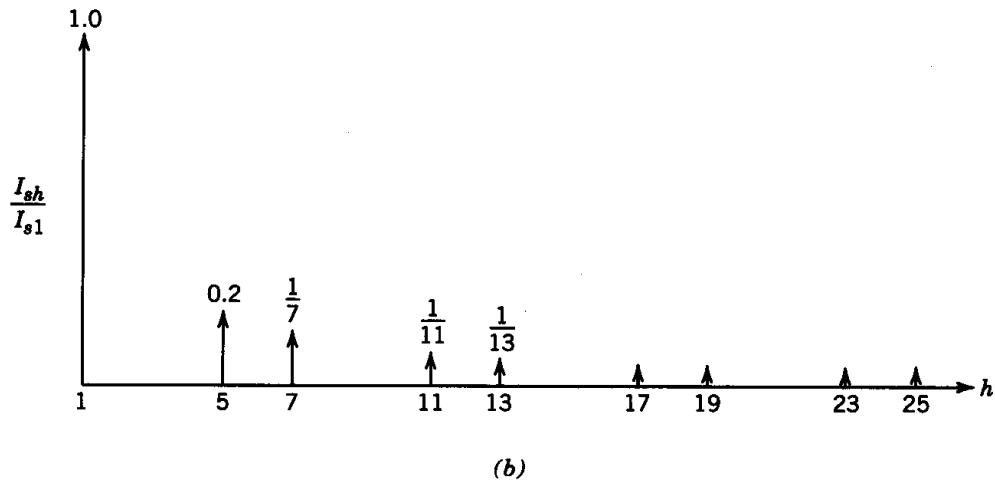
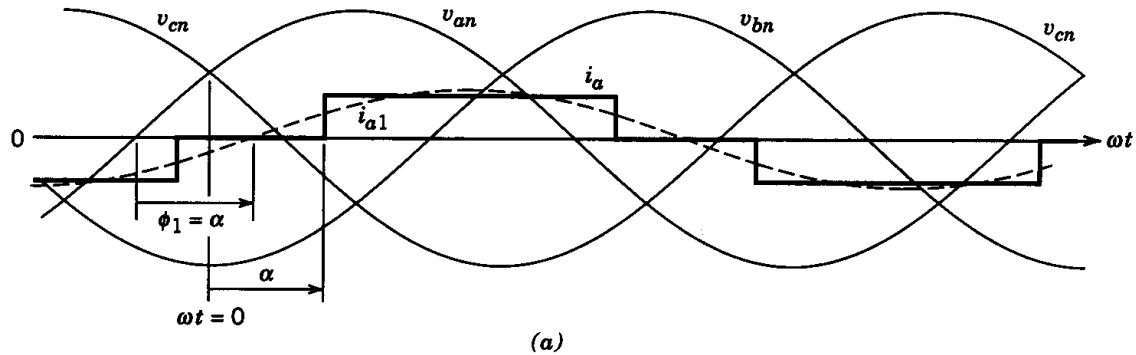


Figure 6-22 Line current in a three-phase thyristor converter of Fig. 6-19.

- Zero ac-side inductance

Input line-current waveforms assuming zero ac-side inductance

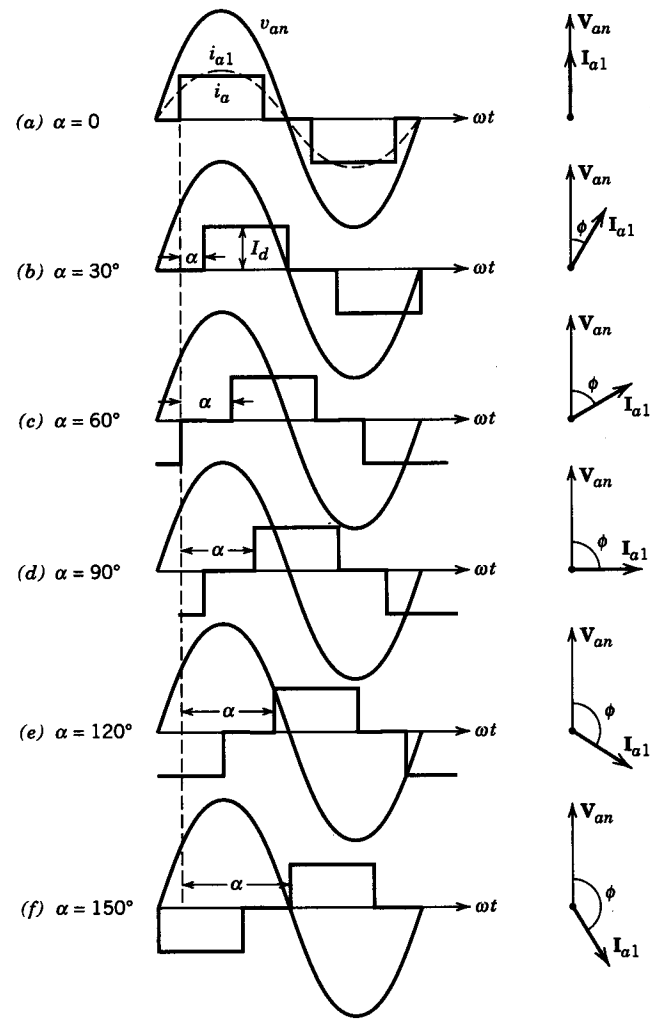


Figure 6-23 Line current as a function of α . (With permission from ref. 2.)

Three-Phase Thyristor Converter

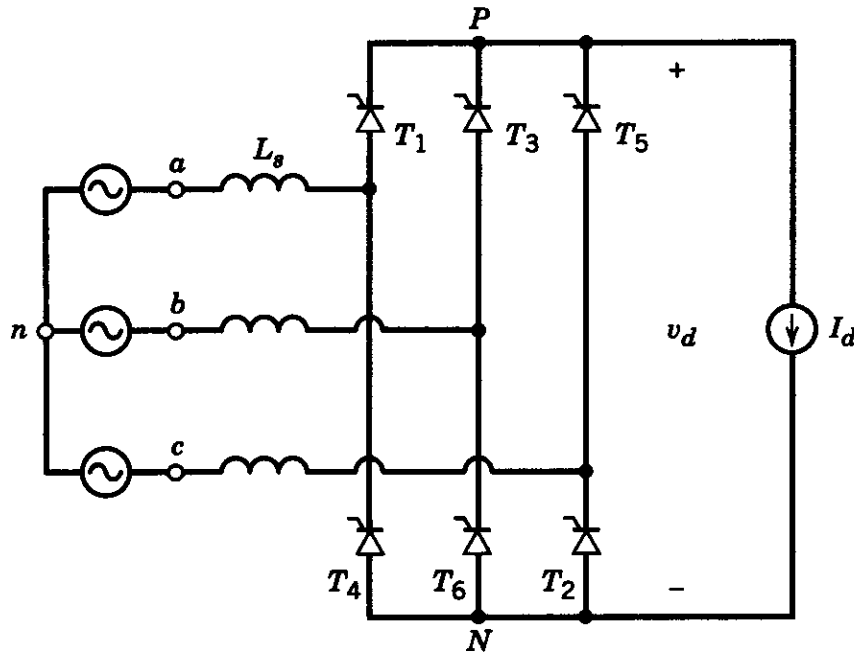


Figure 6-24 Three-phase converter with L_s and a constant dc current.

- AC-side inductance is included

Current Commutation Waveforms

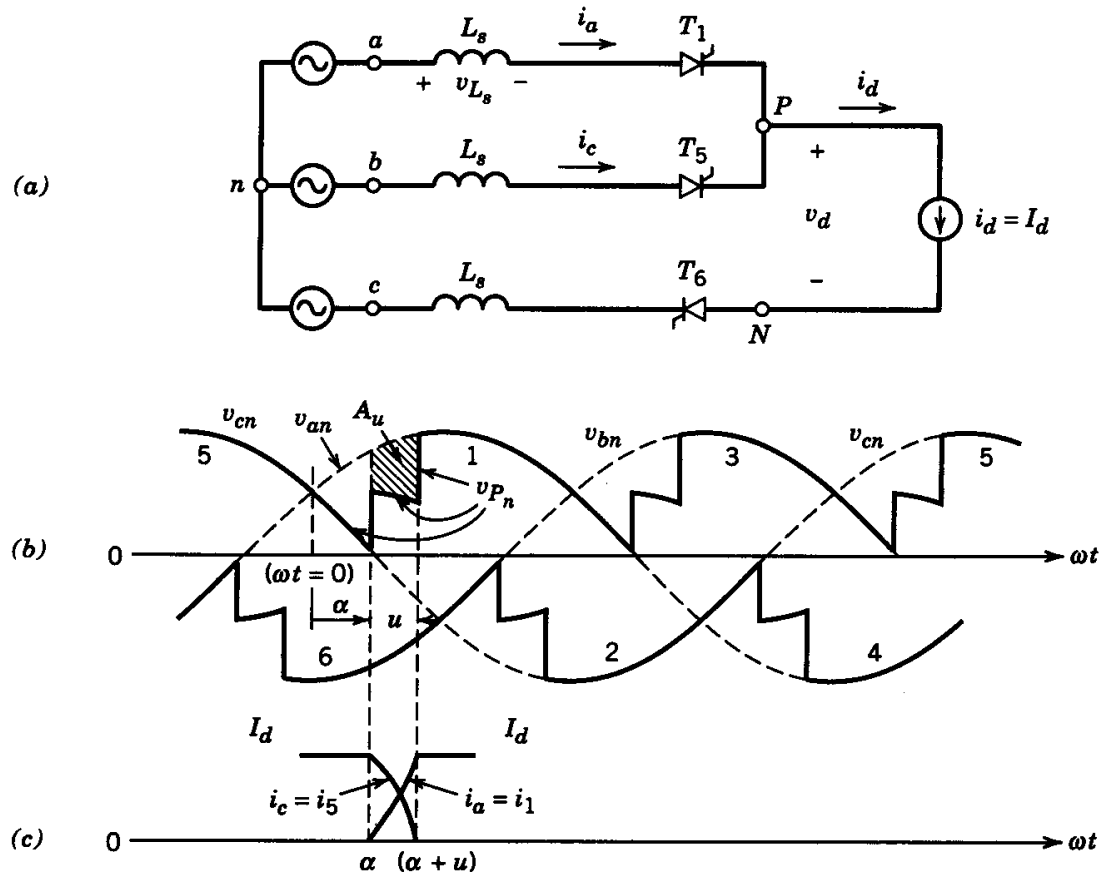


Figure 6-25 Commutation in the presence of L_s .

- Constant dc-side current

Input Line-Current Waveform

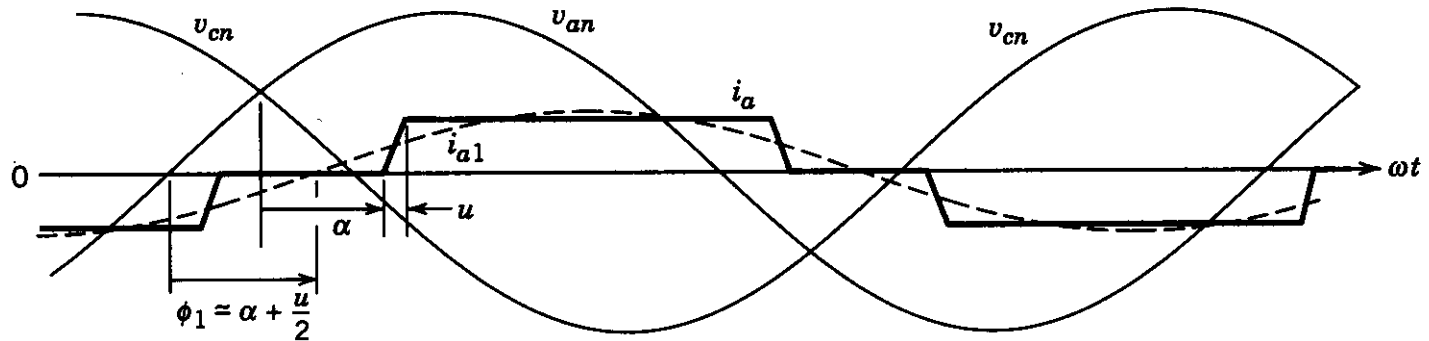


Figure 6-26 Line current in the presence of L_s .

- Finite ac-side inductance

Input Line-Current Harmonics

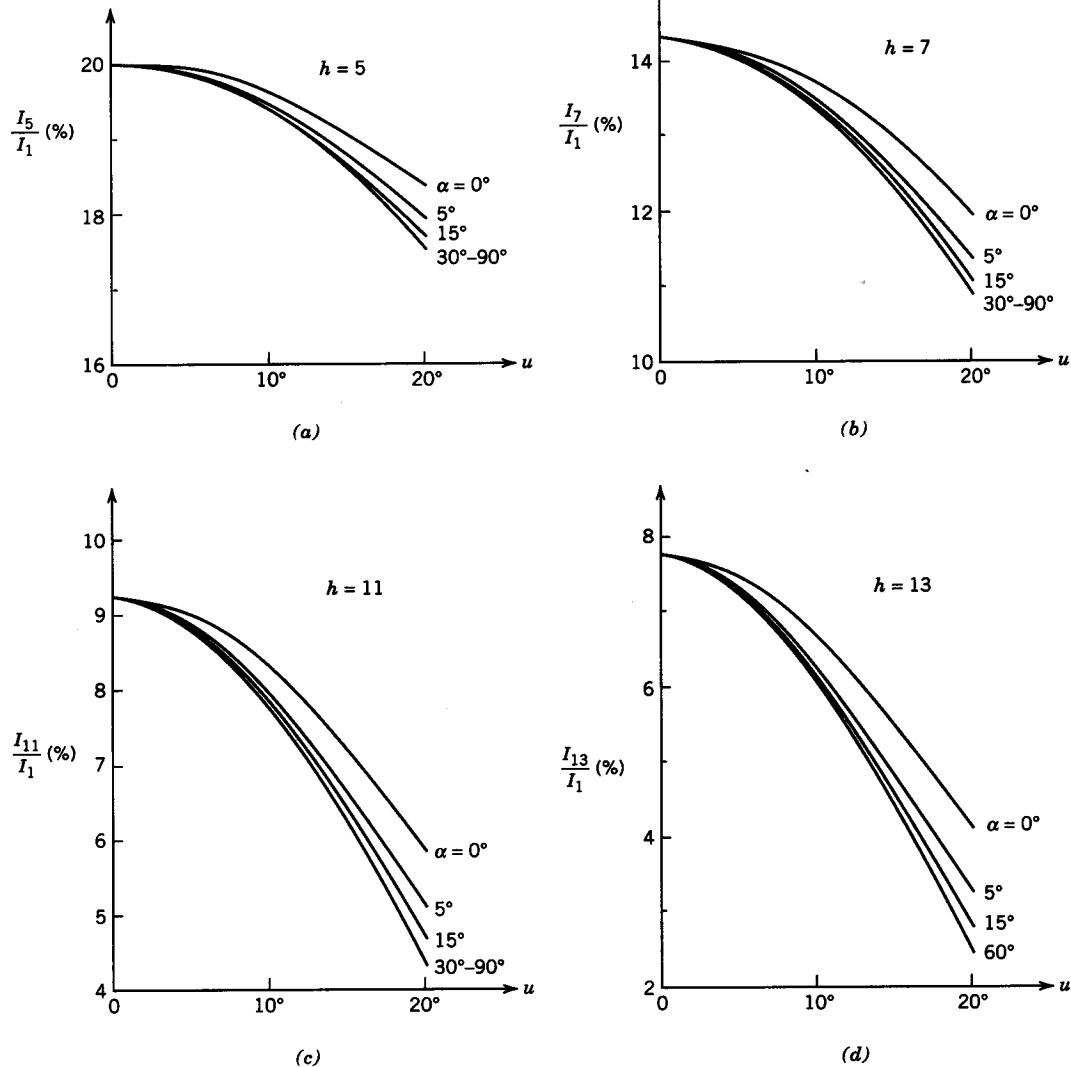


Figure 6-27 Normalized harmonic currents in the presence of L_s . (With permission from ref. 2).

- Finite ac-side inductance

Input Line-Current Harmonics

Table 6-1 Typical and Idealized Harmonics

	<i>h</i>	5	7	11	13	17	19	23	25
Typical	I_h/I_1	0.17	0.10	0.04	0.03	0.02	0.01	0.01	0.01
Idealized	I_h/I_1	0.20	0.14	0.09	0.07	0.06	0.05	0.04	0.04

- Typical and idealized

Three-Phase Thyristor Converter

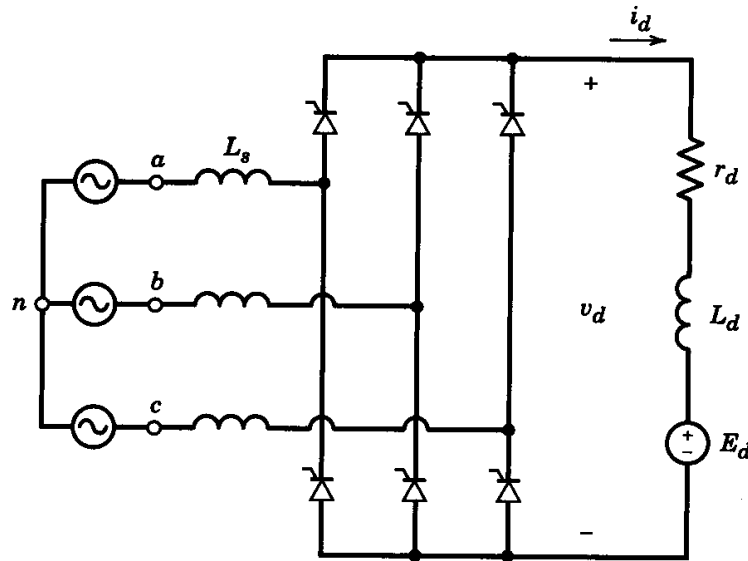


Figure 6-28 A practical thyristor converter.

- Realistic load

Thyristor Converter Waveforms

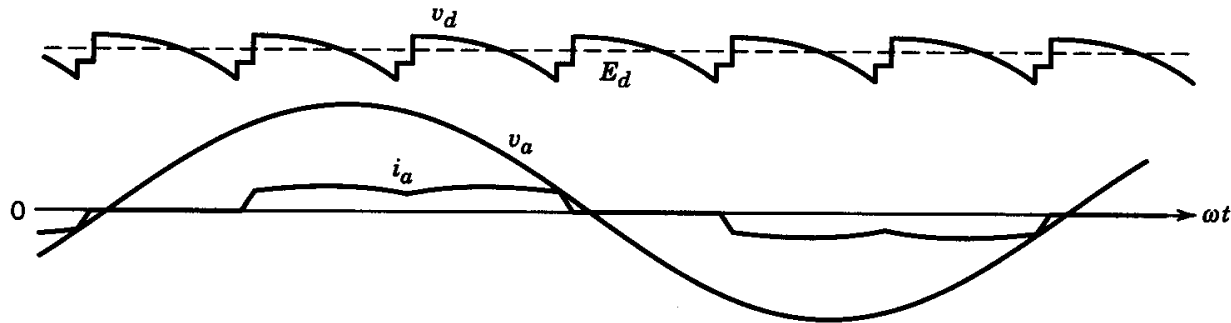


Figure 6-29 Waveforms in the converter of Fig. 6-28. ■

- Realistic load; continuous-conduction mode

Thyristor Converter Waveforms

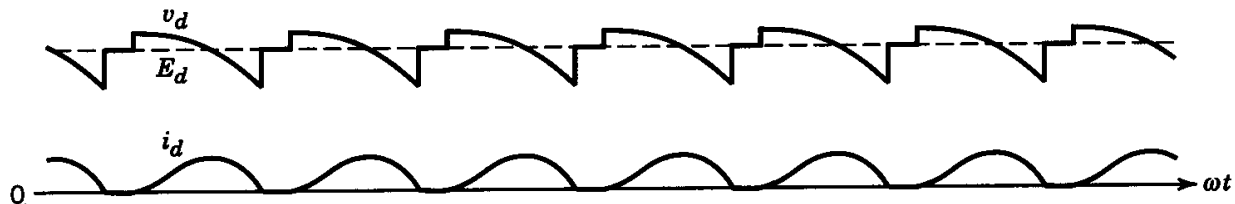


Figure 6-30 Waveforms in a discontinuous-current-conduction mode.

- Realistic load; discontinuous-conduction mode

Thyristor Inverter

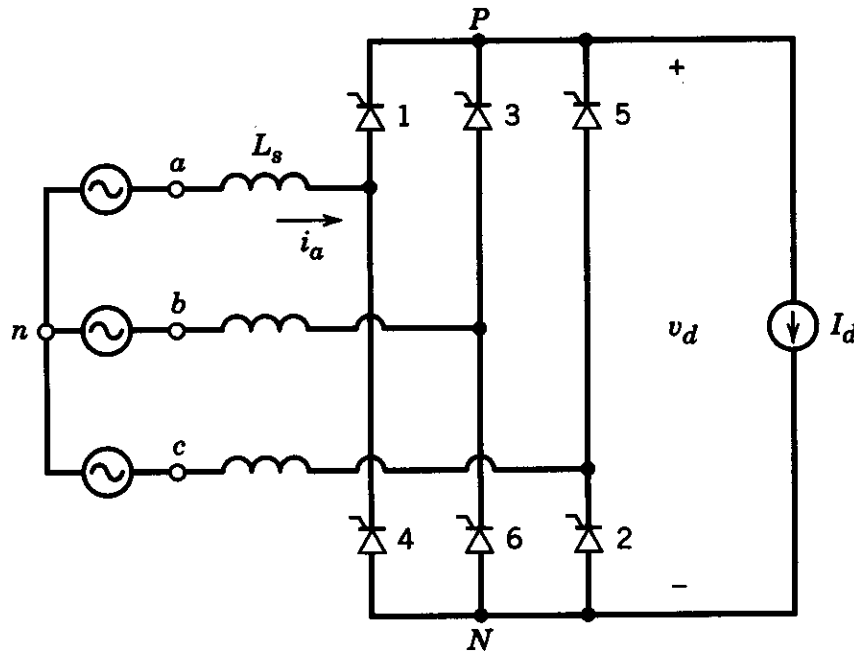


Figure 6-31 Inverter with a constant dc current.

- Constant dc current

Thyristor Inverter Waveforms

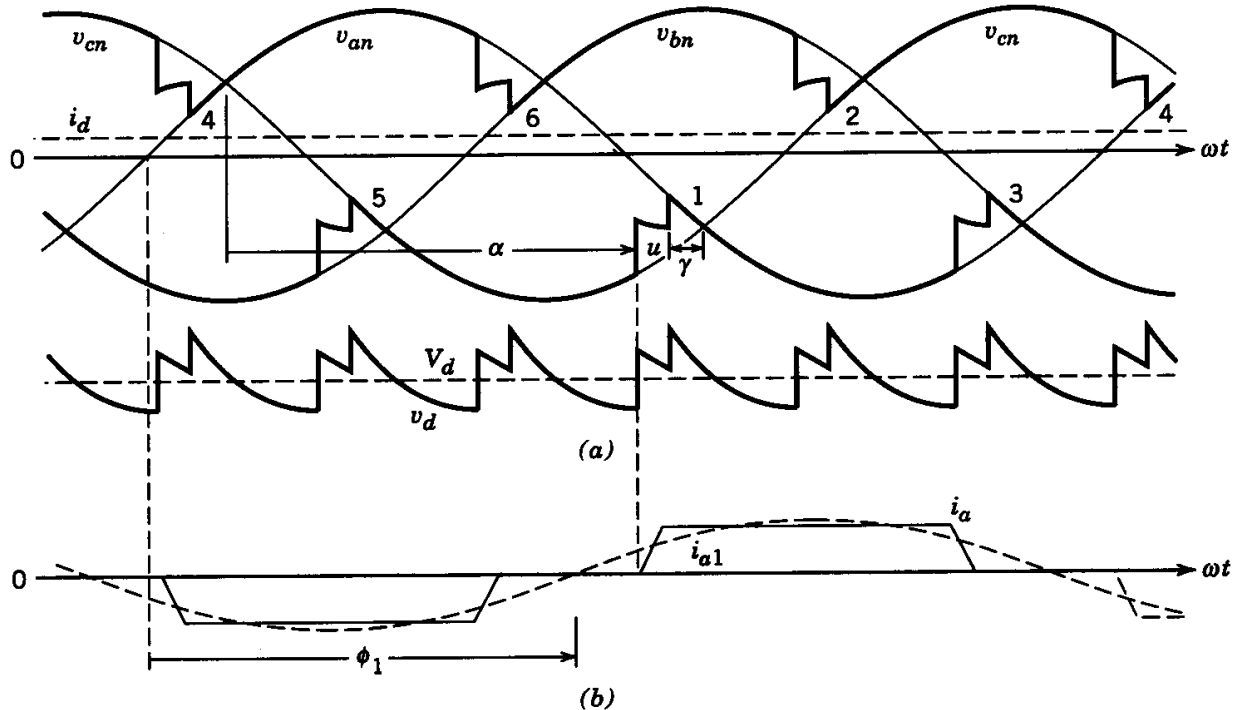


Figure 6-32 Waveforms in the inverter of Fig. 6-31.

- Finite ac-side inductance

Thyristor Inverter

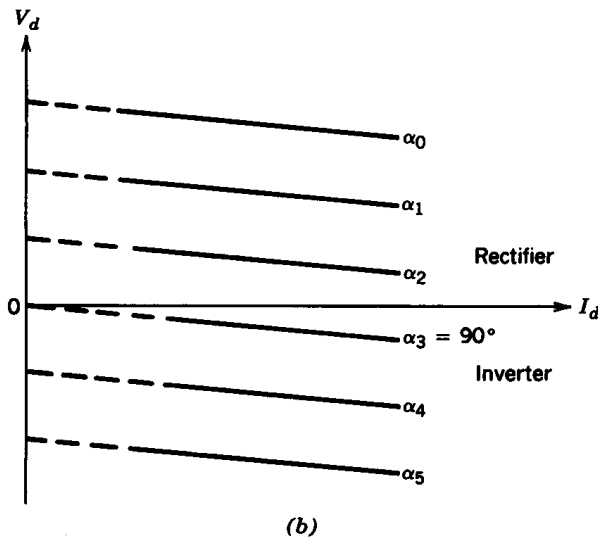
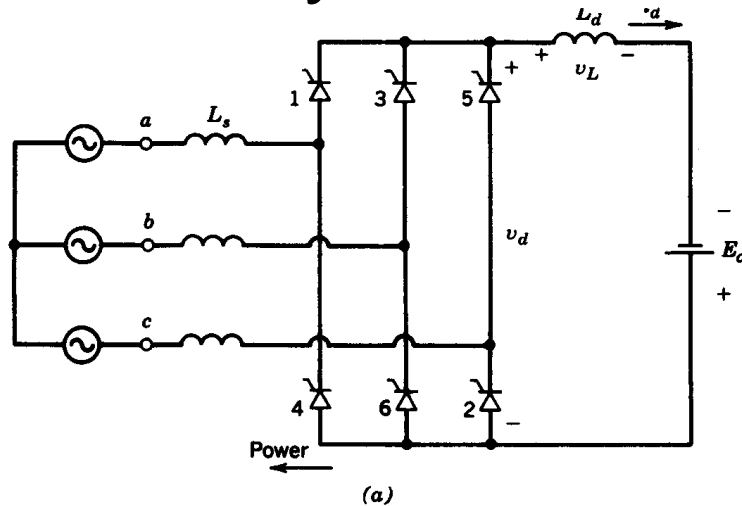


Figure 6-33 (a) Thyristor inverter with a dc voltage source.
(b) V_d versus I_d .

- Family of curves at various values of delay angle

Thyristor Inverter Operation

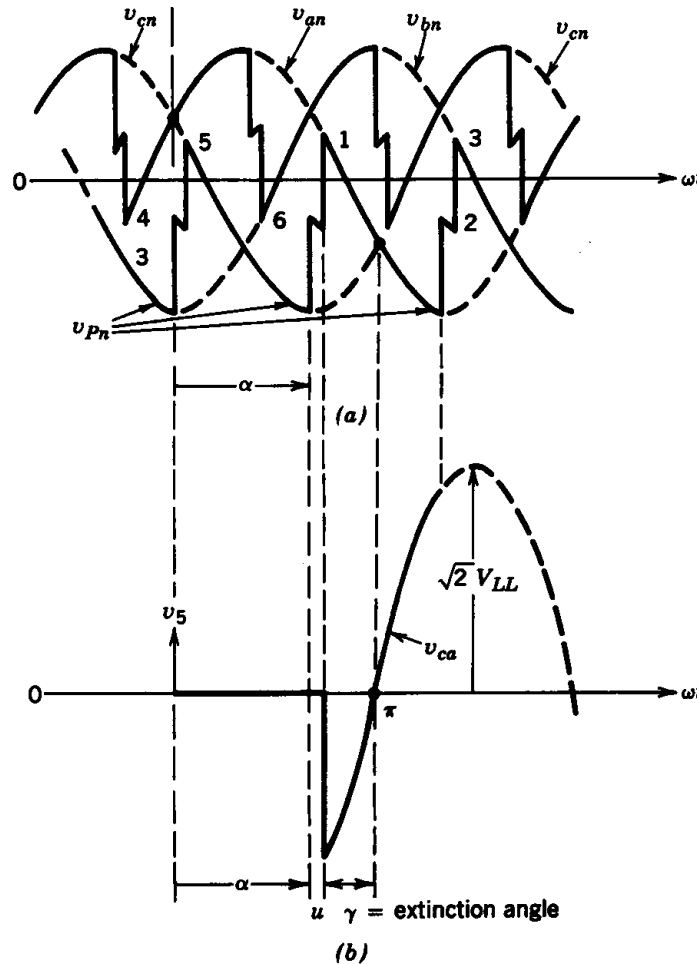


Figure 6-34 Voltage across a thyristor in the inverter mode.

- Importance of extinction angle

Thyristor Converters: Voltage Notching

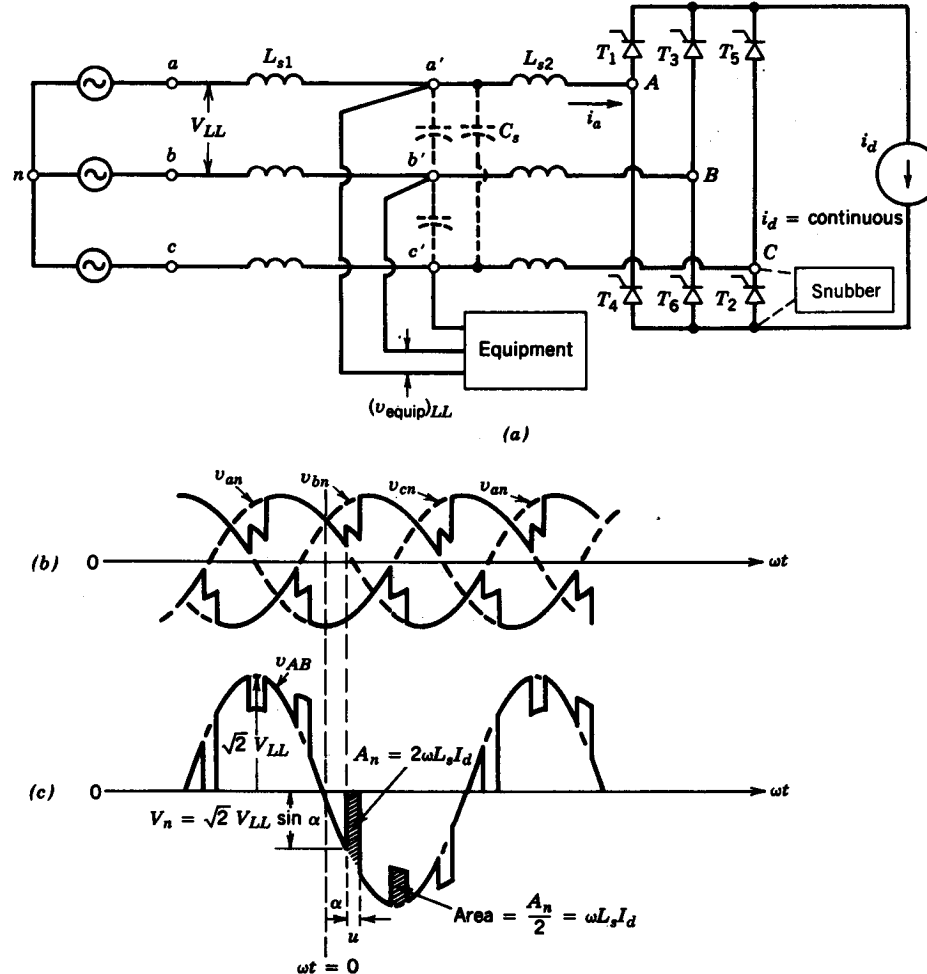


Figure 6-35 Line notching in other equipment voltage: (a) circuit, (b) phase voltages, (c) line-to-line voltage v_{AB} .

- Importance of external ac-side inductance


Limits on Notching and Distortion

Table 6-2 Line Notching and Distortion Limits for 460-V Systems

<i>Class</i>	<i>Line Notch Depth</i> $\rho(\%)$	<i>Line Notch Area</i> $(V \cdot \mu s)$	<i>Voltage Total</i> <i>Harmonic Distortion</i> $(\%)$
Special applications	10	16,400	3
General system	20	22,800	5
Dedicated system	50	36,500	10

- Guidelines

Thyristor Converter Representation

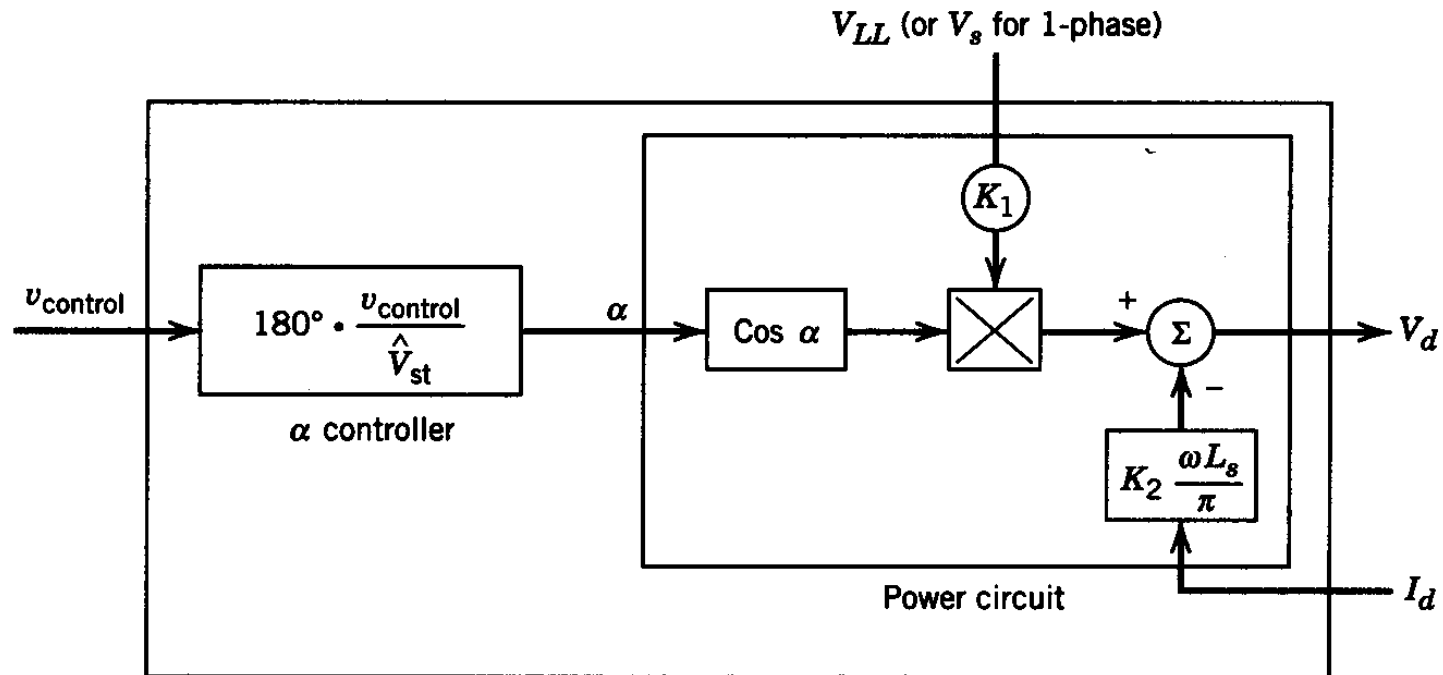

Single-phase full-bridge: $K_1 = 0.9$, $K_2 = 2$

Three-phase full-bridge: $K_1 = 1.35$, $K_2 = 3$

Figure 6-36 Summary of thyristor converter output voltage with a dc current I_d .

- Functional block diagram