


# Chapter 7

## DC-DC Switch-Mode Converters

<b>Chapter 7 dc–dc Switch-Mode Converters</b>	<b>161</b>
7-1 Introduction	161
7-2 Control of dc–dc Converters	162
7-3 Step-Down (Buck) Converter	164
7-4 Step-Up (Boost) Converter	172
7-5 Buck–Boost Converter	178
7-6 Cúk dc–dc Converter	184
7-7 Full Bridge dc–dc Converter	188
7-8 dc–dc Converter Comparison	195
<i>Summary</i>	<i>196</i>
<i>Problems</i>	<i>197</i>
<i>References</i>	<i>199</i>

- dc-dc converters for switch-mode dc power supplies and dc-motor drives


# Block Diagram of DC-DC Converters

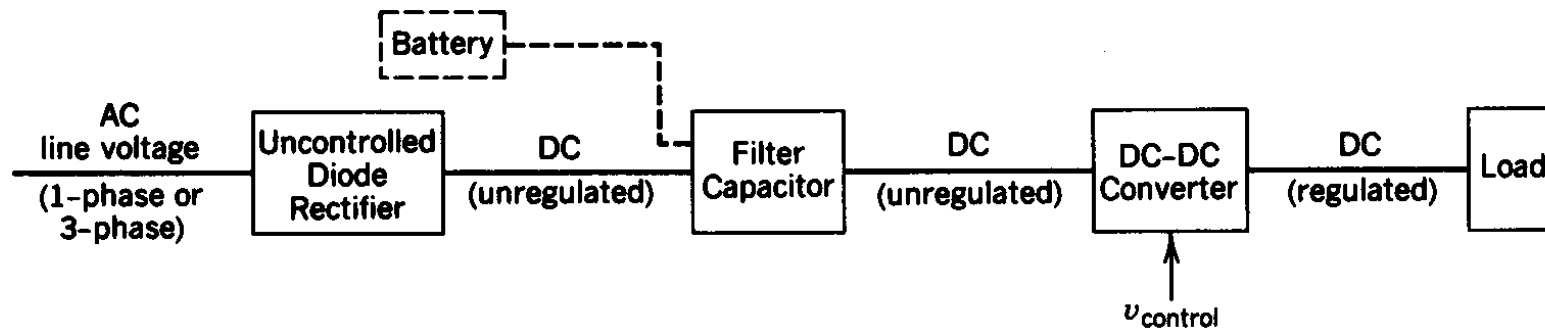

**Figure 7-1** A dc-dc converter system.

- Functional block diagram

# Stepping Down a DC Voltage

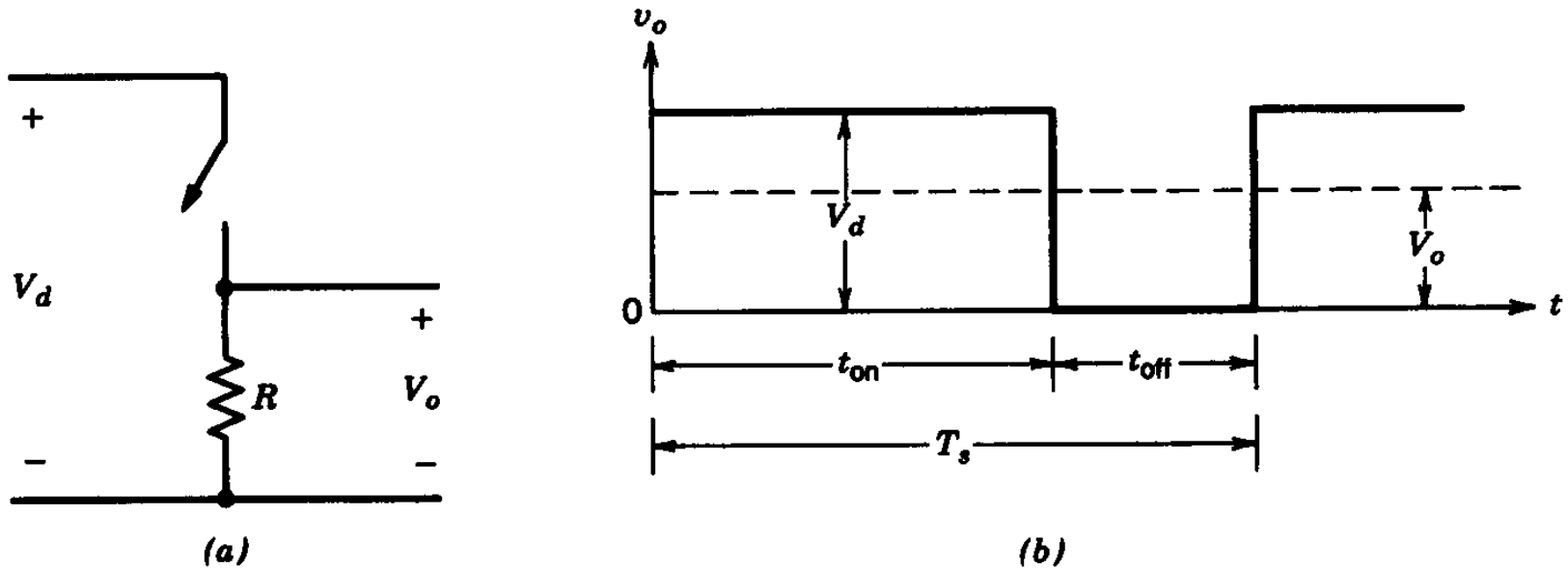

**Figure 7-2** Switch-mode dc–dc conversion.

- A simple approach that shows the evolution

# Pulse-Width Modulation in DC-DC Converters

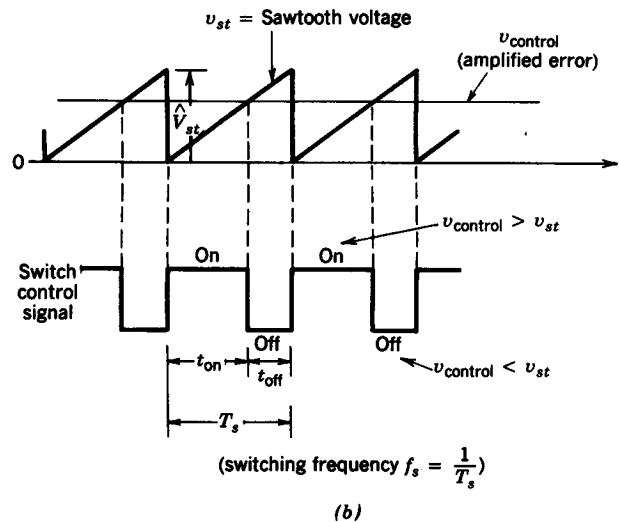
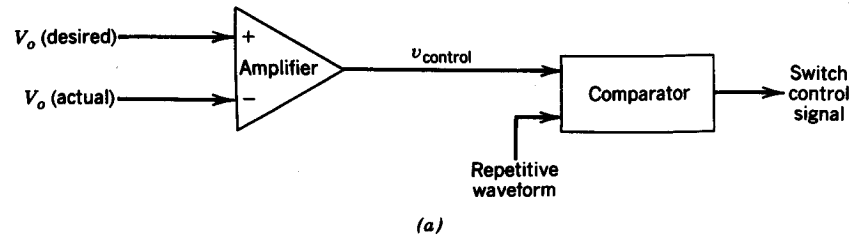


Figure 7-3 Pulse-width modulator: (a) block diagram; (b) comparator signals.

- Role of PWM

# Step-Down DC-DC Converter


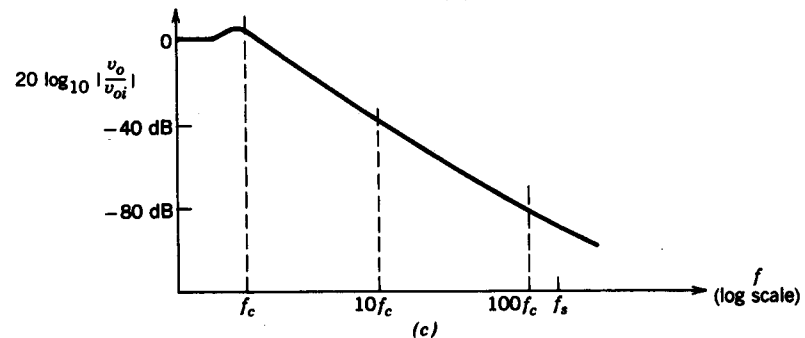
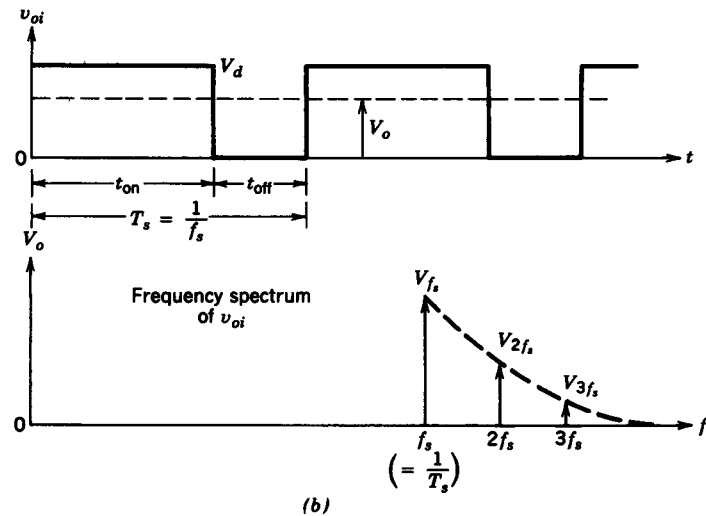
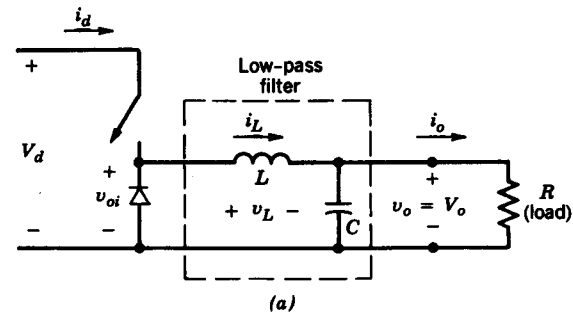


Figure 7-4 Step-down dc-dc converter.

- Pulsating input to the low-pass filter


# Step-Down DC-DC Converter: Waveforms

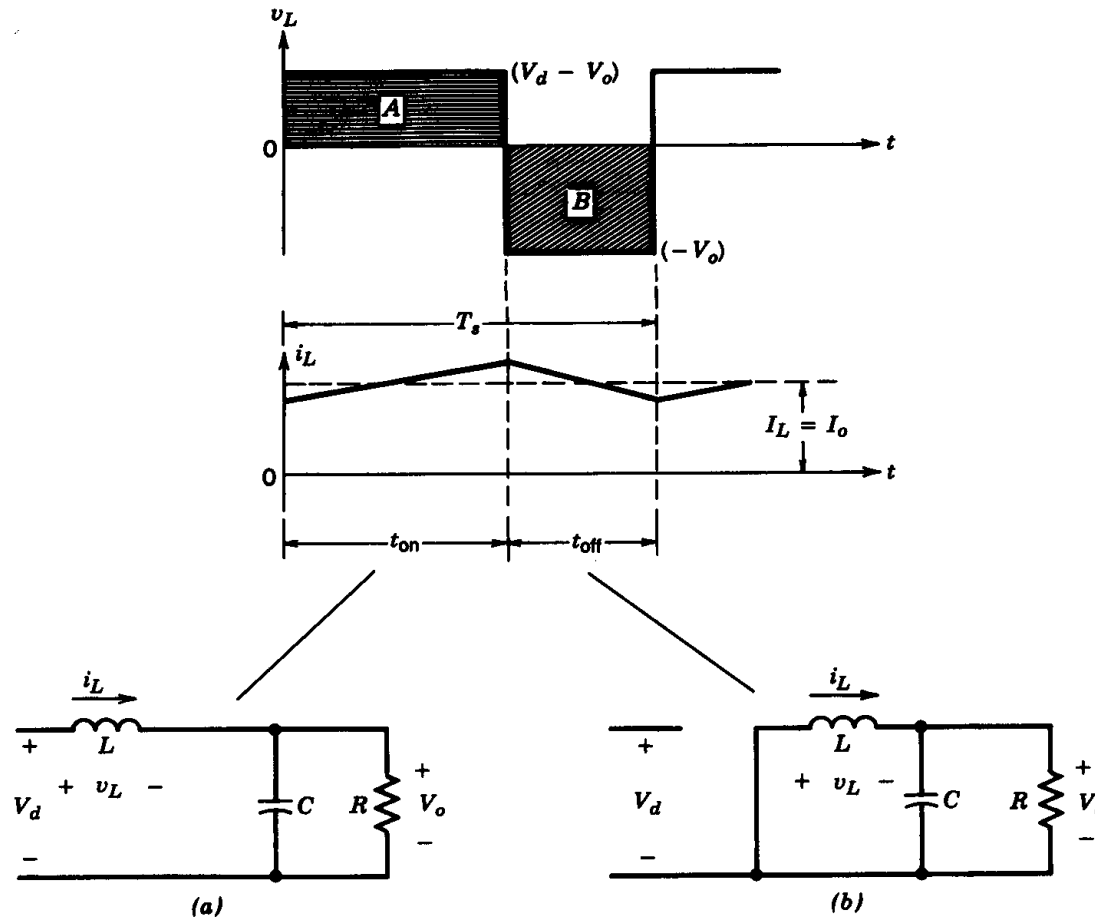

**Figure 7-5** Step-down converter circuit states (assuming  $i_L$  flows continuously): (a) switch on; (b) switch off.

- Steady state; inductor current flows continuously


# Step-Down DC-DC Converter: Waveforms at the boundary of Cont./Discont. Conduction

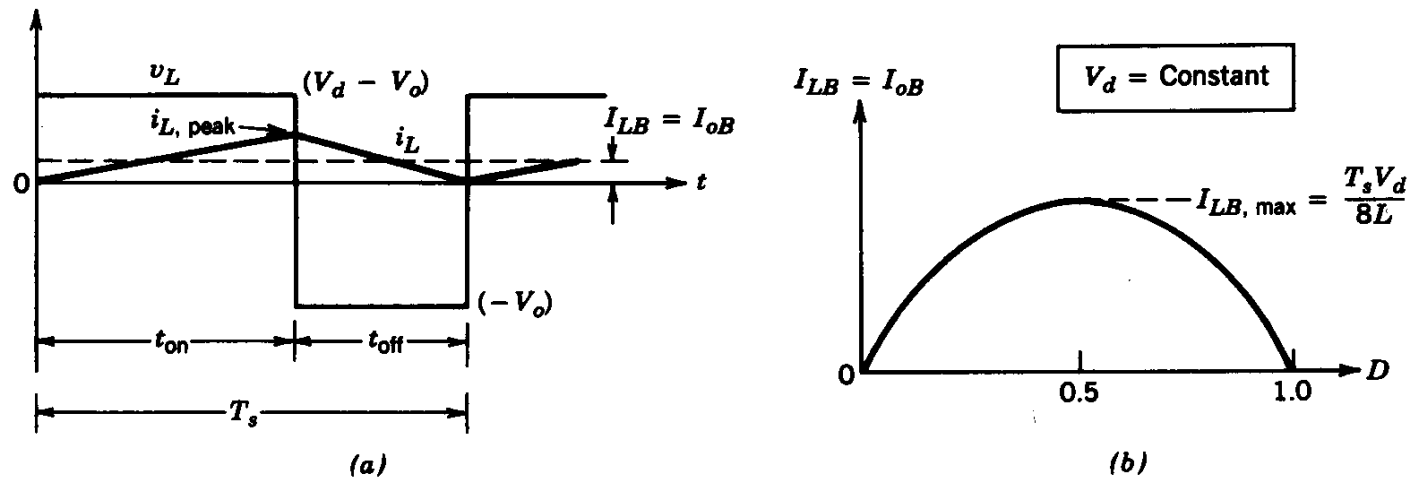

**Figure 7-6** Current at the boundary of continuous–discontinuous conduction: (a) current waveform; (b)  $I_{LB}$  versus  $D$  keeping  $V_d$  constant.

- Critical current below which inductor current becomes discontinuous

# Step-Down DC-DC Converter: Discontinuous Conduction Mode

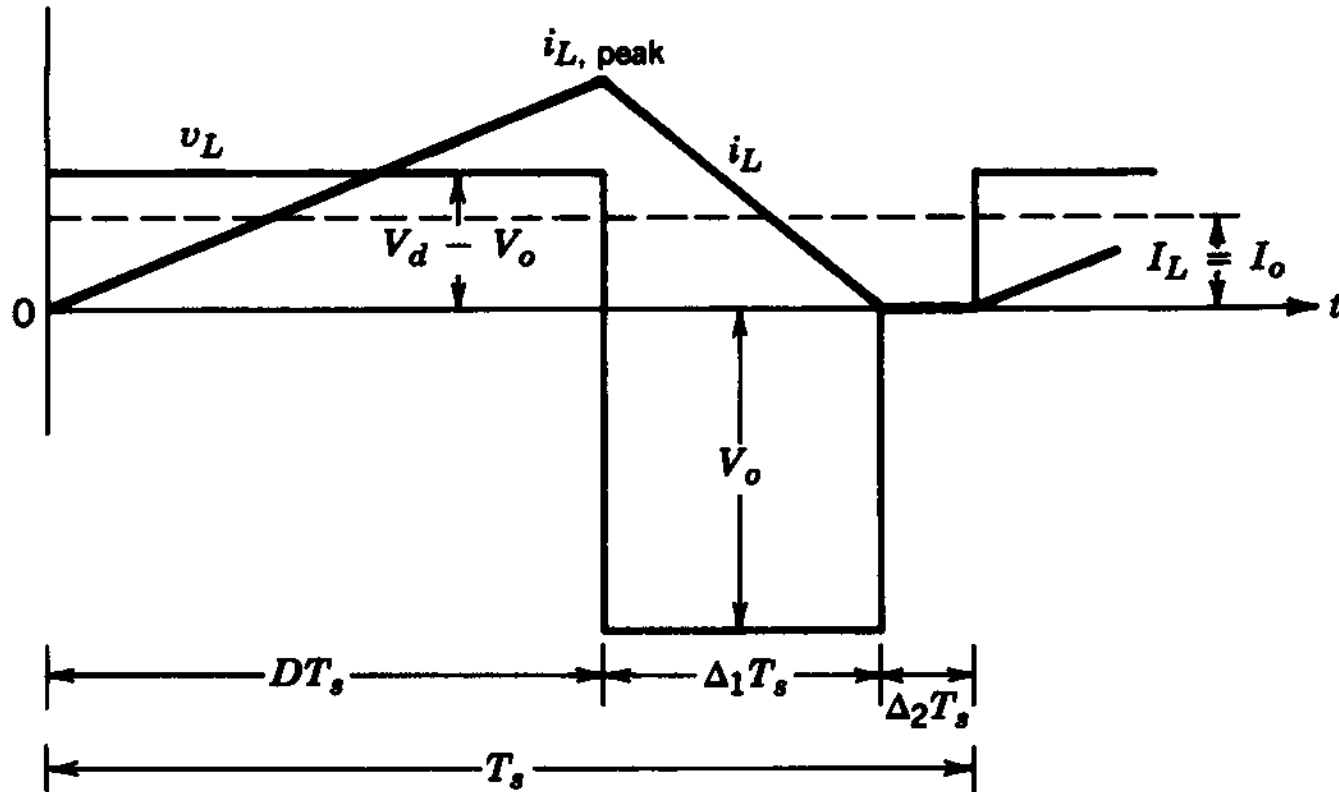

**Figure 7-7** Discontinuous conduction in step-down converter.

- Steady state; inductor current discontinuous



# Step-Down DC-DC Converter: Limits of Cont./Discont. Conduction


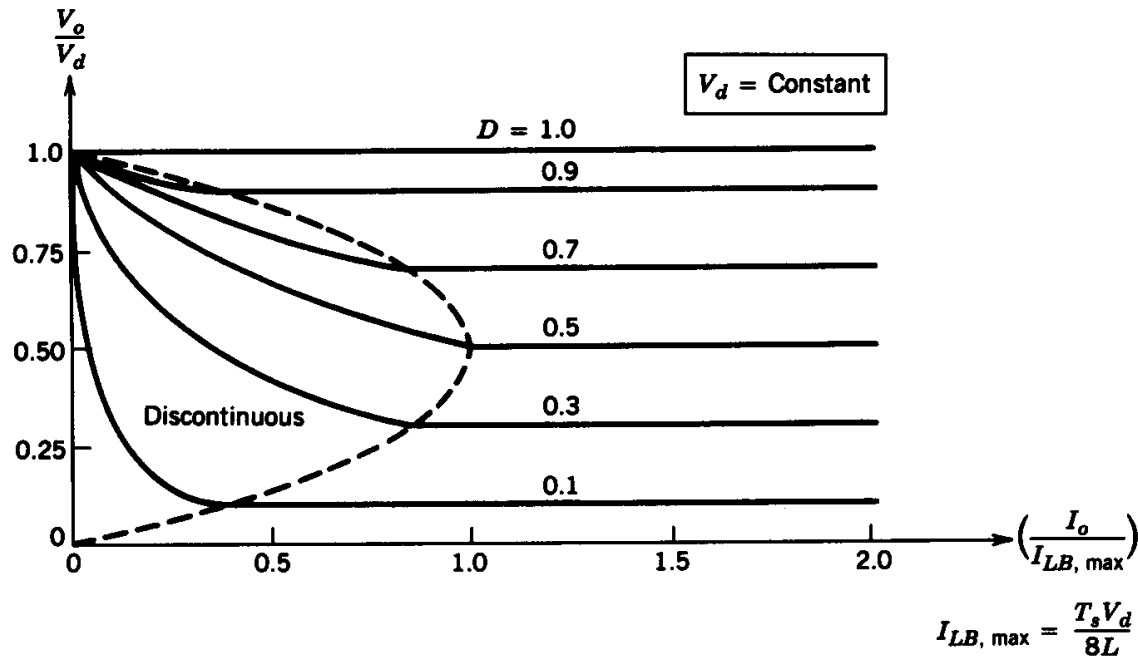


Figure 7-8 Step-down converter characteristics keeping  $V_d$  constant.

- The duty-ratio of 0.5 has the highest value of the critical current

# Step-Down DC-DC Converter: Limits of Cont./Discont. Conduction

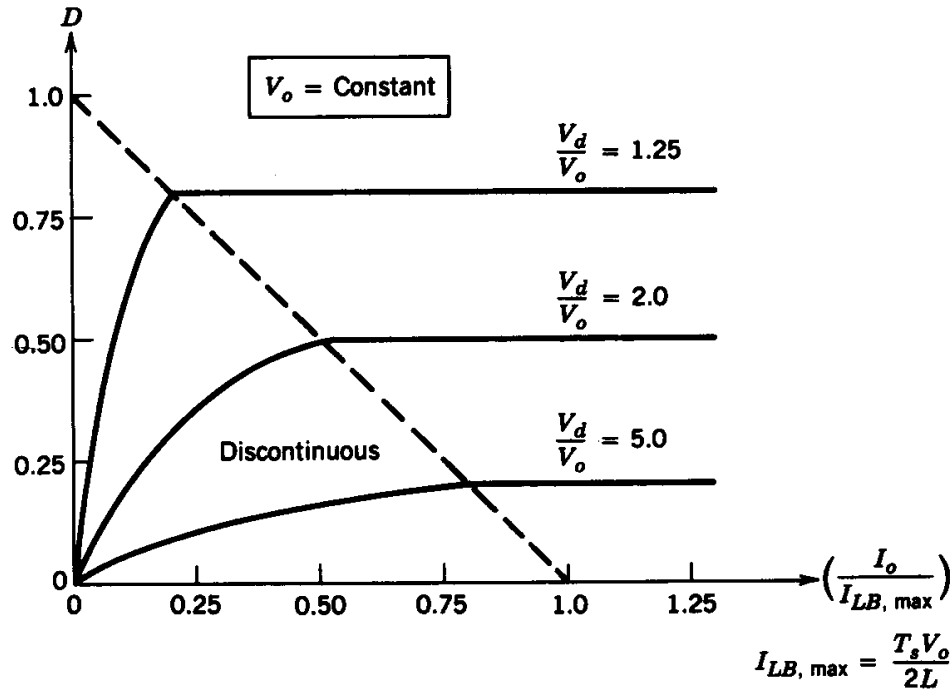

**Figure 7-9** Step-down converter characteristics keeping  $V_o$  constant.

- Output voltage is kept constant

# Step-Down Conv.: Output Voltage Ripple


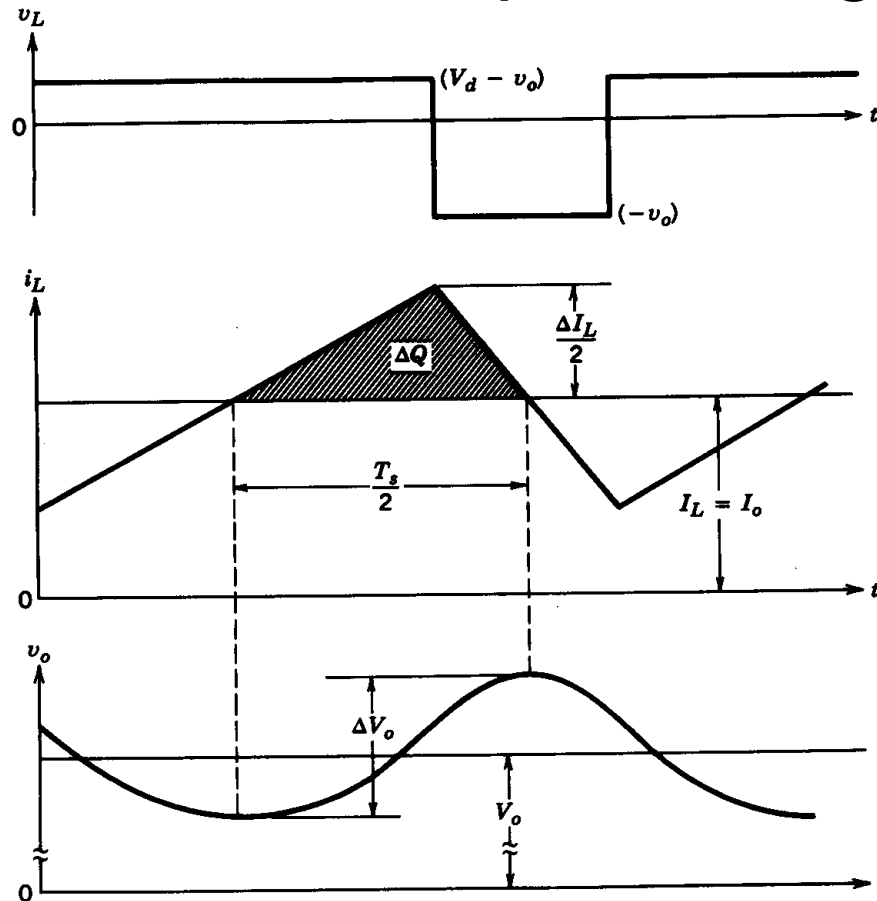


Figure 7-10 Output voltage ripple in a step-down converter.

- ESR is assumed to be zero


# Step-Up DC-DC Converter

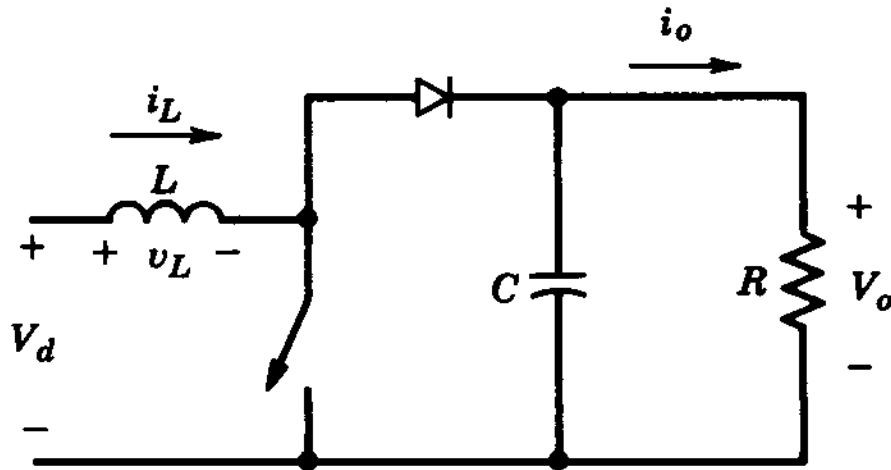

**Figure 7-11** Step-up dc–dc converter.

- Output voltage must be greater than the input


# Step-Up DC-DC Converter Waveforms

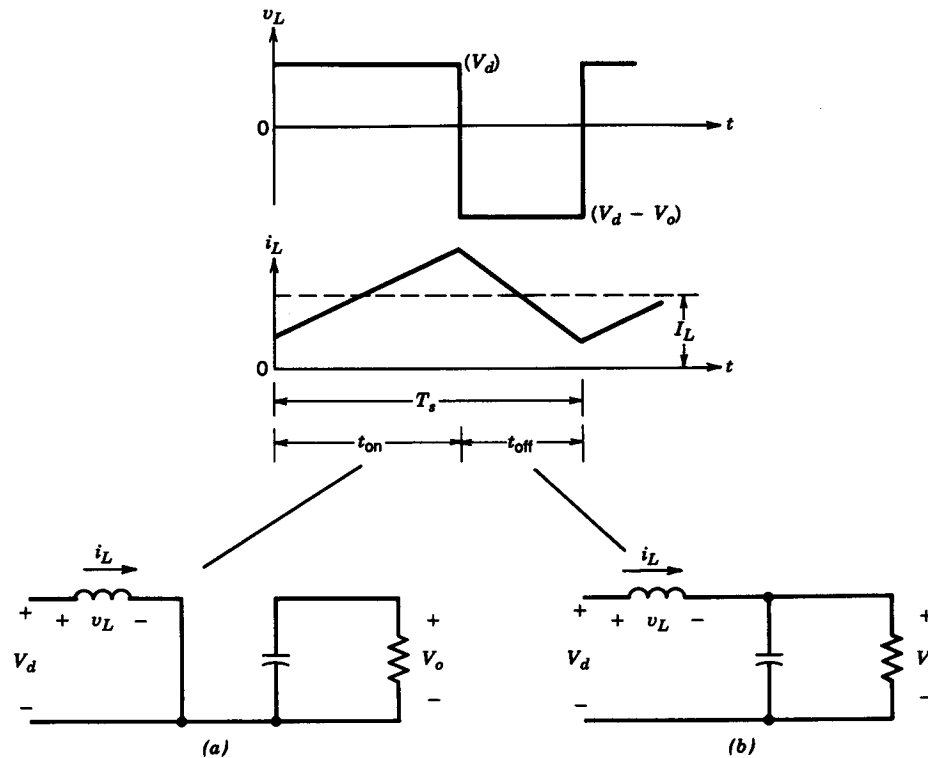

**Figure 7-12** Continuous-conduction mode: (a) switch on; (b) switch off.

- Continuous current conduction mode


# Step-Up DC-DC Converter: Limits of Cont./Discont. Conduction

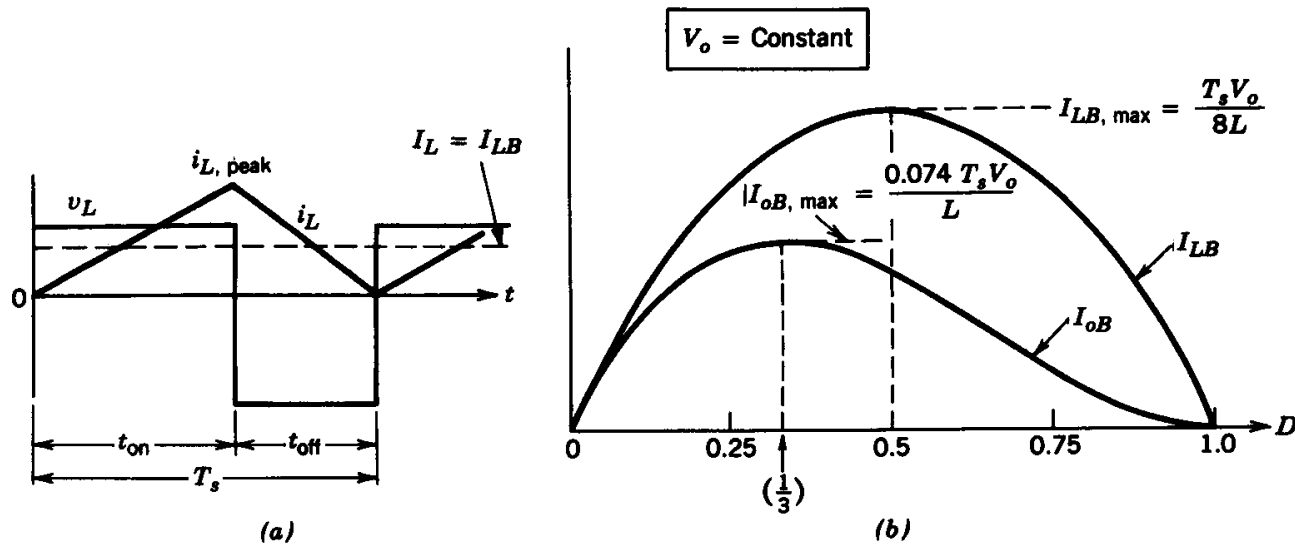

**Figure 7-13** Step-up dc–dc converter at the boundary of continuous–discontinuous conduction.

- The output voltage is held constant

# Step-Up DC-DC Converter: Discont. Conduction

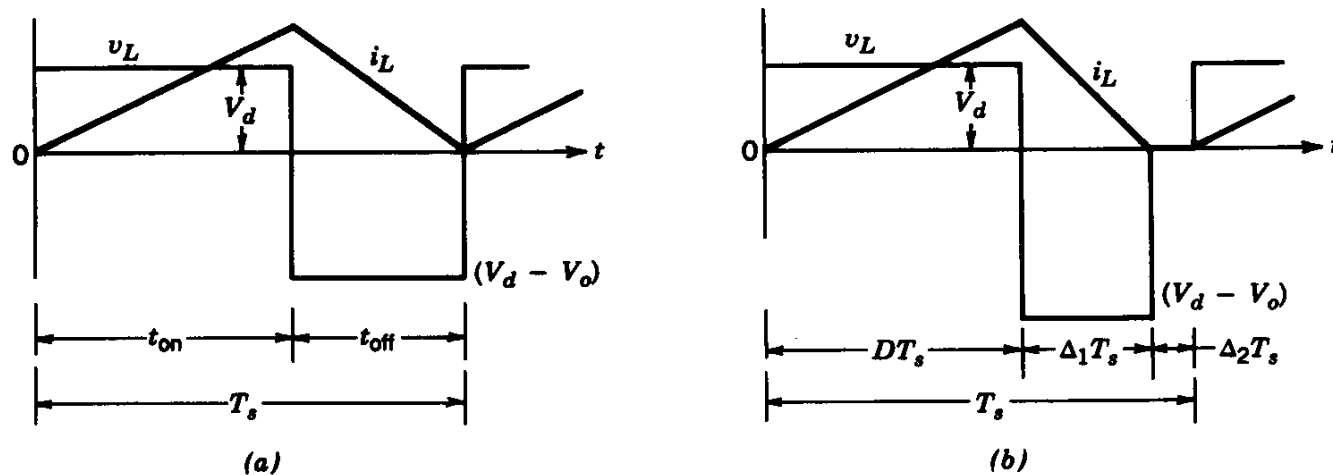

**Figure 7-14** Step-up converter waveforms: (a) at the boundary of continuous-discontinuous conduction; (b) at discontinuous conduction.

- Occurs at light loads

# Step-Up DC-DC Converter: Limits of Cont./Discont. Conduction


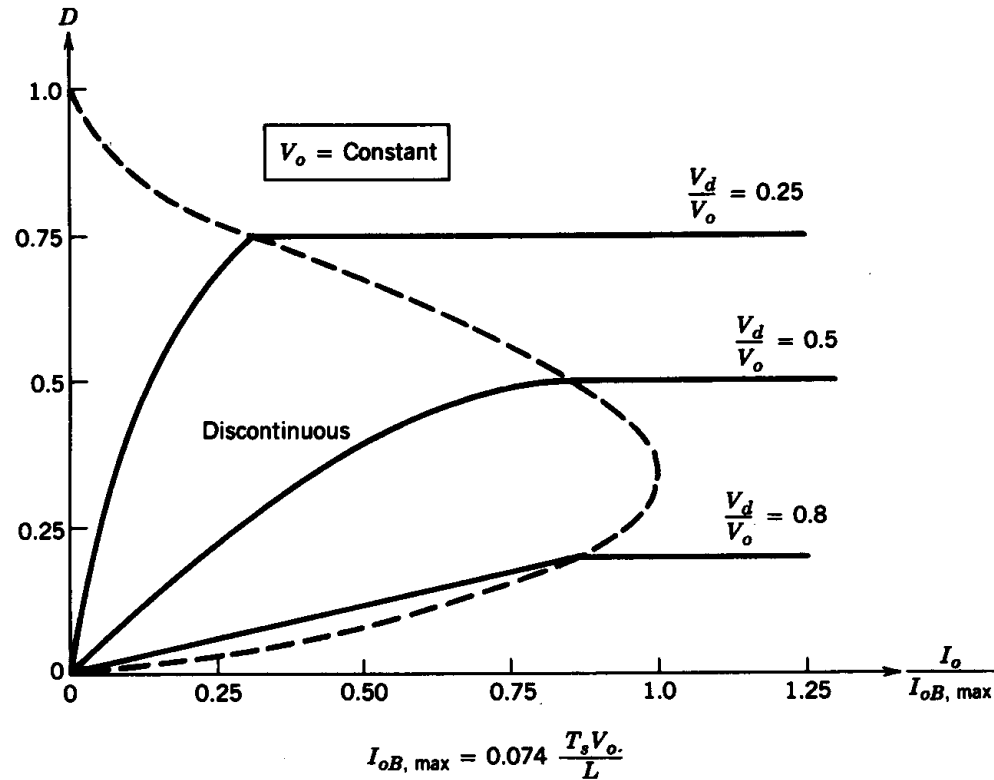


Figure 7-15 Step-up converter characteristics keeping  $V_o$  constant.

- The output voltage is held constant

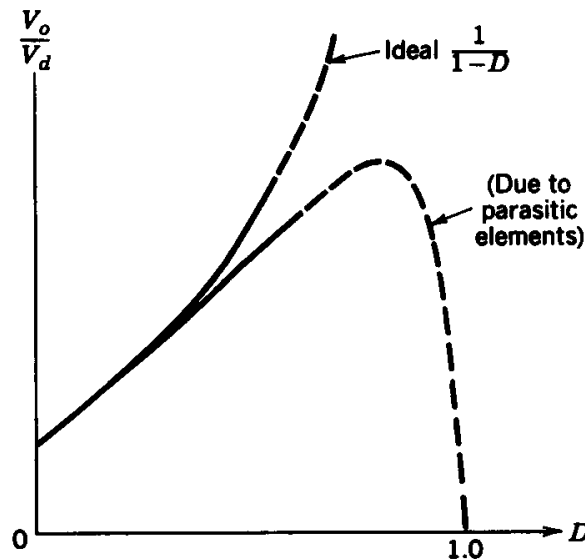


# Step-Up DC-DC Converter: Effect of Parasitics



**Figure 7-16** Effect of parasitic elements on voltage conversion ratio (step-up converter).

- The duty-ratio is generally limited before the parasitic effects become significant


# Step-Up DC-DC Converter Output Ripple

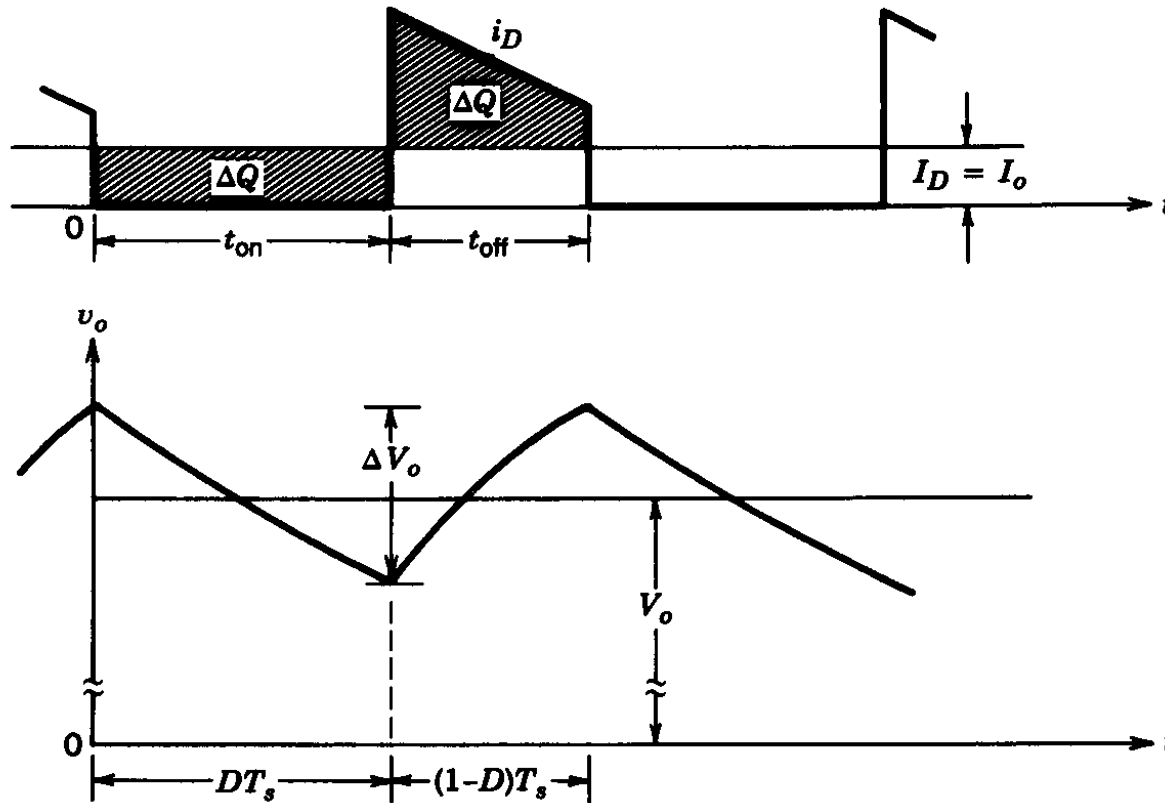

**Figure 7-17** Step-up converter output voltage ripple.

- ESR is assumed to be zero

# Step-Down/Up DC-DC Converter

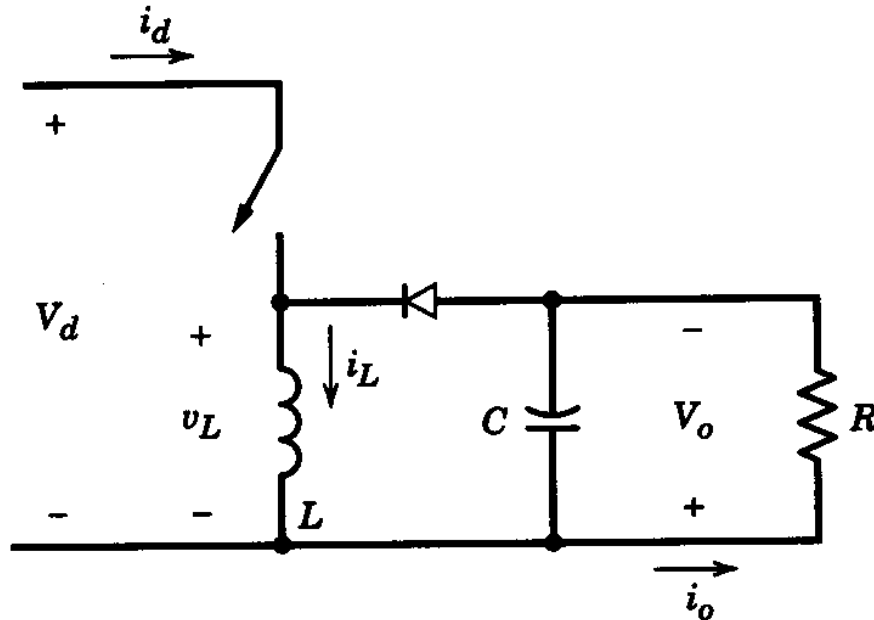

**Figure 7-18** Buck–boost converter.

- The output voltage can be higher or lower than the input voltage

# Step-Up DC-DC Converter: Waveforms

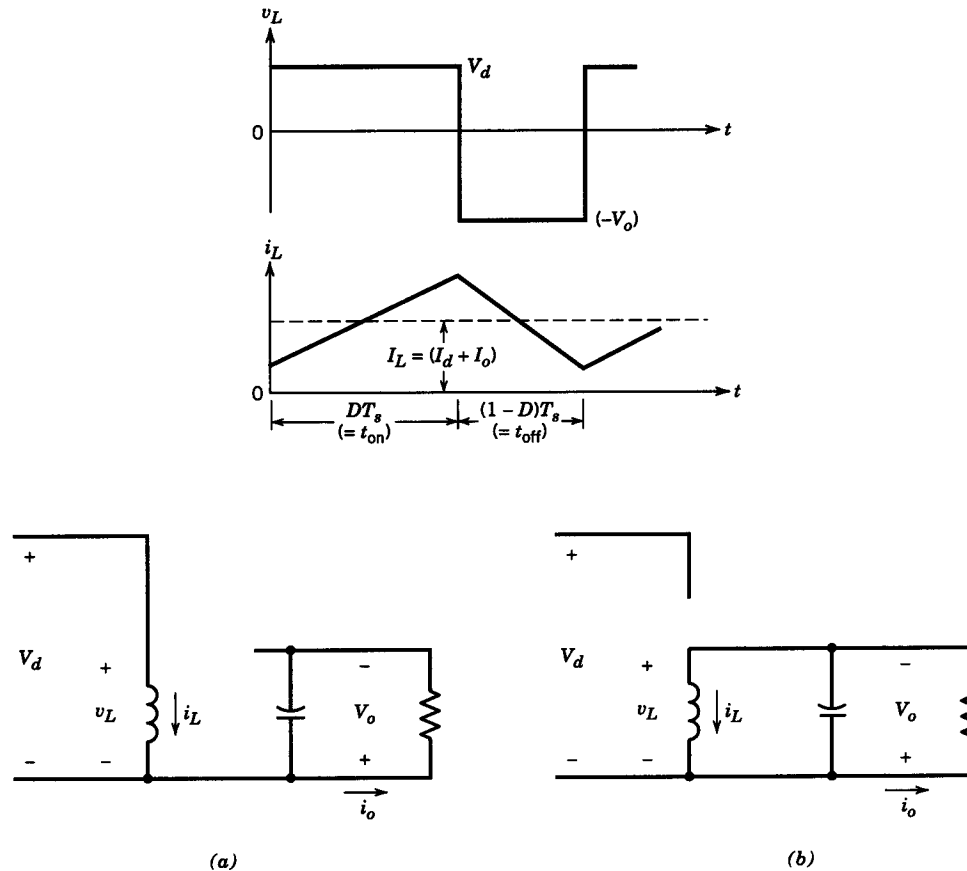


Figure 7-19 Buck-boost converter ( $i_L > 0$ ): (a) switch on; (b) switch off.

- Continuation conduction mode

# Step-Up DC-DC Converter: Limits of Cont./Discont. Conduction


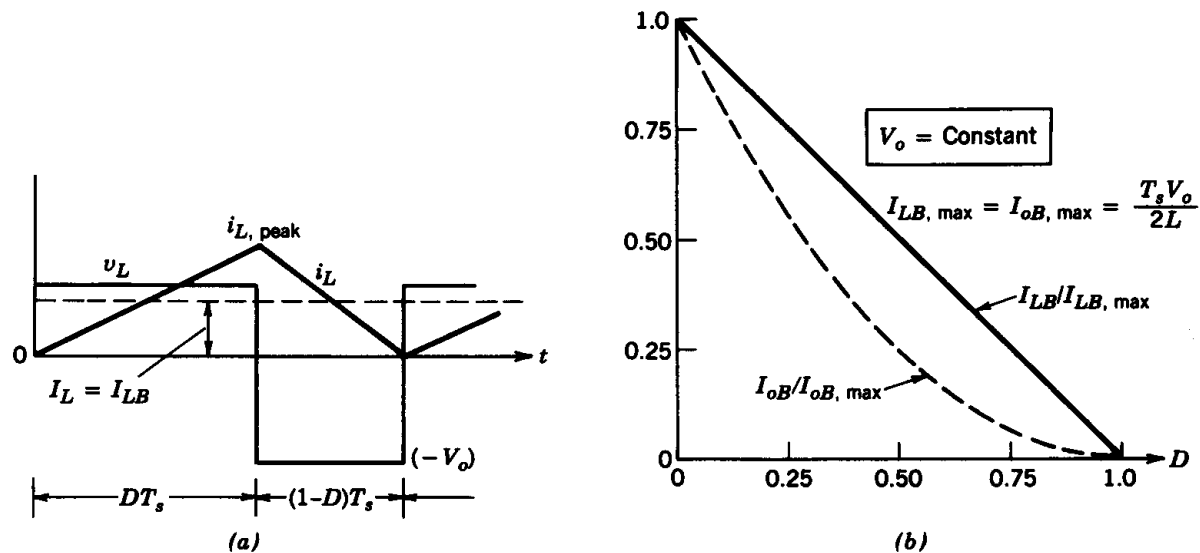


Figure 7-20 Buck-boost converter: boundary of continuous-discontinuous conduction.

- The output voltage is held constant

# Step-Up DC-DC Converter: Discontinuous Conduction Mode

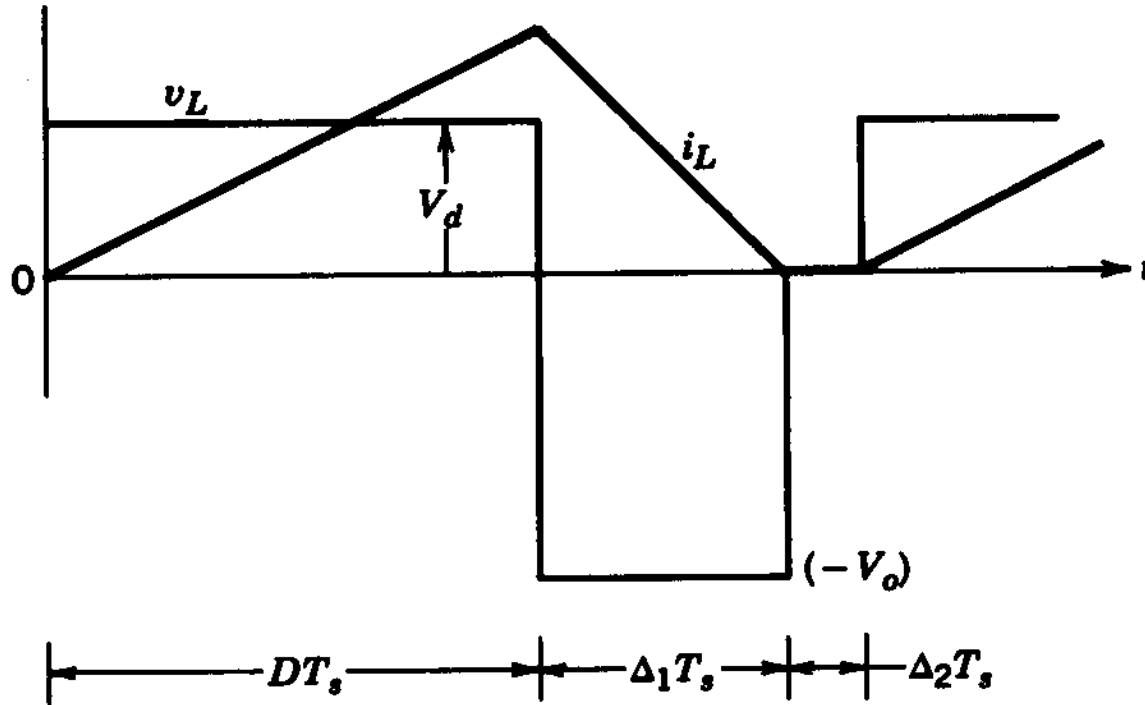

**Figure 7-21** Buck–boost converter waveforms in a discontinuous-conduction mode.

- This occurs at light loads

# Step-Up DC-DC Converter: Limits of Cont./Discont. Conduction

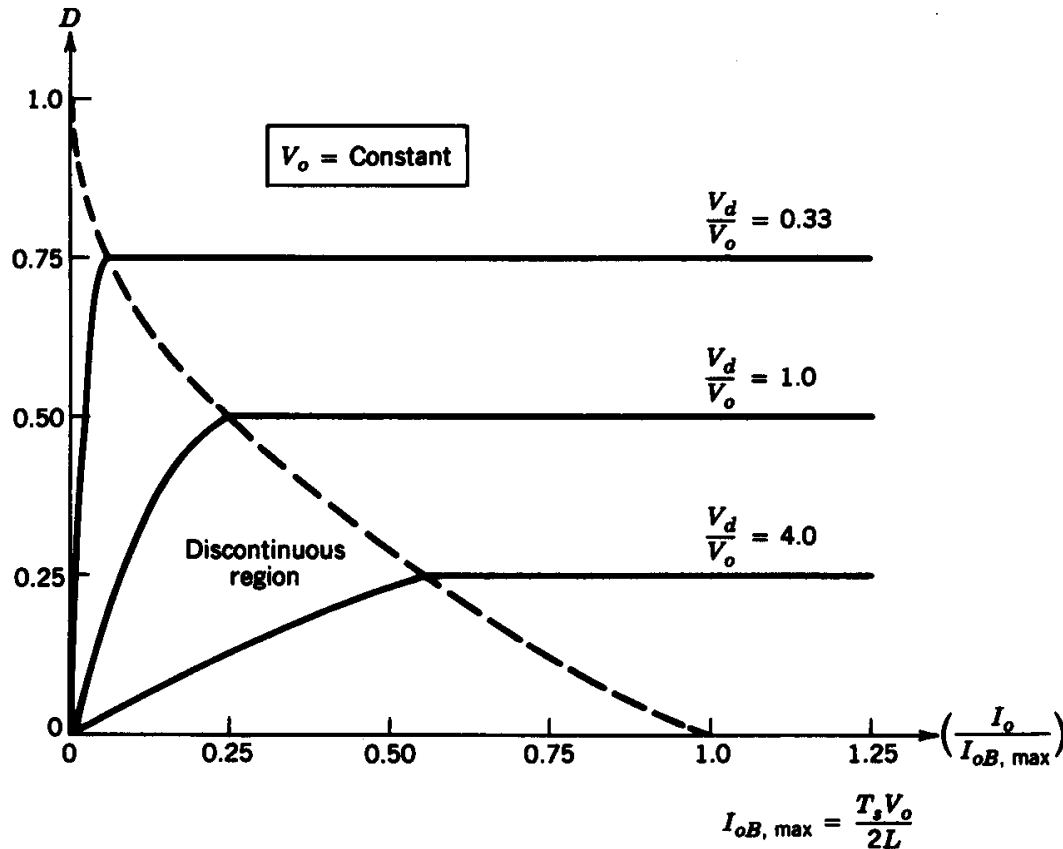
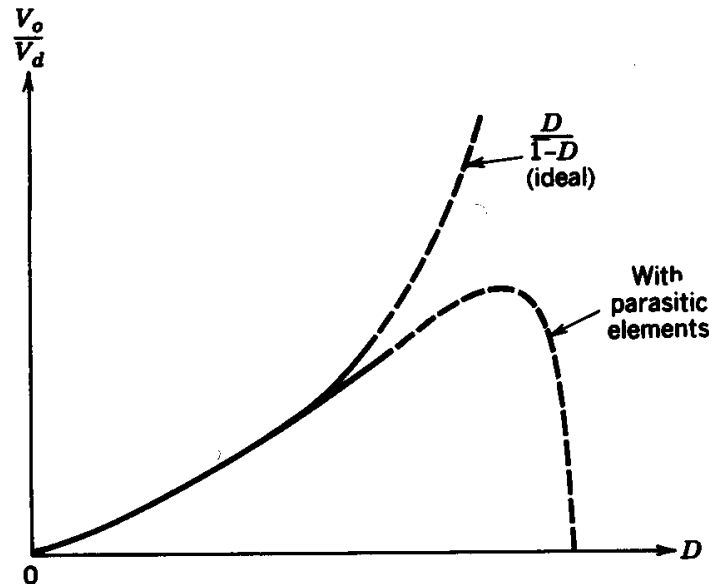


Figure 7-22 Buck-boost converter characteristics keeping  $V_o$  constant.

- The output voltage is held constant

# Step-Up DC-DC Converter: Effect of Parasitics

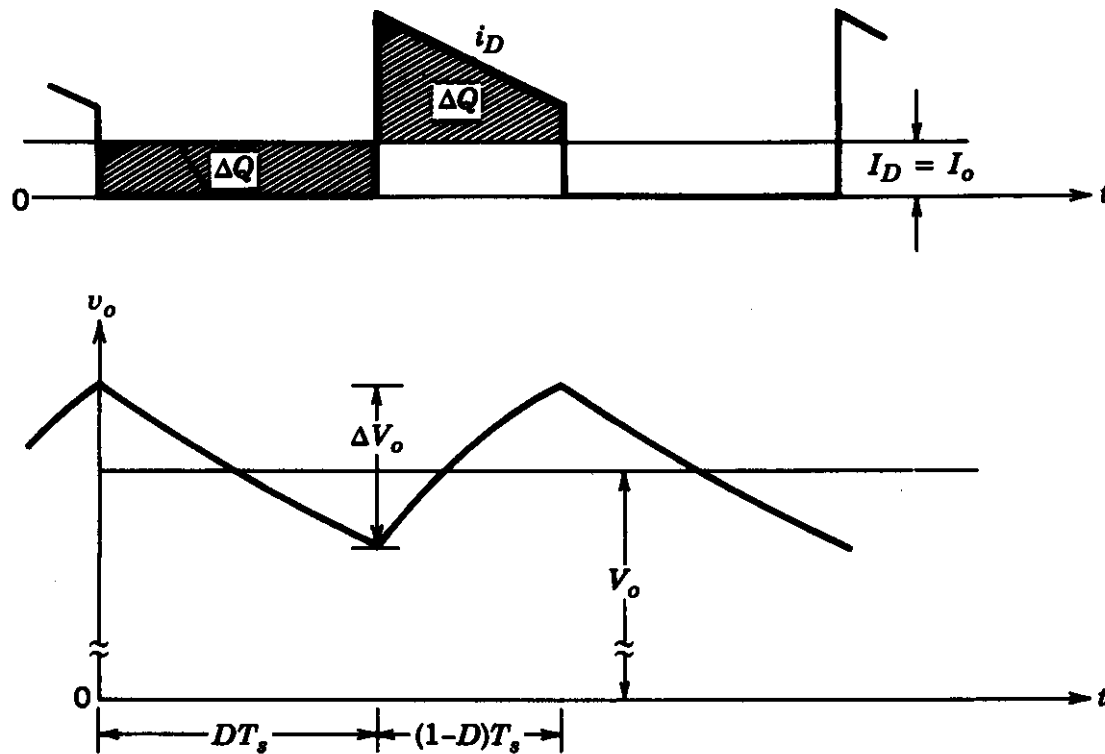


**Figure 7-23** Effect of parasitic elements on the voltage conversion ratio in a buck-boost converter.

- The duty-ratio is limited to avoid these parasitic effects from becoming significant




# Step-Up DC-DC Converter: Output Voltage Ripple



**Figure 7-24** Output voltage ripple in a buck–boost converter.

- ESR is assumed to be zero


# Cuk DC-DC Converter

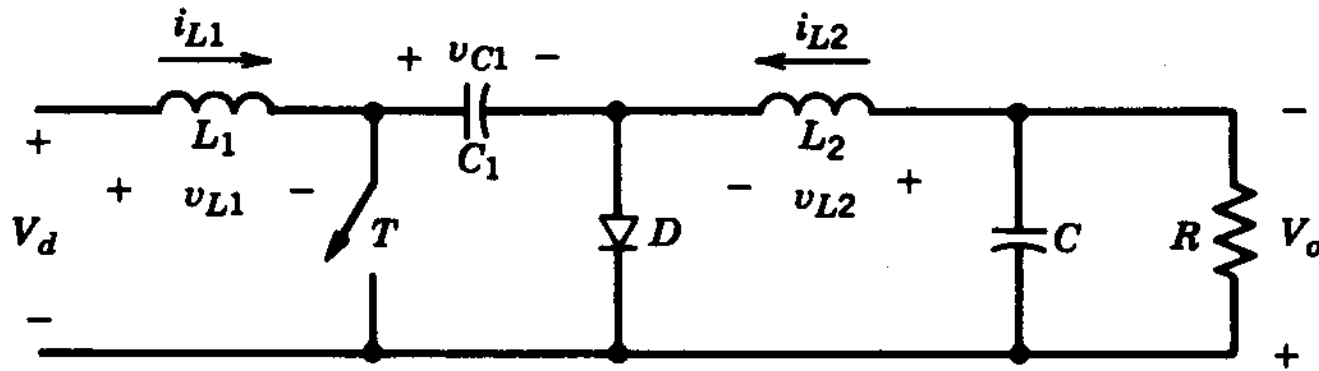

**Figure 7-25** Cúk converter.

- The output voltage can be higher or lower than the input voltage

# Cuk DC-DC Converter: Waveforms

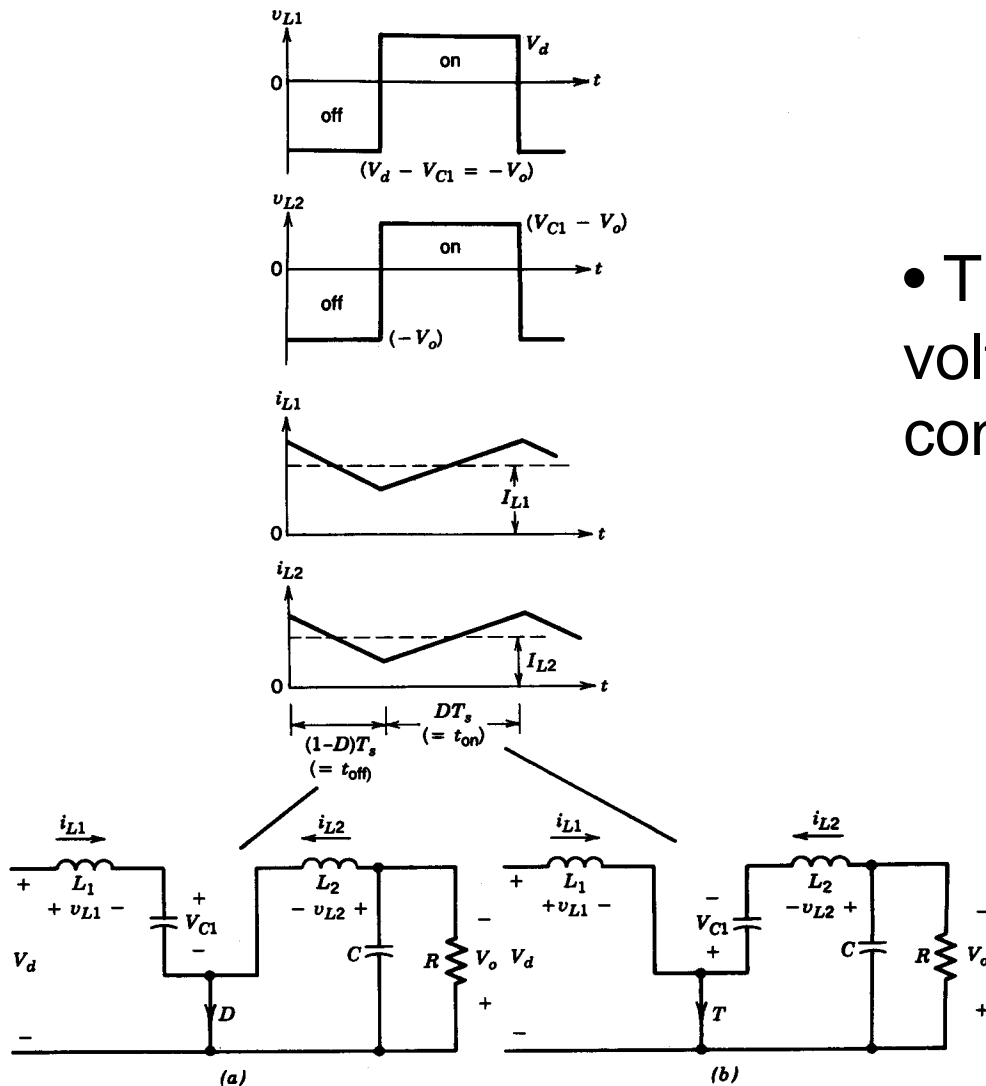

- The capacitor voltage is assumed constant

Figure 7-26 Cuk converter waveforms: (a) switch off; (b) switch on.

# Converter for DC-Motor Drives

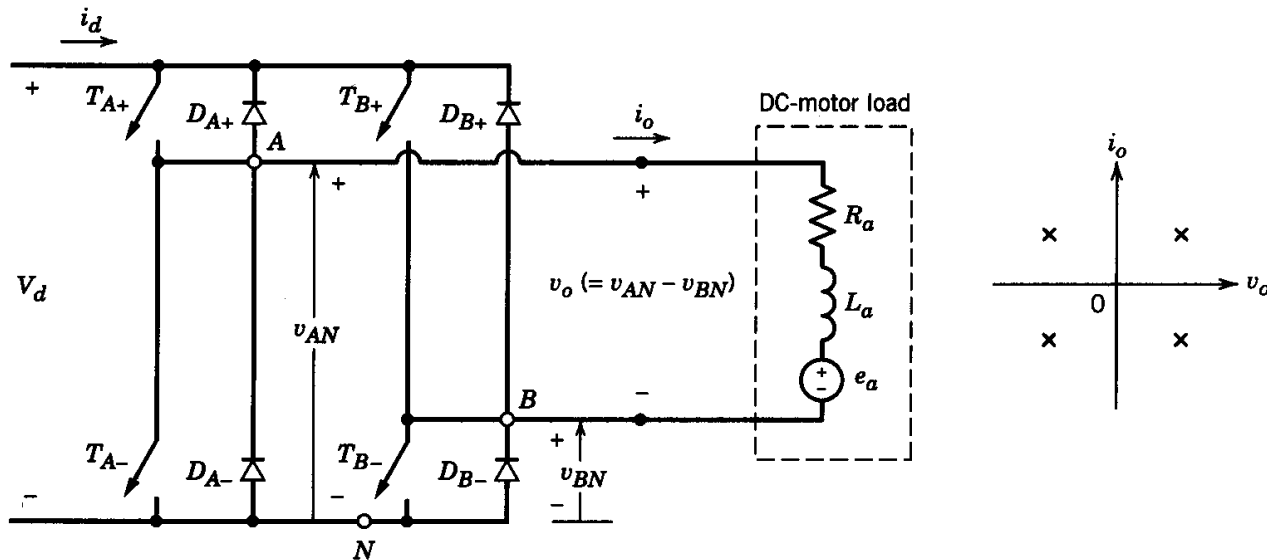


Figure 7-27 Full-bridge dc-dc converter.

- Four quadrant operation is possible

# Converter Waveforms

- Bi-polar voltage switching

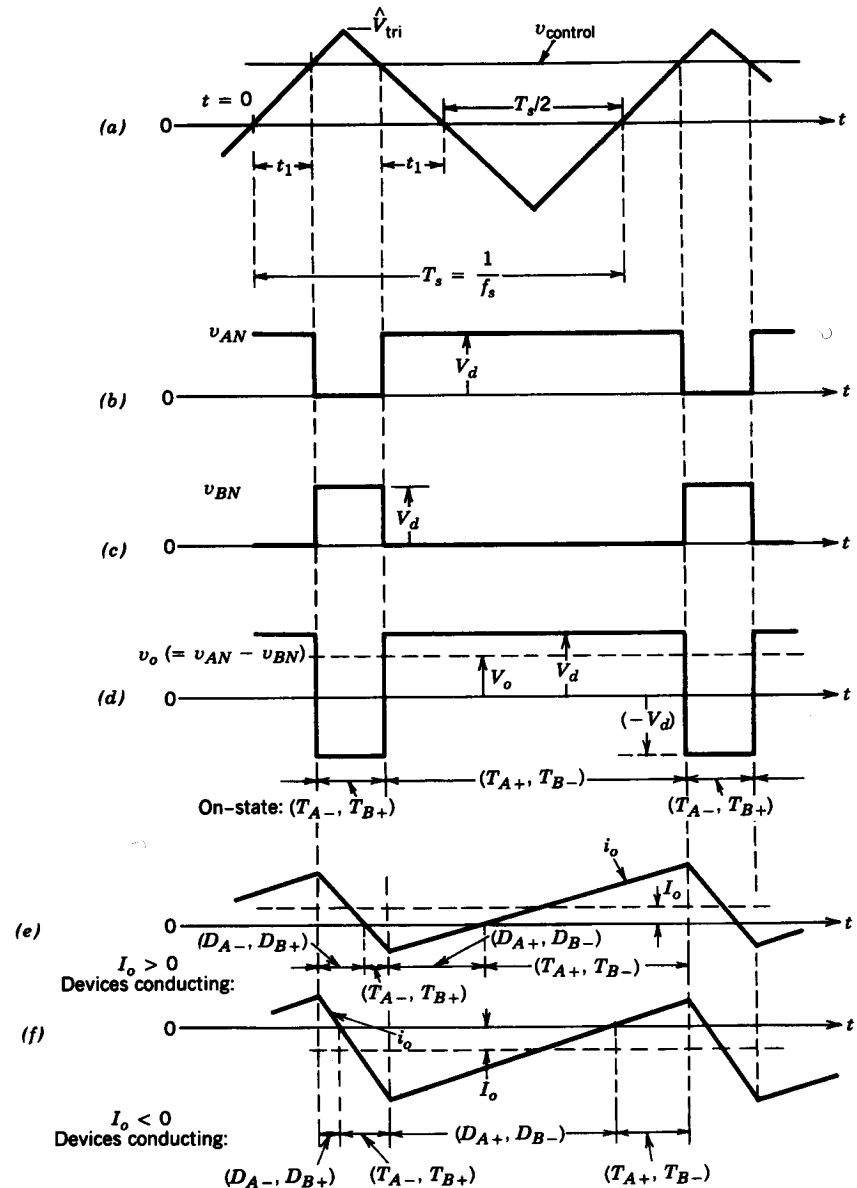


Figure 7-28 PWM with bipolar voltage switching.

# Converter Waveforms


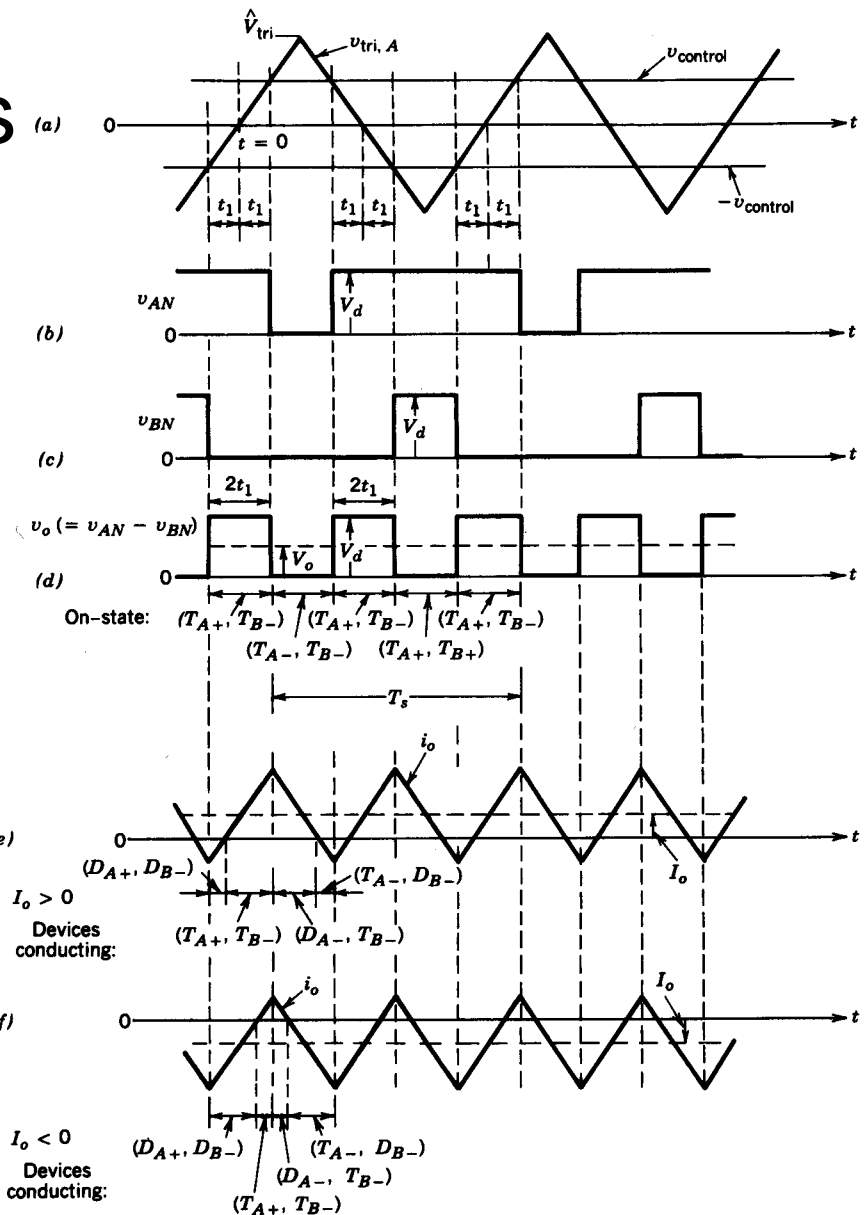


Figure 7-29 PWM with unipolar voltage switching.

- Uni-polar voltage switching


# Output Ripple in Converters for DC-Motor Drives

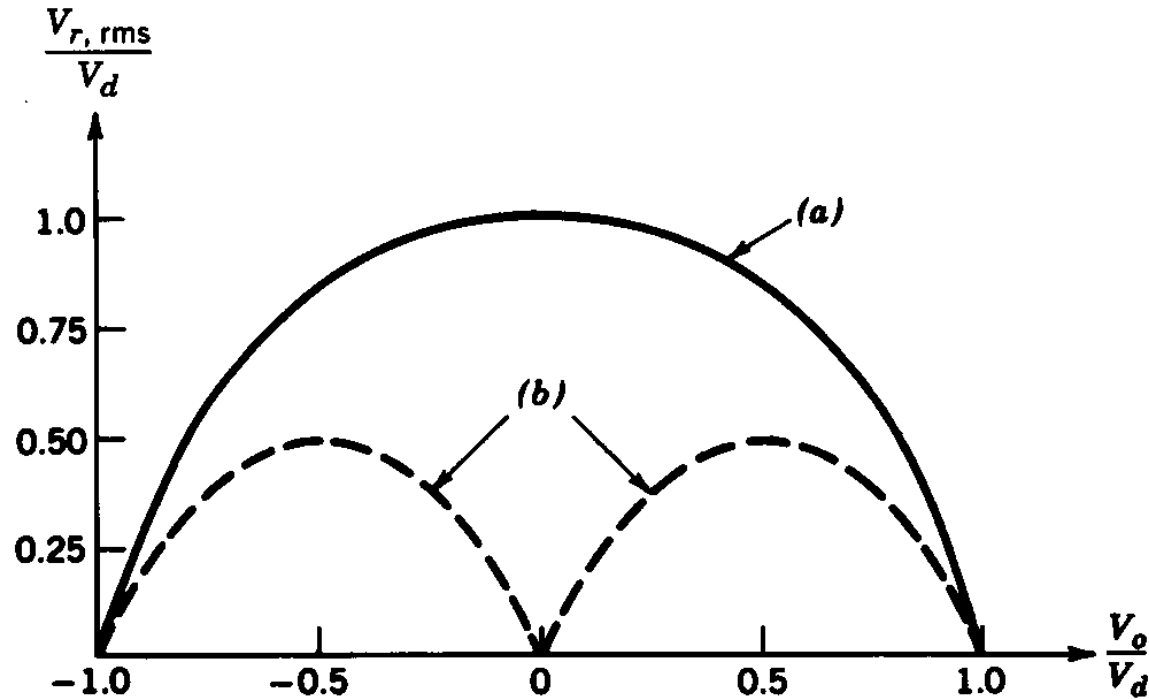

**Figure 7-30**  $V_{r,rms}$  in a full-bridge converter using PWM: (a) with bipolar voltage switching; (b) with unipolar voltage switching.

- bi-polar and uni-polar voltage switching

# Switch Utilization in DC-DC Converters

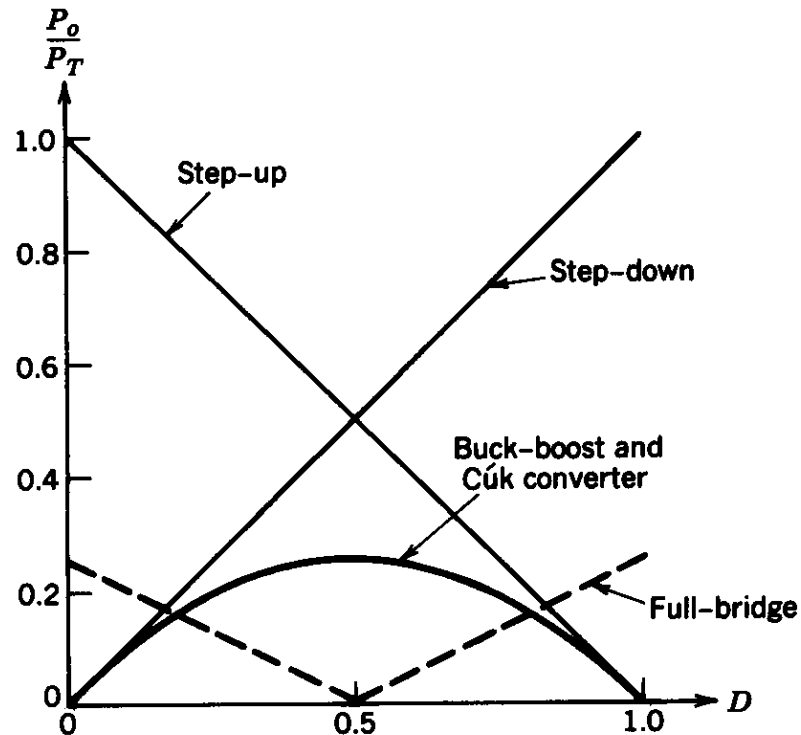


**Figure 7-31** Switch utilization in dc-dc converters.

- It varies significantly in various converters




# Equivalent Circuits in DC-DC Converters

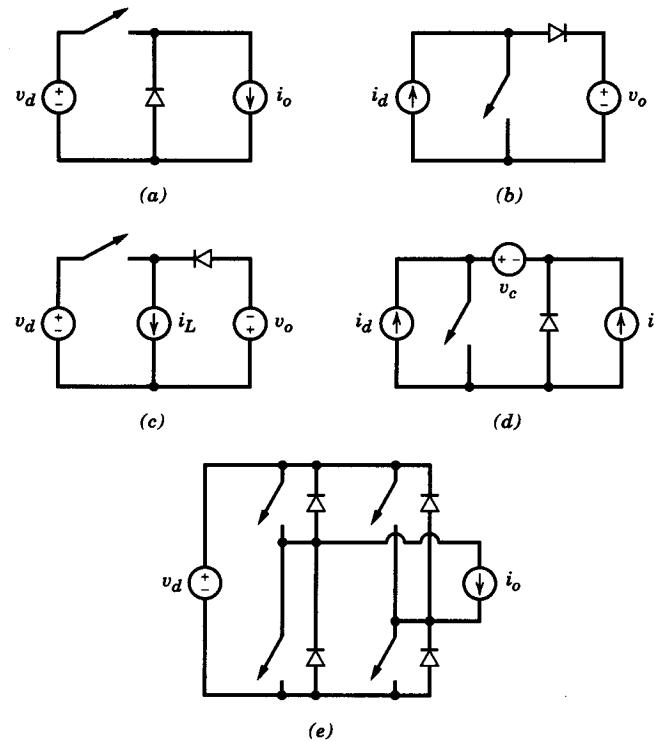

**Figure 7-32** Converter equivalent circuits: (a) step-down; (b) step-up; (c) step-down/step-up; (d) Cúk; (e) full-bridge.

- replacing inductors and capacitors by current and voltage sources, respectively

# Reversing the Power Flow in DC-DC Conv.

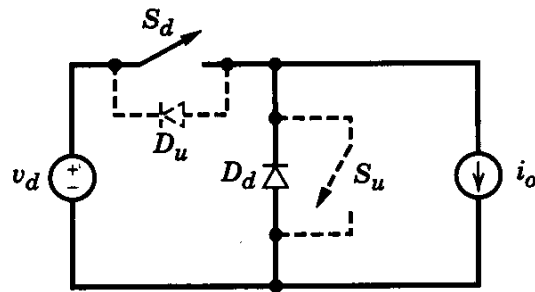

**Figure 7-33** Reversible power flow with reversible direction of the output current  $i_o$ .

- For power flow from right to left, the input current direction should also reverse